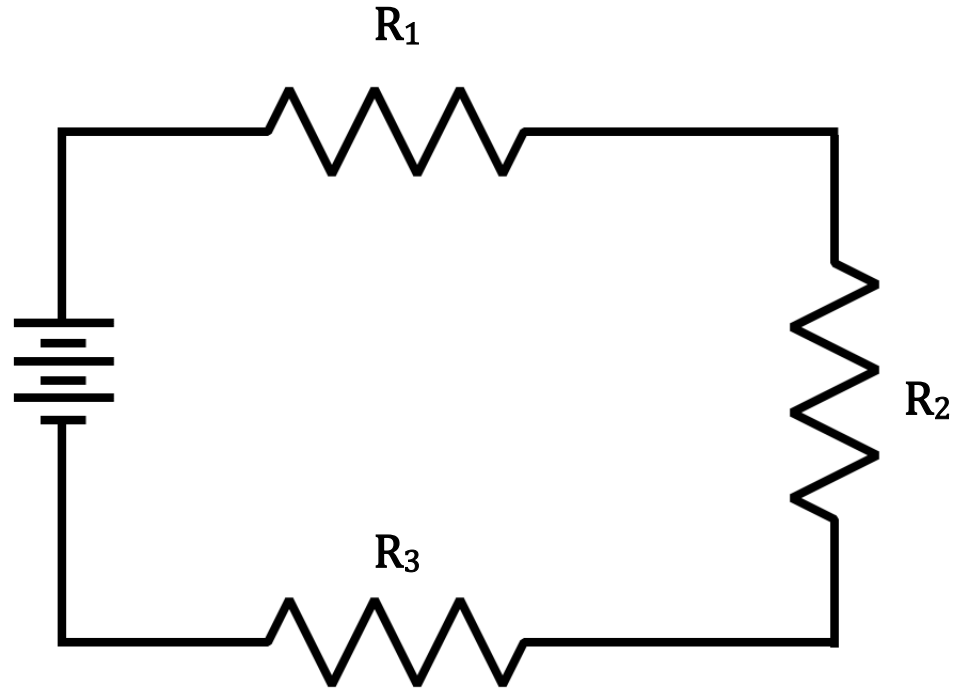


Series Circuit Math - Example 6

Series Example 6



$$P_T = 903.94 \text{ Watts}$$

$$E_1 = 60.8 \text{ volts}$$

$$E_2 = 25.08 \text{ Volts}$$

$$E_3 = 152 \text{ Volts}$$

$$I_T = \underline{\hspace{2cm}}$$

$$R_T = \underline{\hspace{2cm}}$$

$$R_2 = \underline{\hspace{2cm}}$$

$$P_2 = \underline{\hspace{2cm}}$$


$$I_3 = \underline{\hspace{2cm}}$$

$$R_1 = \underline{\hspace{2cm}}$$

$$R_3 = \underline{\hspace{2cm}}$$

$$P_3 = \underline{\hspace{2cm}}$$

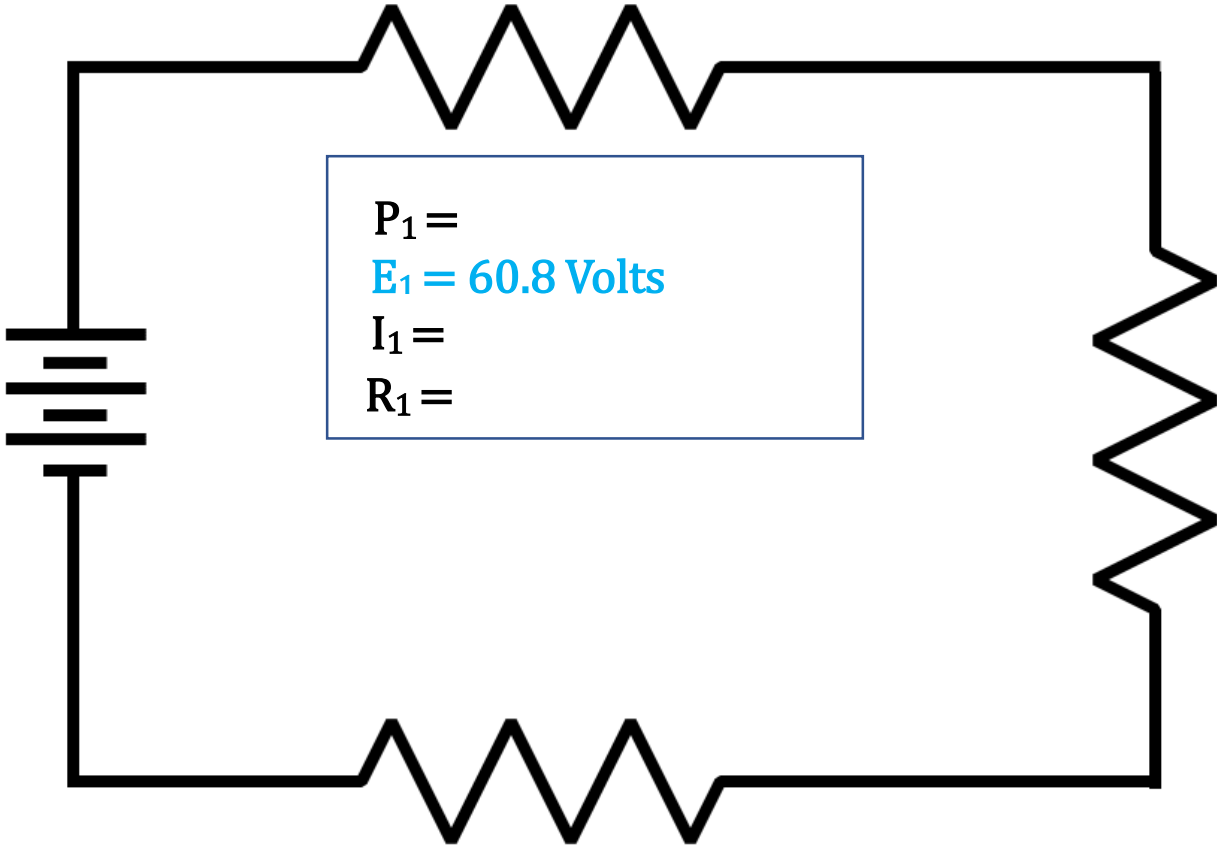$P_T = 903.94 \text{ Watts}$
 $E_T =$
 $I_T =$
 $R_T =$




$P_1 =$
 $E_1 = 60.8 \text{ Volts}$
 $I_1 =$
 $R_1 =$

$P_2 =$
 $E_2 = 25.08 \text{ Volts}$
 $I_2 =$
 $R_2 =$

$P_T = 903.94 \text{ Watts}$
 $E_1 = 60.8 \text{ volts}$
 $E_2 = 25.08 \text{ Volts}$
 $E_3 = 152 \text{ Volts}$

$P_3 =$
 $E_3 = 152 \text{ Volts}$
 $I_3 =$
 $R_3 =$

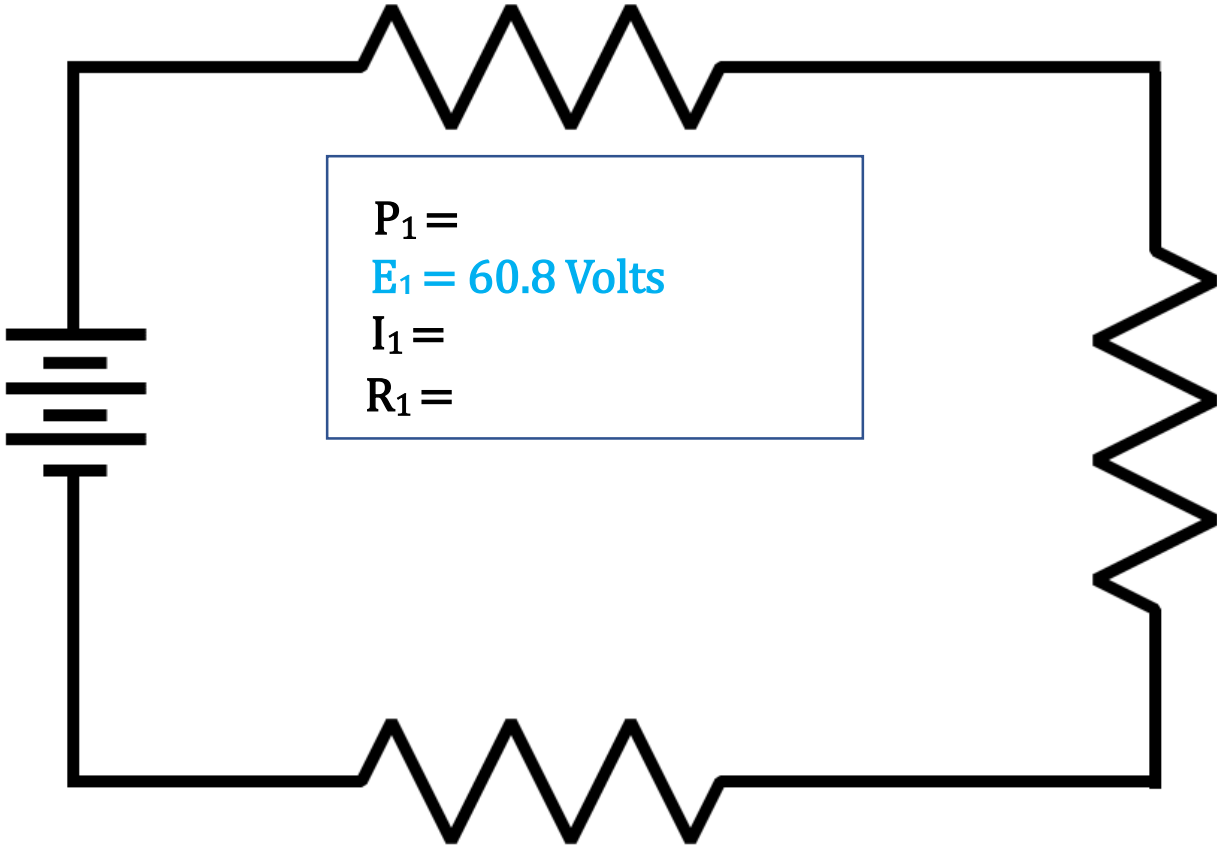$P_T = 903.94$ Watts
 $E_T = 237.88$ Volts
 $I_T =$
 $R_T =$




$P_1 =$
 $E_1 = 60.8$ Volts
 $I_1 =$
 $R_1 =$

$P_2 =$
 $E_2 = 25.08$ Volts
 $I_2 =$
 $R_2 =$

$P_T = 903.94$ Watts
 $E_1 = 60.8$ volts
 $E_2 = 25.08$ Volts
 $E_3 = 152$ Volts

$P_3 =$
 $E_3 = 152$ Volts
 $I_3 =$
 $R_3 =$

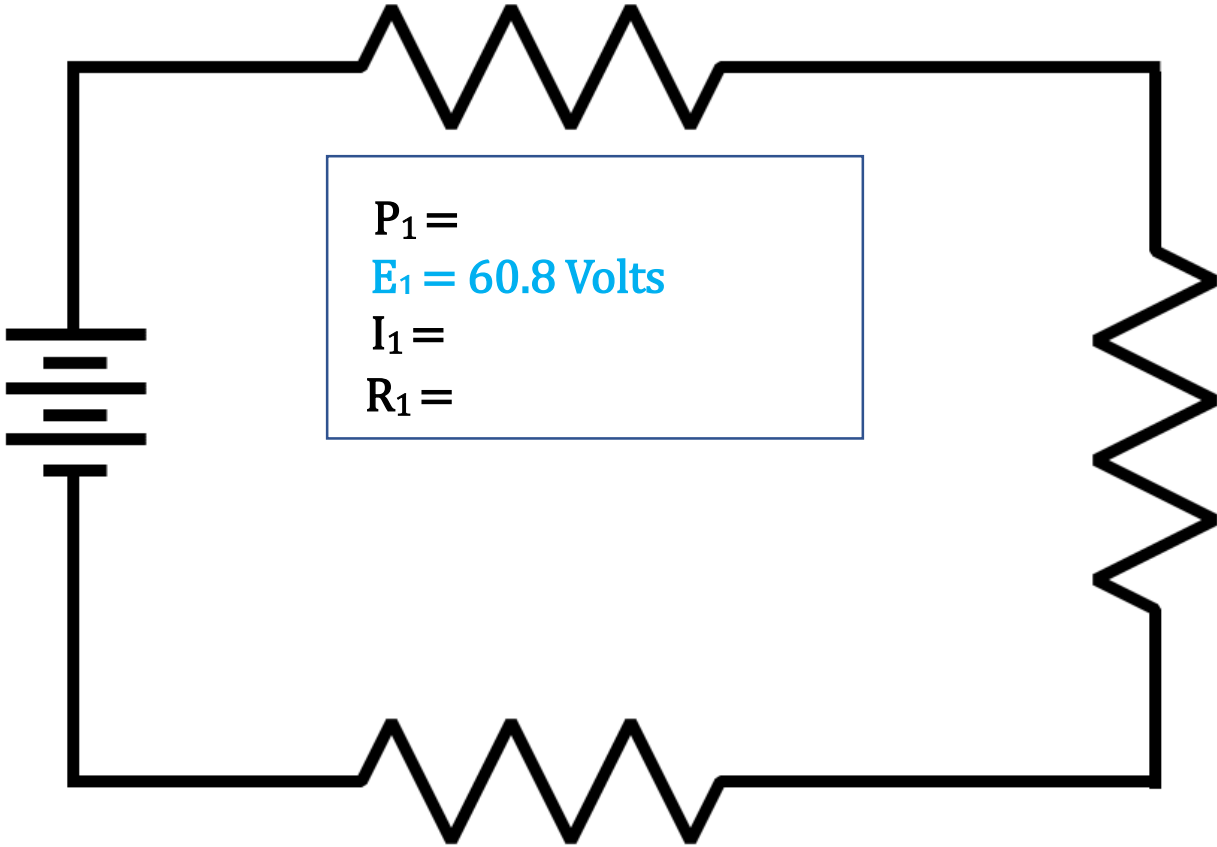$P_T = 903.94$ Watts
 $E_T = 237.88$ Volts
 $I_T = 3.8$ Amps
 $R_T = 62.6$ Ohms




$P_2 =$
 $E_2 = 25.08$ Volts
 $I_2 =$
 $R_2 =$

$P_T = 903.94$ Watts
 $E_1 = 60.8$ volts
 $E_2 = 25.08$ Volts
 $E_3 = 152$ Volts

$P_3 =$
 $E_3 = 152$ Volts
 $I_3 =$
 $R_3 =$

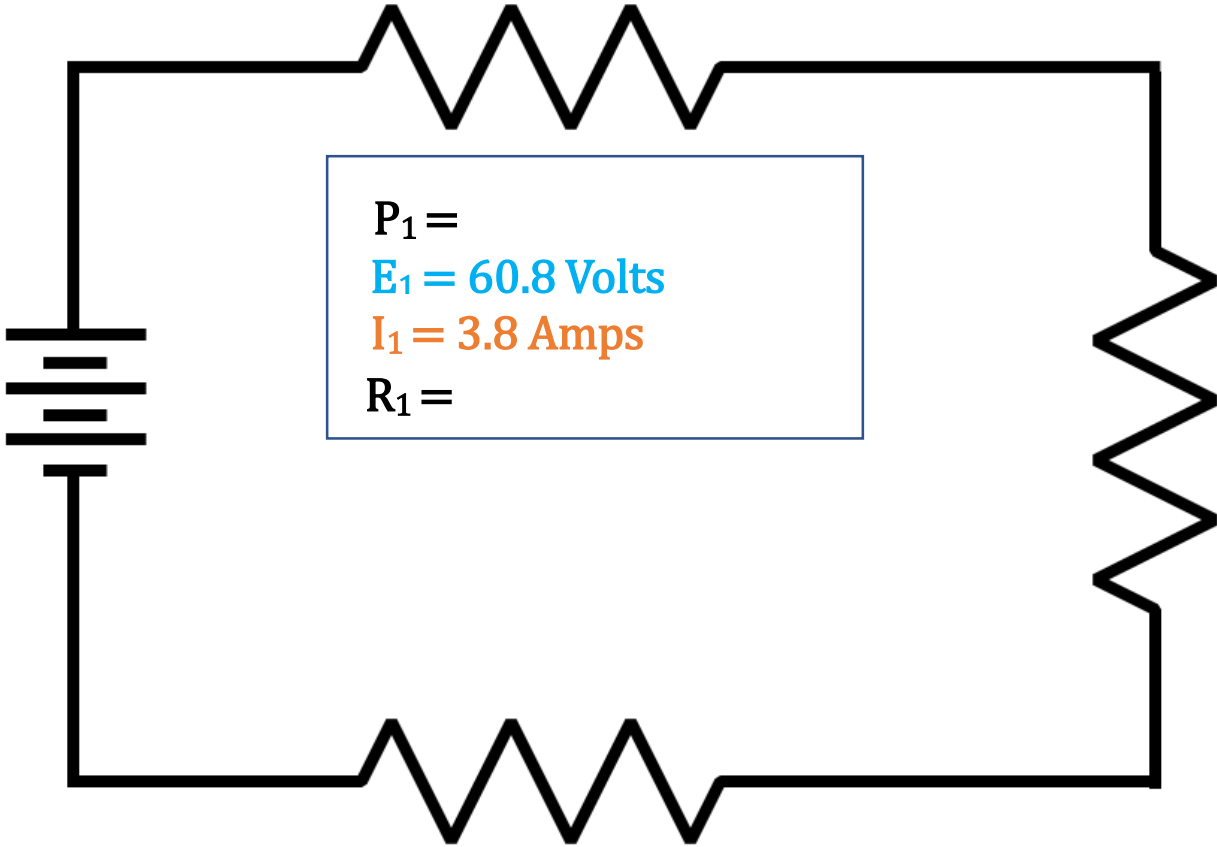$P_T = 903.94$ Watts
 $E_T = 237.88$ Volts
 $I_T = 3.8$ Amps
 $R_T = 62.6$ Ohms




$P_1 =$
 $E_1 = 60.8$ Volts
 $I_1 = 3.8$ Amps
 $R_1 =$

$P_2 =$
 $E_2 = 25.08$ Volts
 $I_2 = 3.8$ Amps
 $R_2 =$

$P_3 =$
 $E_3 = 152$ Volts
 $I_3 = 3.8$ Amps
 $R_3 =$

$P_T = 903.94$ Watts
 $E_1 = 60.8$ volts
 $E_2 = 25.08$ Volts
 $E_3 = 152$ Volts

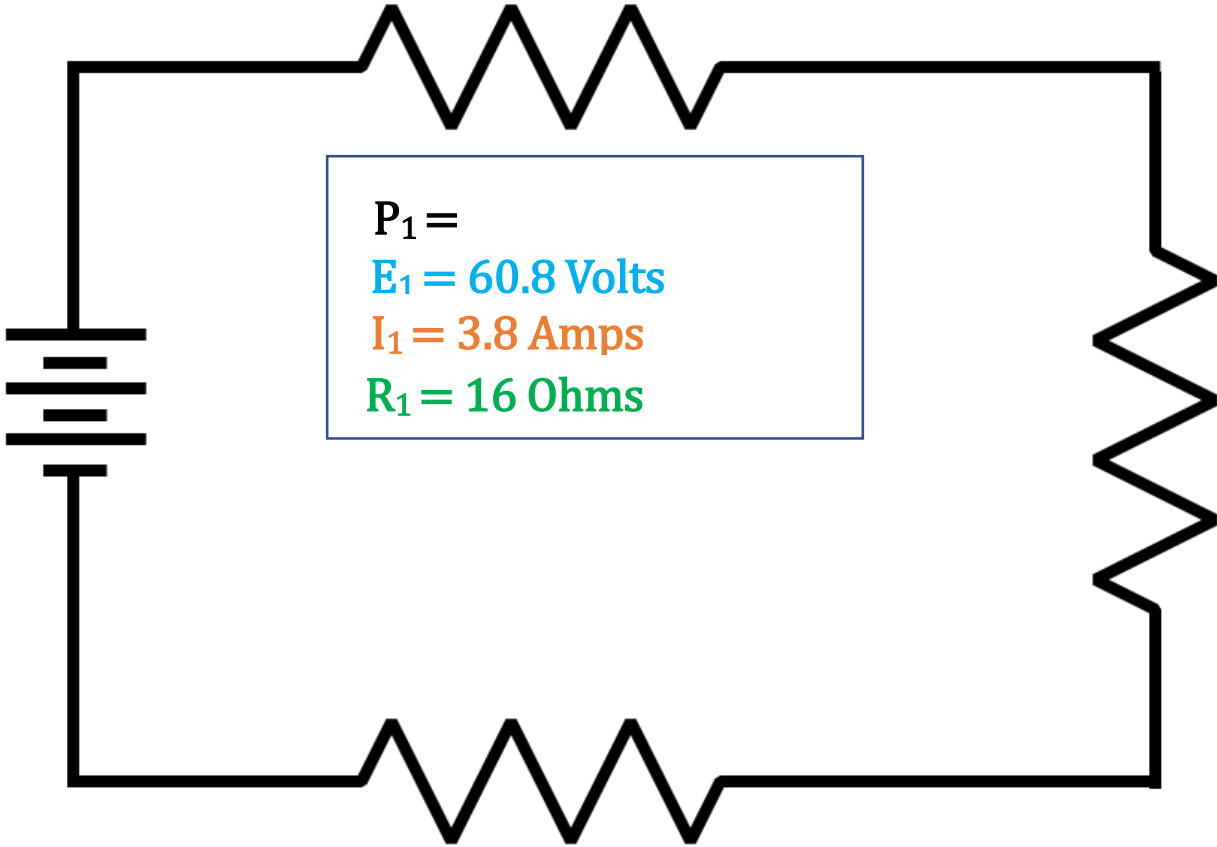$P_T = 903.94$ Watts
 $E_T = 237.88$ Volts
 $I_T = 3.8$ Amps
 $R_T = 62.6$ Ohms



$P_1 =$
 $E_1 = 60.8$ Volts
 $I_1 = 3.8$ Amps
 $R_1 = 16$ Ohms

$P_2 =$
 $E_2 = 25.08$ Volts
 $I_2 = 3.8$ Amps
 $R_2 = 6.6$ Ohms

$P_3 =$
 $E_3 = 152$ Volts
 $I_3 = 3.8$ Amps
 $R_3 = 40$ Ohms

$P_T = 903.94$ Watts
 $E_1 = 60.8$ volts
 $E_2 = 25.08$ Volts
 $E_3 = 152$ Volts

