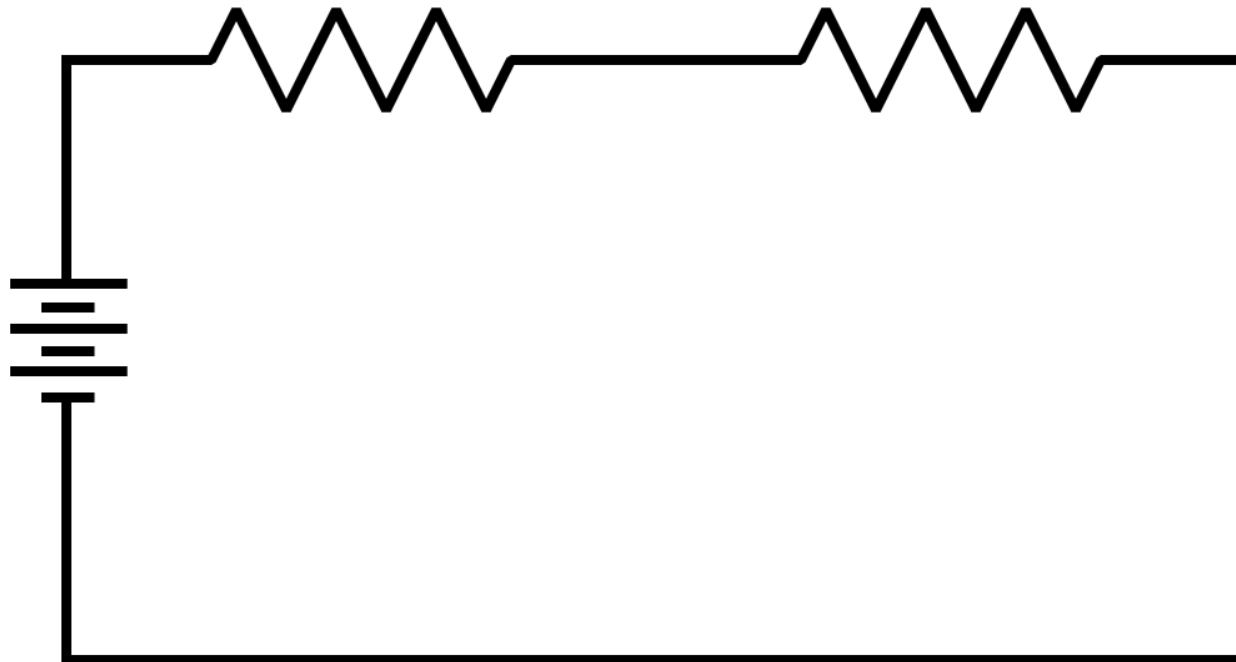


Series Circuit Math - Example 5

Series Example 5



$$I_T = 1.25 \text{ Amps}$$

$$R_T = 96 \text{ Ohms}$$

$$R_1 = 3.68 \text{ Ohms}$$


Find All Values of E, I and R using Ohm's Law and Series Rules

Series Example 5

$P_1 =$
 $E_1 =$
 $I_1 =$
 $R_1 = 3.68 \text{ Ohms}$

$P_2 =$
 $E_2 =$
 $I_2 =$
 $R_2 =$

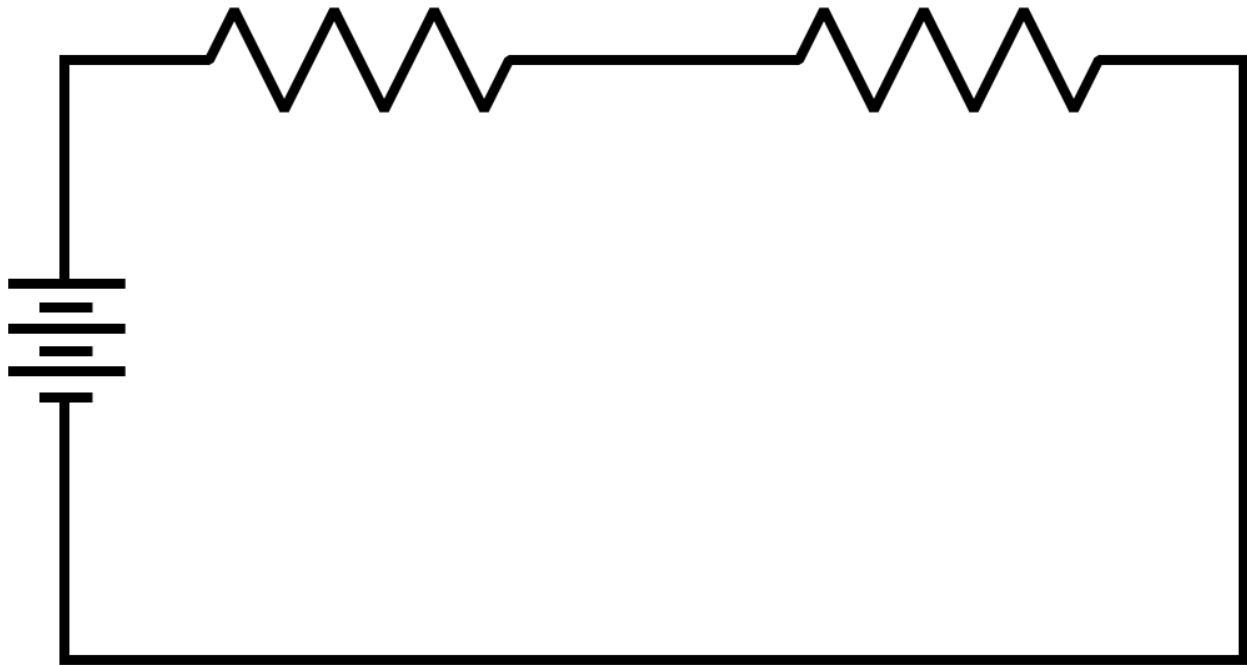$P_T =$
 $E_T =$
 $I_T = 1.25 \text{ Amps}$
 $R_T = 96 \text{ Ohms}$



$I_T = 1.25 \text{ Amps}$

$R_T = 96 \text{ Ohms}$

$R_1 = 3.68 \text{ Ohms}$


Find All Values of E, I and R using Ohm's Law and Series Rules

Series Example 5

$P_1 =$
 $E_1 =$
 $I_1 =$
 $R_1 = 3.68 \text{ Ohms}$

$P_2 =$
 $E_2 =$
 $I_2 =$
 $R_2 =$

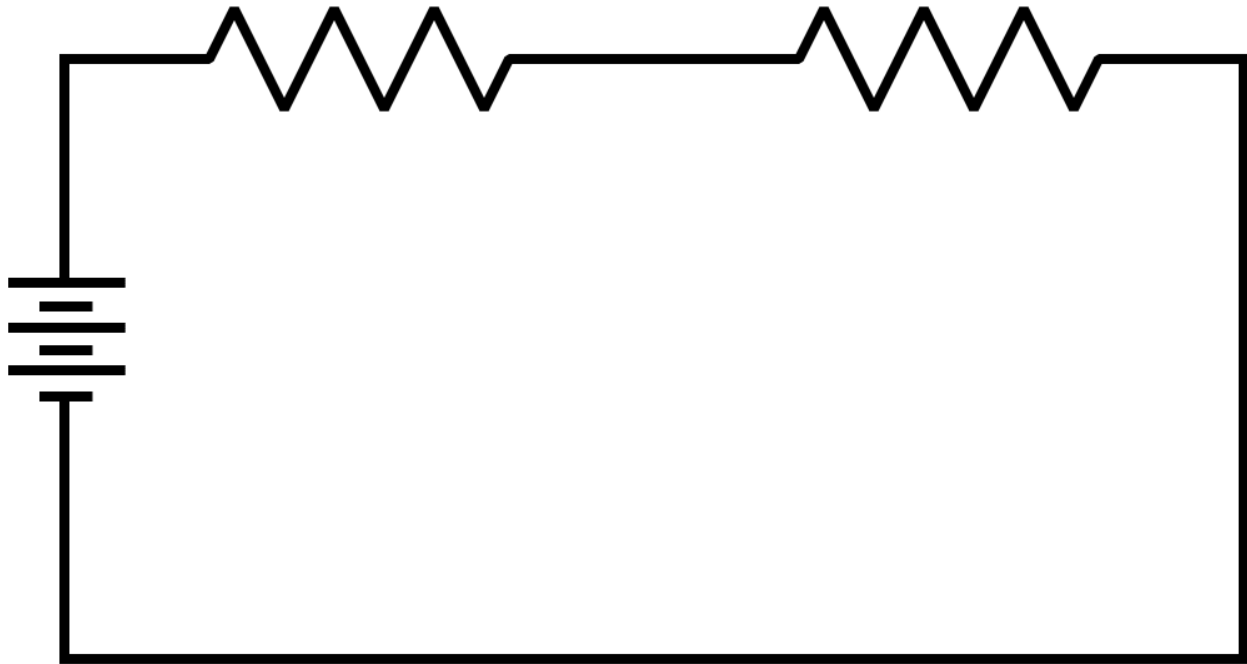$P_T = 150 \text{ Watts}$
 $E_T = 120 \text{ Volts}$
 $I_T = 1.25 \text{ Amps}$
 $R_T = 96 \text{ Ohms}$



$I_T = 1.25 \text{ Amps}$

$R_T = 96 \text{ Ohms}$

$R_1 = 3.68 \text{ Ohms}$

Find All Values of E, I and R using Ohm's Law and Series Rules

Series Example 5

$P_1 =$

$E_1 =$

$I_1 = 1.25 \text{ Amps}$

$R_1 = 3.68 \text{ Ohms}$

$P_2 =$

$E_2 =$

$I_2 = 1.25 \text{ Amps}$


$R_2 =$

$P_T = 150 \text{ Watts}$

$E_T = 120 \text{ Volts}$

$I_T = 1.25 \text{ Amps}$

$R_T = 96 \text{ Ohms}$

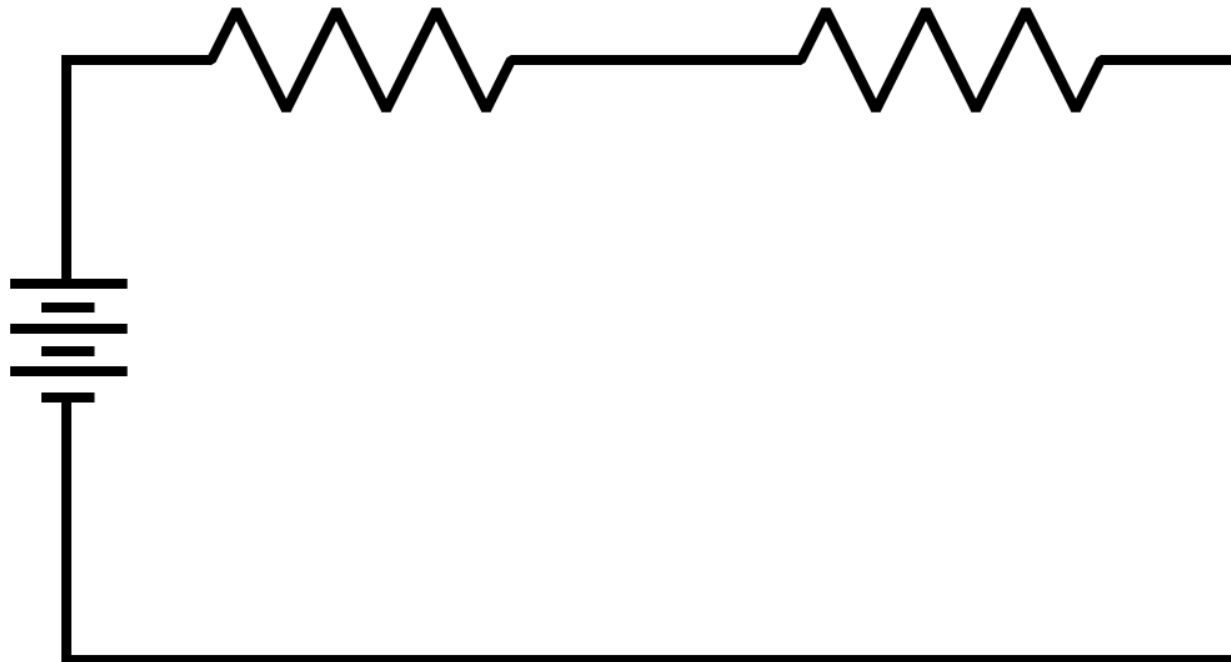

$I_T = 1.25 \text{ Amps}$

$R_T = 96 \text{ Ohms}$

$R_1 = 3.68 \text{ Ohms}$

Find All Values of E, I and R using Ohm's Law and Series Rules

Series Example 5

$$P_1 = 5.75 \text{ Watts}$$

$$E_1 = 4.6 \text{ Volts}$$

$$I_1 = 1.25 \text{ Amps}$$

$$R_1 = 3.68 \text{ Ohms}$$

$$P_2 =$$

$$E_2 =$$

$$I_2 = 1.25 \text{ Amps}$$


$$R_2 =$$

$$P_T = 150 \text{ Watts}$$

$$E_T = 120 \text{ Volts}$$

$$I_T = 1.25 \text{ Amps}$$

$$R_T = 96 \text{ Ohms}$$

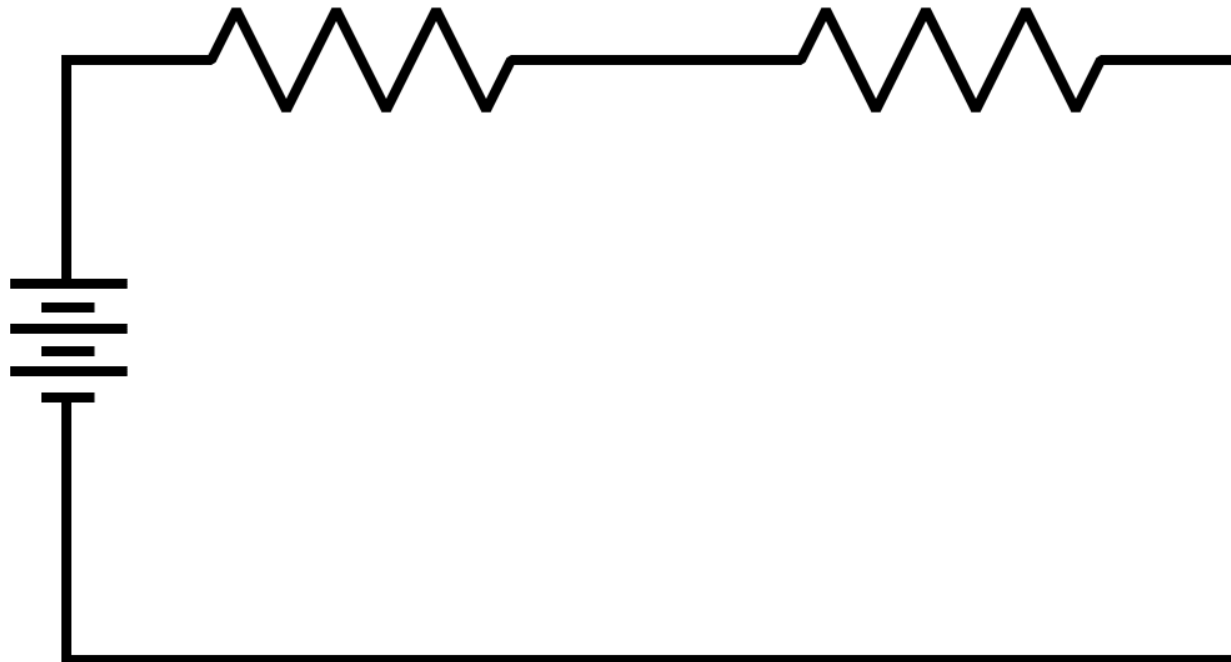

$$I_T = 1.25 \text{ Amps}$$

$$R_T = 96 \text{ Ohms}$$

$$R_1 = 3.68 \text{ Ohms}$$

Find All Values of E, I and R using Ohm's Law and Series Rules

Series Example 5

$$P_1 = 5.75 \text{ Watts}$$

$$E_1 = 4.6 \text{ Volts}$$

$$I_1 = 1.25 \text{ Amps}$$

$$R_1 = 3.68 \text{ Ohms}$$

$$P_2 =$$

$$E_2 =$$

$$I_2 = 1.25 \text{ Amps}$$


$$R_2 = 92.32 \text{ Ohms}$$

$$P_T = 150 \text{ Watts}$$

$$E_T = 120 \text{ Volts}$$

$$I_T = 1.25 \text{ Amps}$$

$$R_T = 96 \text{ Ohms}$$

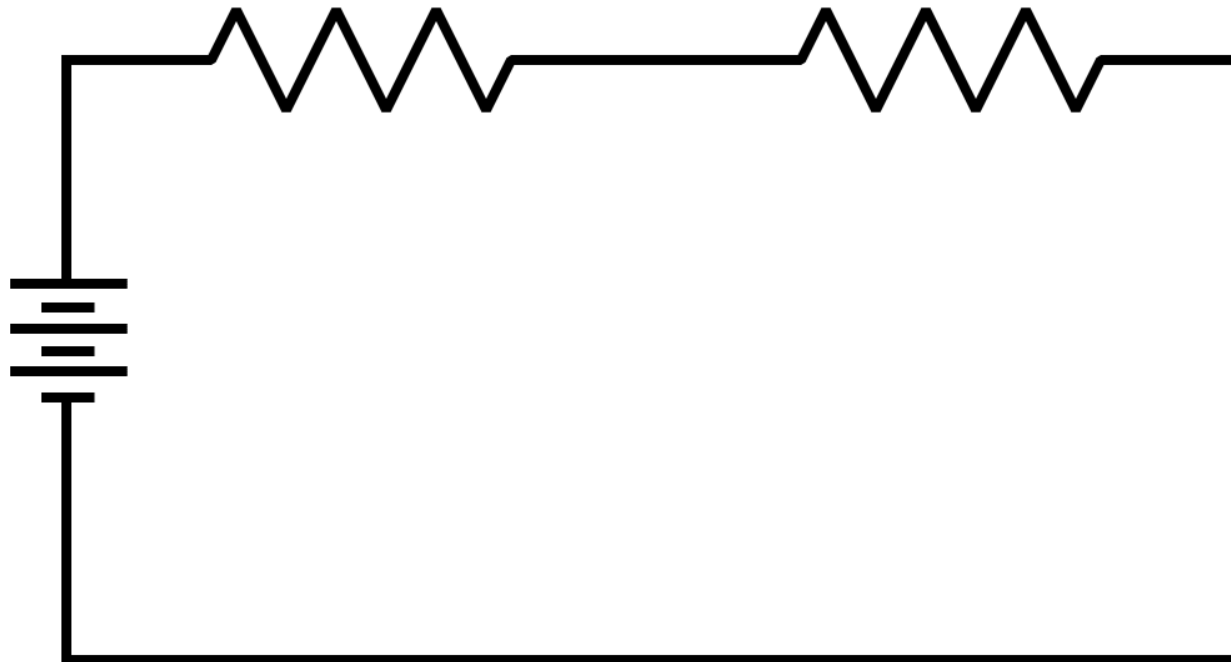

$$I_T = 1.25 \text{ Amps}$$

$$R_T = 96 \text{ Ohms}$$

$$R_1 = 3.68 \text{ Ohms}$$

Find All Values of E, I and R using Ohm's Law and Series Rules

Series Example 5

$$P_1 = 5.75 \text{ Watts}$$

$$E_1 = 4.6 \text{ Volts}$$

$$I_1 = 1.25 \text{ Amps}$$

$$R_1 = 3.68 \text{ Ohms}$$

$$P_2 = 144.25 \text{ Watts}$$

$$E_2 = 115.4 \text{ Volts}$$

$$I_2 = 1.25 \text{ Amps}$$


$$R_2 = 92.32 \text{ Ohms}$$

$$P_T = 150 \text{ Watts}$$

$$E_T = 120 \text{ Volts}$$

$$I_T = 1.25 \text{ Amps}$$

$$R_T = 96 \text{ Ohms}$$

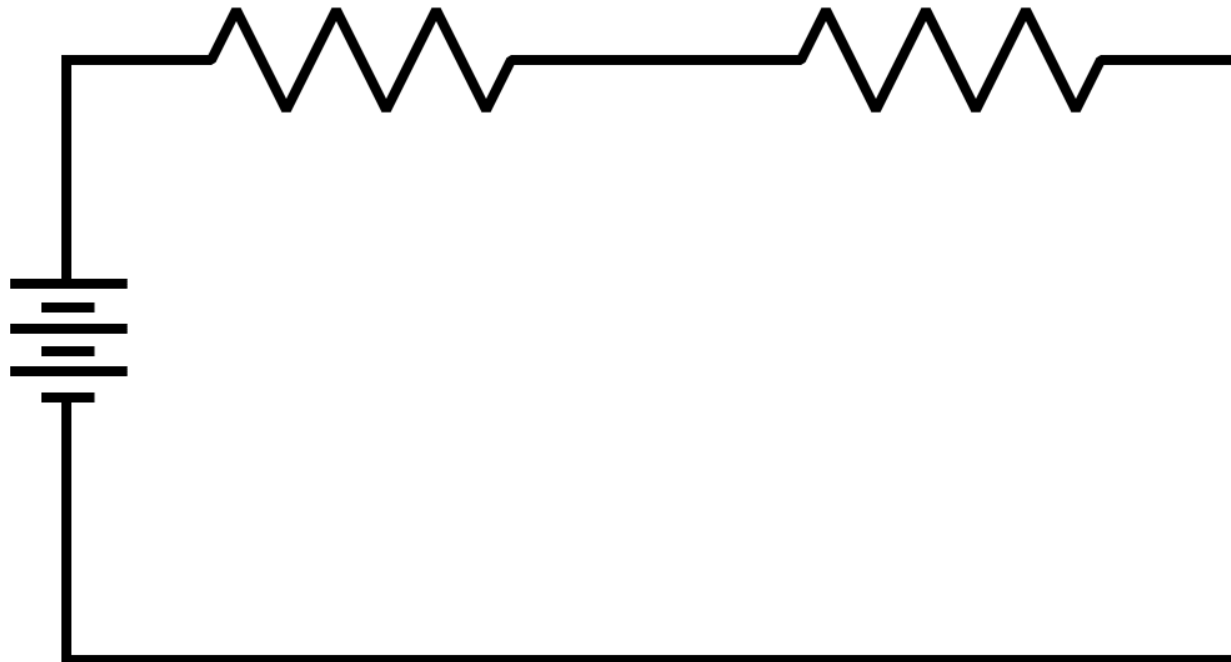

$$I_T = 1.25 \text{ Amps}$$

$$R_T = 96 \text{ Ohms}$$

$$R_1 = 3.68 \text{ Ohms}$$

Find All Values of E, I and R using Ohm's Law and Series Rules