

Series Circuit Math - Example 3

Series Example 3



$$E_2 = 24 \text{ Volts}$$

$$E_3 = 48 \text{ Volts}$$

$$R_3 = 16 \text{ Ohms}$$

$$R_T = 32 \text{ Ohms}$$

Find All Values of E, I and R using Ohm's Law and Series Rules

$E_1 =$

$I_1 =$

$R_1 =$

$E_2 = 24 \text{ Volts}$

$I_2 =$

$R_2 =$

$E_3 = 48 \text{ Volts}$

$I_3 =$

$R_3 = 16 \text{ Ohms}$

$E_T =$

$I_T =$

$R_T = 32 \text{ Ohms}$



$E_1 =$

$I_1 =$

$R_1 =$

$E_2 = 24 \text{ Volts}$

$I_2 =$

$R_2 =$

$E_3 = 48 \text{ Volts}$


$I_3 = 3 \text{ Amps}$

$R_3 = 16 \text{ Ohms}$

$E_T =$

$I_T =$

$R_T = 32 \text{ Ohms}$

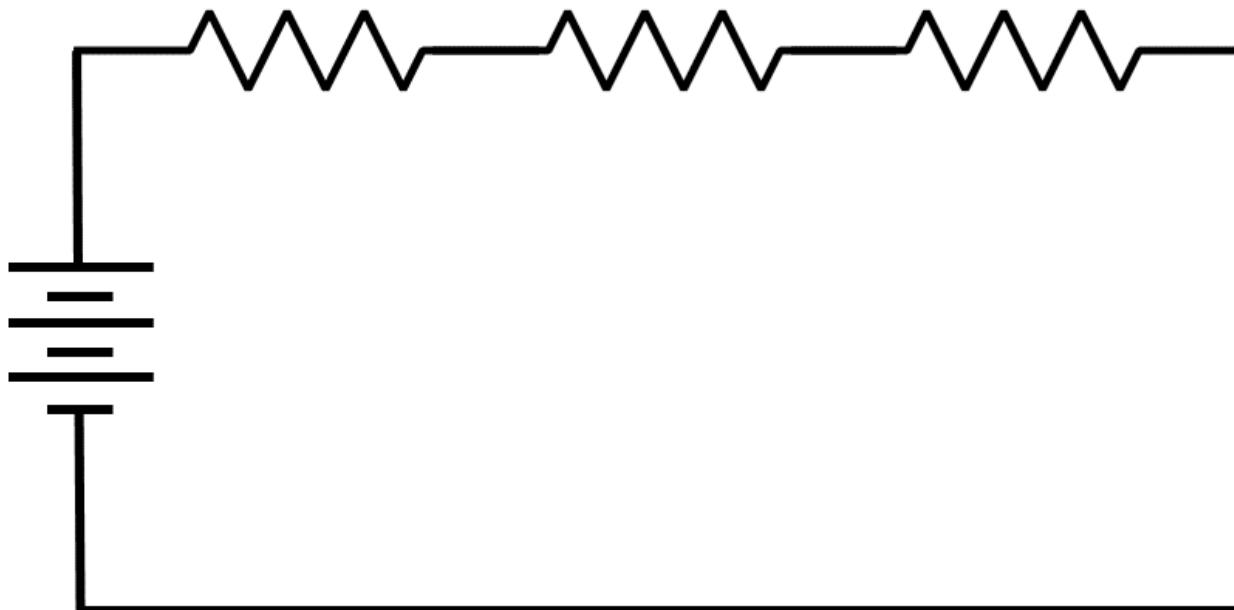

$$E_1 =$$

I₁ = 3 Amps

$$R_1 =$$

$$E_2 = 24 \text{ Volts}$$

I₂ = 3 Amps

$$R_2 =$$

$$E_3 = 48 \text{ Volts}$$

I₃ = 3 Amps

$$R_3 = 16 \text{ Ohms}$$

$$E_T =$$

I_T = 3 Amps

$$R_T = 32 \text{ Ohms}$$



$$E_1 =$$

$$I_1 = 3 \text{ Amps}$$

$$R_1 =$$

$$E_2 = 24 \text{ Volts}$$

$$I_2 = 3 \text{ Amps}$$

$$R_2 = 8 \text{ Ohms}$$

$$E_3 = 48 \text{ Volts}$$


$$I_3 = 3 \text{ Amps}$$

$$R_3 = 16 \text{ Ohms}$$

$$E_T = 96 \text{ Volts}$$

$$I_T = 3 \text{ Amps}$$

$$R_T = 32 \text{ Ohms}$$

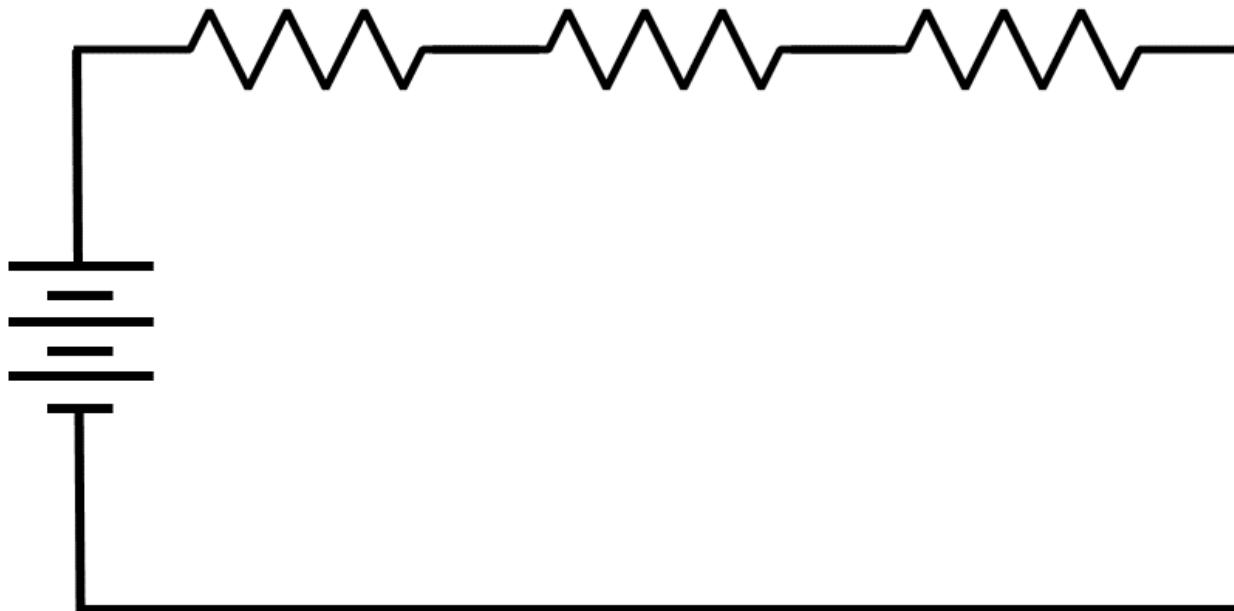

$$E_1 =$$

$$I_1 = 3 \text{ Amps}$$

$$R_1 = 8 \text{ Ohms}$$

$$E_2 = 24 \text{ Volts}$$

$$I_2 = 3 \text{ Amps}$$

$$R_2 = 8 \text{ Ohms}$$

$$E_3 = 48 \text{ Volts}$$


$$I_3 = 3 \text{ Amps}$$

$$R_3 = 16 \text{ Ohms}$$

$$E_T = 96 \text{ Volts}$$

$$I_T = 3 \text{ Amps}$$

$$R_T = 32 \text{ Ohms}$$

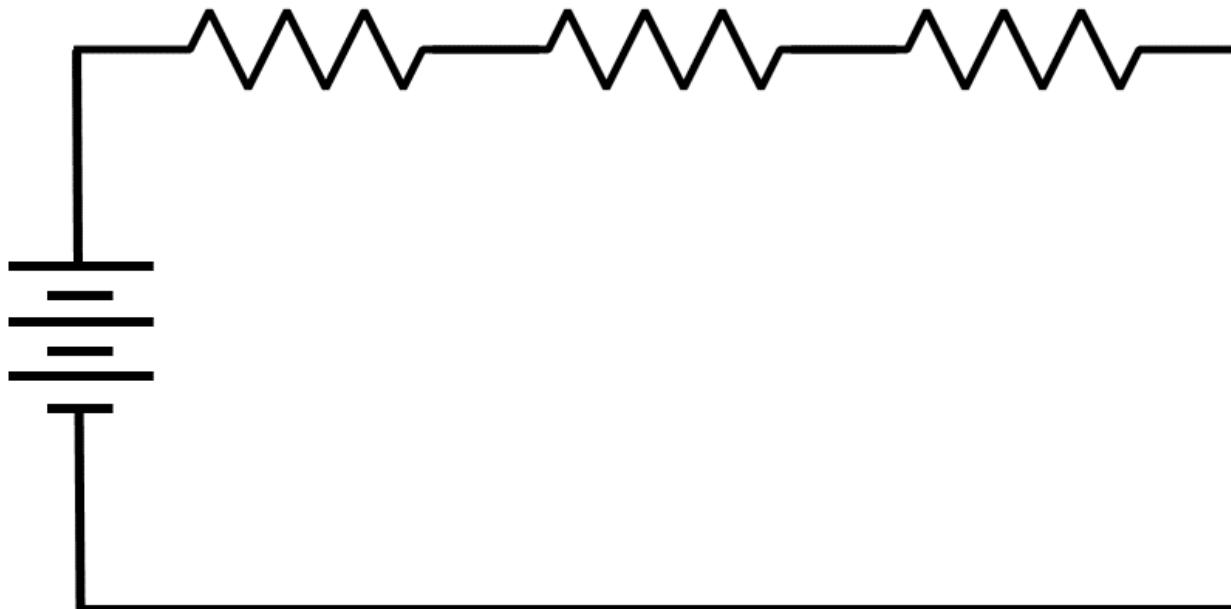

$E_1 = 24$ Volts

$I_1 = 3$ Amps

$R_1 = 8$ Ohms

$E_2 = 24$ Volts

$I_2 = 3$ Amps

$R_2 = 8$ Ohms

$E_3 = 48$ Volts

$I_3 = 3$ Amps

$R_3 = 16$ Ohms

$E_T = 96$ Volts

$I_T = 3$ Amps

$R_T = 32$ Ohms



