


Series Parallel Math Example 1

Math

Rule

$P_1 =$
 $E_1 =$
 $I_1 =$
 $R_1 = 4 \text{ Ohms}$

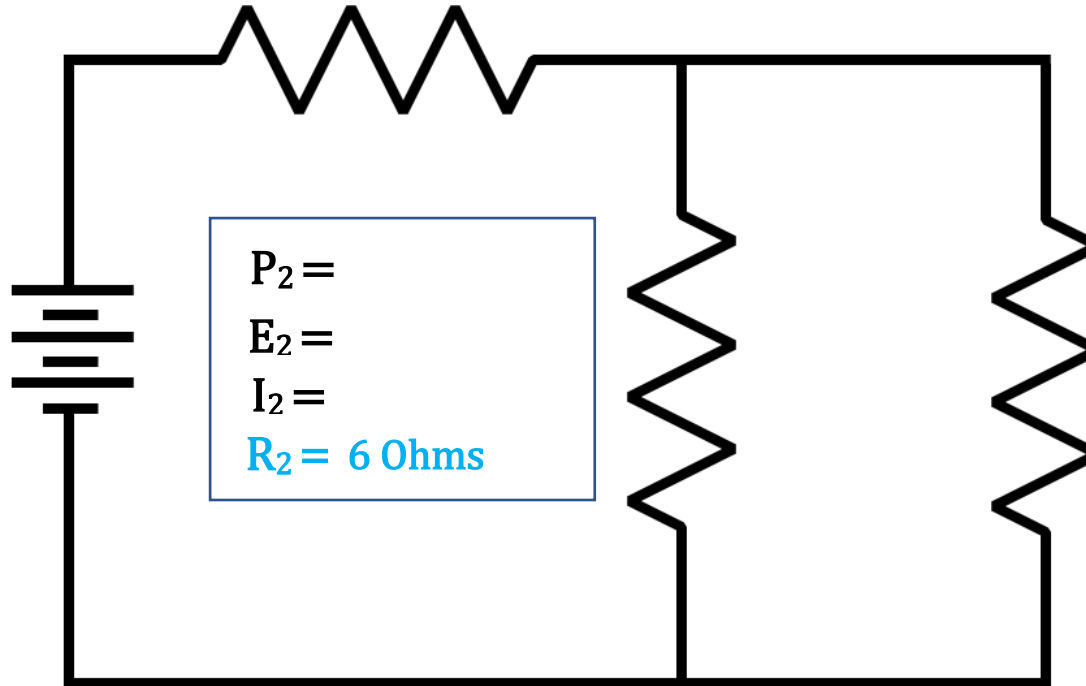$P_T =$
 $E_T = 12.6 \text{ Volts}$
 $I_T =$
 $R_T =$



$P_2 =$
 $E_2 =$
 $I_2 =$
 $R_2 = 6 \text{ Ohms}$


$P_3 =$
 $E_3 =$
 $I_3 =$
 $R_3 = 9 \text{ Ohms}$

Math

Rule

$P_1 =$
 $E_1 =$
 $I_1 =$
 $R_1 = 4 \text{ Ohms}$

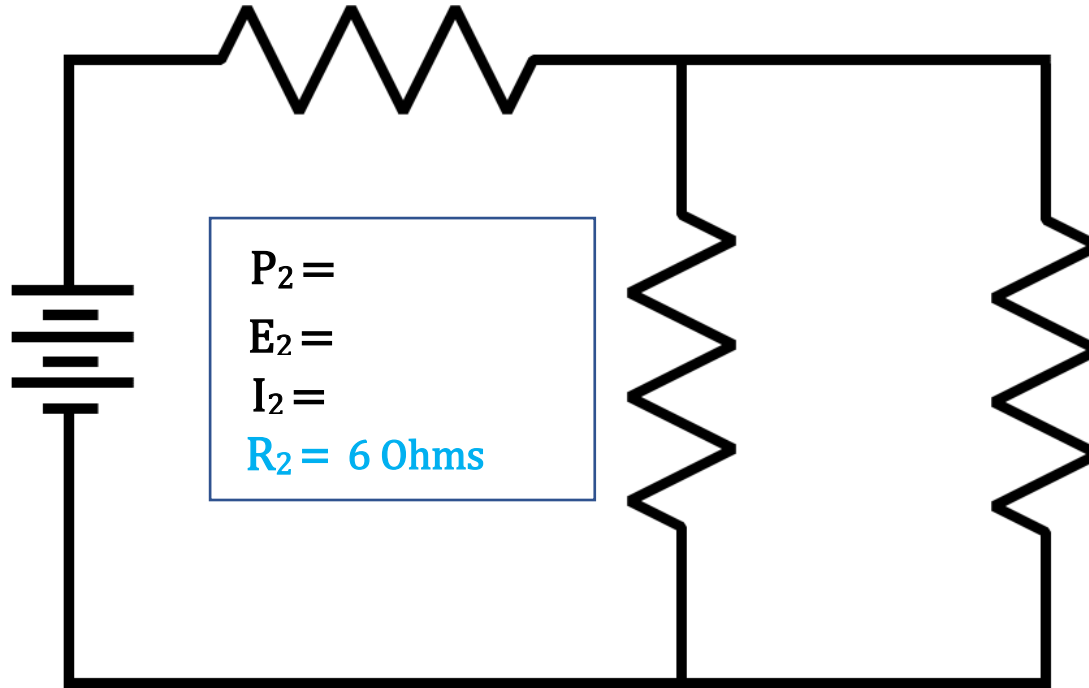$P_T =$
 $E_T = 12.6 \text{ Volts}$
 $I_T =$
 $R_T =$



$P_2 =$
 $E_2 =$
 $I_2 =$
 $R_2 = 6 \text{ Ohms}$

$P_3 =$
 $E_3 =$
 $I_3 =$
 $R_3 = 9 \text{ Ohms}$


$$R_{2,3} = \frac{R_2 \times R_3}{R_2 + R_3} \quad R_{2,3} = \frac{6 \times 9}{6 + 9} \quad R_{2,3} = \frac{54}{15} \quad R_{2,3} = 3.6 \text{ Ohms}$$

Math

Rule

$P_1 =$
 $E_1 =$
 $I_1 =$
 $R_1 = 4 \text{ Ohms}$

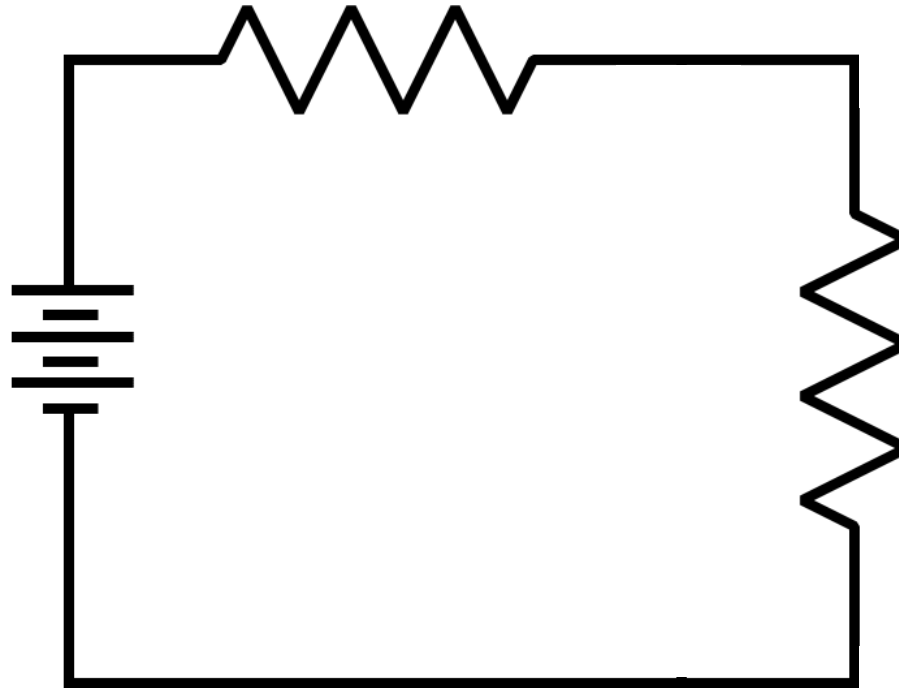$P_T =$
 $E_T = 12.6 \text{ Volts}$
 $I_T =$
 $R_T =$



$P_{2,3} =$
 $E_{2,3} =$
 $I_{2,3} =$
 $R_{2,3} = 3.6 \text{ Ohms}$


$$R_{2,3} = \frac{R_2 \times R_3}{R_2 + R_3} \quad R_{2,3} = \frac{6 \times 9}{6 + 9} \quad R_{2,3} = \frac{54}{15} \quad R_{2,3} = 3.6 \text{ Ohms}$$

Math

Rule

$P_1 =$
 $E_1 =$
 $I_1 =$
 $R_1 = 4 \text{ Ohms}$

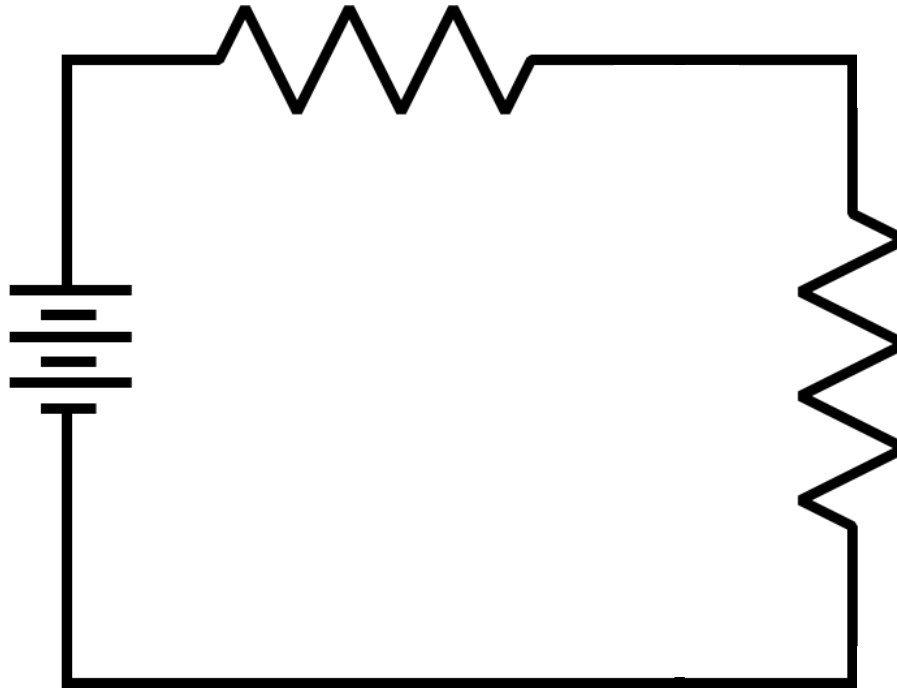$P_T =$
 $E_T = 12.6 \text{ Volts}$
 $I_T =$
 $R_T =$



$P_{2,3} =$
 $E_{2,3} =$
 $I_{2,3} =$
 $R_{2,3} = 3.6 \text{ Ohms}$

$$R_{2,3} = \frac{R_2 \times R_3}{R_2 + R_3} \quad R_{2,3} = \frac{6 \times 9}{6 + 9} \quad R_{2,3} = \frac{54}{15} \quad R_{2,3} = 3.6 \text{ Ohms}$$


$$R_T = R_1 + R_{2,3} = 4 + 3.6 = 7.6 \text{ Ohms}$$

Math

Rule

$P_1 =$
 $E_1 =$
 $I_1 =$
 $R_1 = 4 \text{ Ohms}$

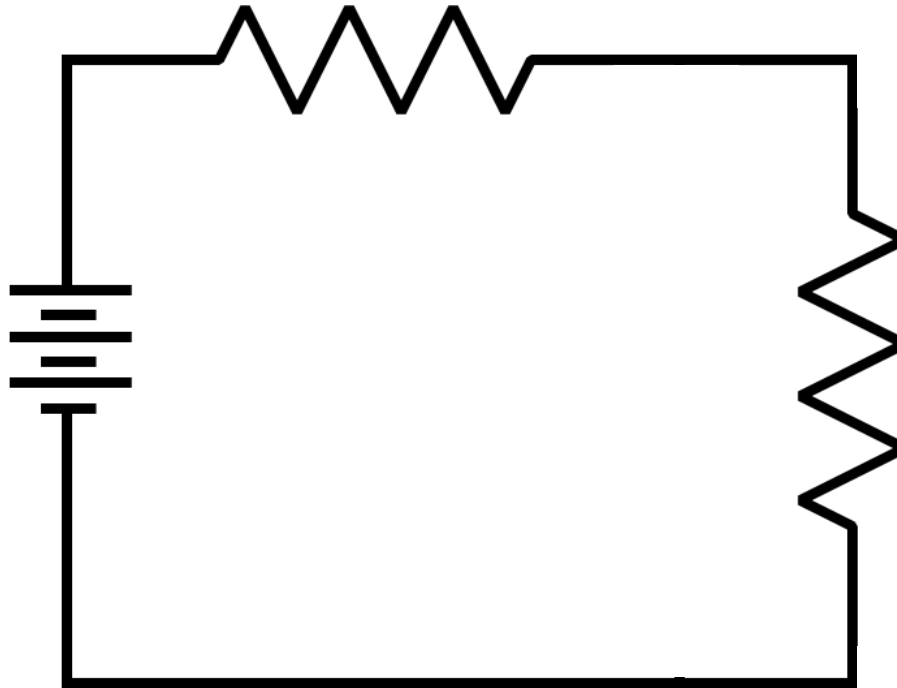$P_T =$
 $E_T = 12.6 \text{ Volts}$
 $I_T =$
 $R_T = 7.6 \text{ Ohms}$



$P_{2,3} =$
 $E_{2,3} =$
 $I_{2,3} =$
 $R_{2,3} = 3.6 \text{ Ohms}$

$$R_{2,3} = \frac{R_2 \times R_3}{R_2 + R_3} \quad R_{2,3} = \frac{6 \times 9}{6 + 9} \quad R_{2,3} = \frac{54}{15} \quad R_{2,3} = 3.6 \text{ Ohms}$$


$$R_T = R_1 + R_{2,3} = 4 + 3.6 = 7.6 \text{ Ohms}$$

Math

Rule

$P_1 =$
 $E_1 =$
 $I_1 =$
 $R_1 = 4 \text{ Ohms}$

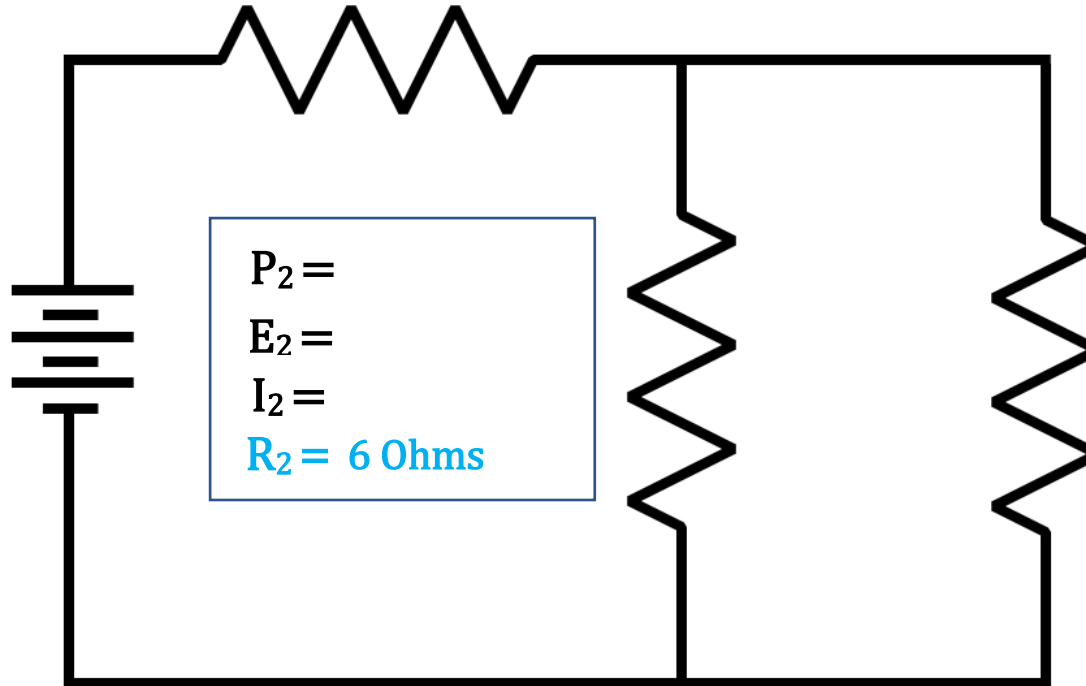$P_T =$
 $E_T = 12.6 \text{ Volts}$
 $I_T =$
 $R_T = 7.6 \text{ Ohms}$



$P_2 =$
 $E_2 =$
 $I_2 =$
 $R_2 = 6 \text{ Ohms}$


$P_3 =$
 $E_3 =$
 $I_3 =$
 $R_3 = 9 \text{ Ohms}$

Math

Rule

$P_1 =$
 $E_1 =$
 $I_1 =$
 $R_1 = 4 \text{ Ohms}$

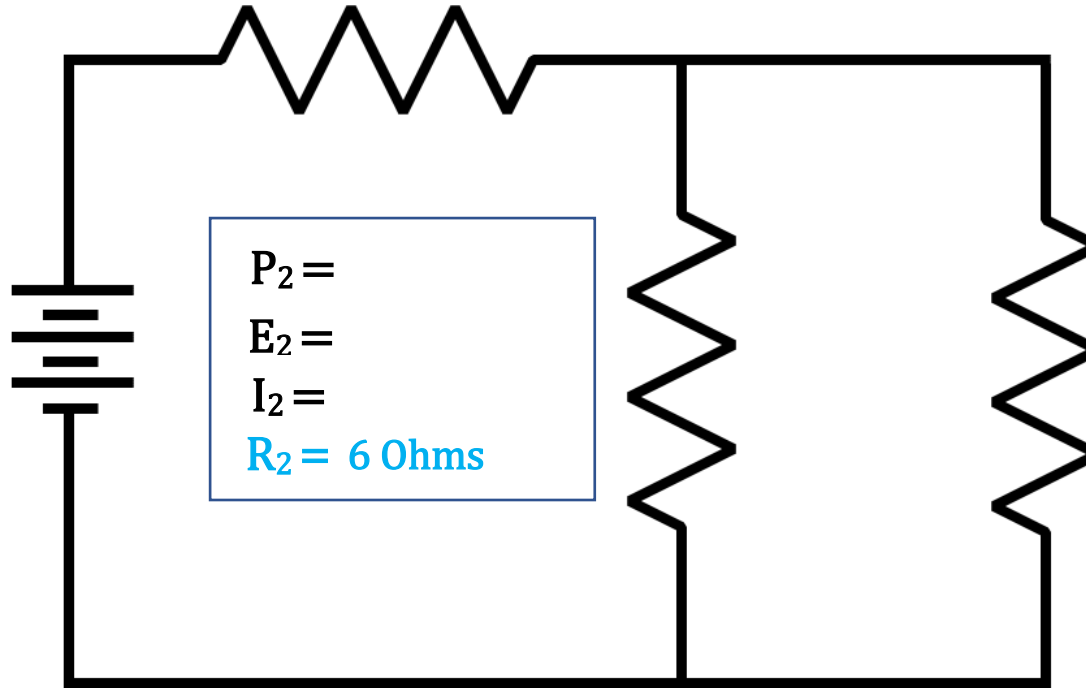$P_T = 20.92 \text{ Watts}$
 $E_T = 12.6 \text{ Volts}$
 $I_T = 1.66 \text{ Amps}$
 $R_T = 7.6 \text{ Ohms}$



$P_2 =$
 $E_2 =$
 $I_2 =$
 $R_2 = 6 \text{ Ohms}$


$P_3 =$
 $E_3 =$
 $I_3 =$
 $R_3 = 9 \text{ Ohms}$

Math

Rule

$P_1 =$
 $E_1 =$
 $I_1 = 1.66 \text{ Amps}$
 $R_1 = 4 \text{ Ohms}$

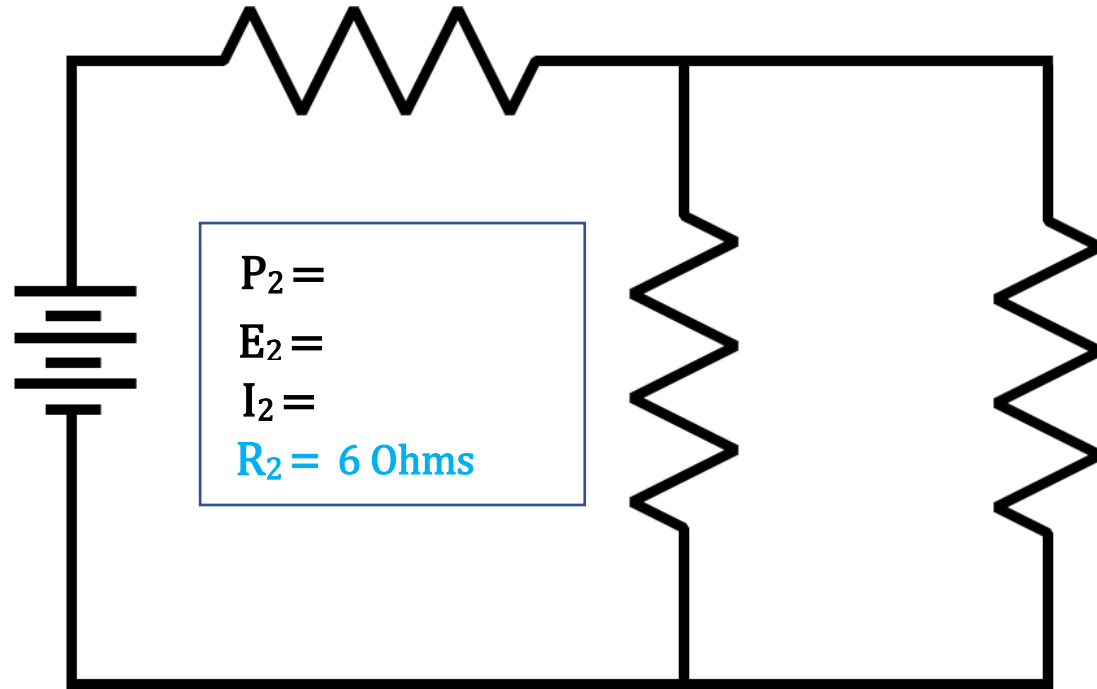$P_T = 20.92 \text{ Watts}$
 $E_T = 12.6 \text{ Volts}$
 $I_T = 1.66 \text{ Amps}$
 $R_T = 7.6 \text{ Ohms}$



$P_2 =$
 $E_2 =$
 $I_2 =$
 $R_2 = 6 \text{ Ohms}$


$P_3 =$
 $E_3 =$
 $I_3 =$
 $R_3 = 9 \text{ Ohms}$

Math

Rule

$P_1 = 11.02$ Watts
 $E_1 = 6.64$ Volts
 $I_1 = 1.66$ Amps
 $R_1 = 4$ Ohms

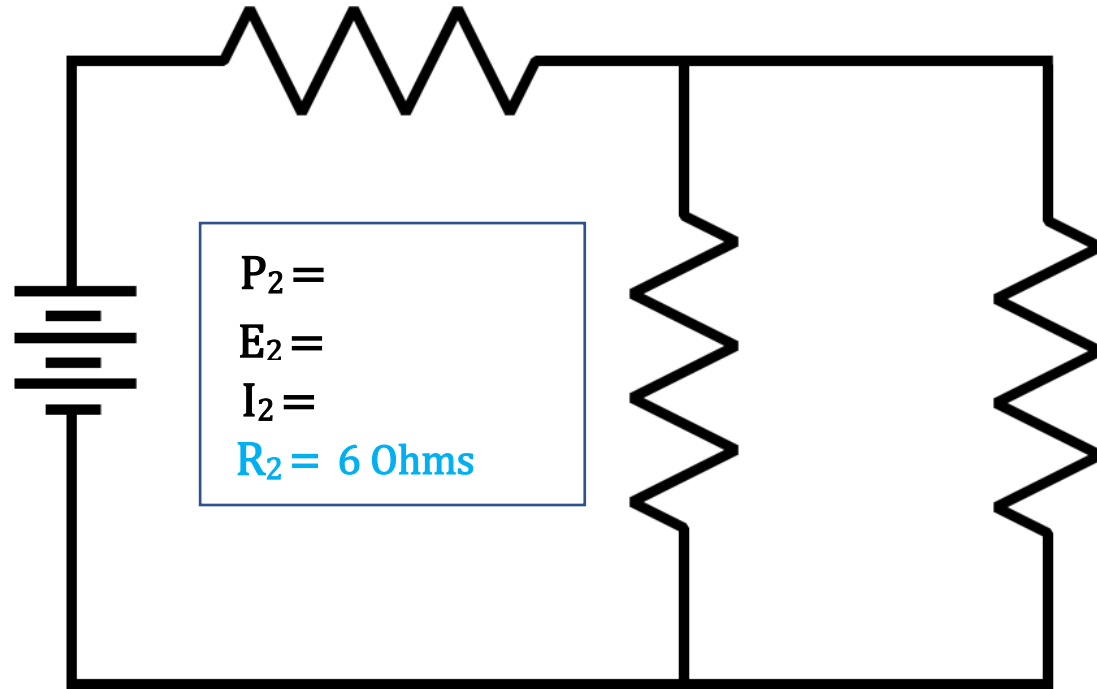$P_T = 20.92$ Watts
 $E_T = 12.6$ Volts
 $I_T = 1.66$ Amps
 $R_T = 7.6$ Ohms



$P_2 =$
 $E_2 =$
 $I_2 =$
 $R_2 = 6$ Ohms


$P_3 =$
 $E_3 =$
 $I_3 =$
 $R_3 = 9$ Ohms

Math

Rule

$P_1 = 11.02$ Watts
 $E_1 = 6.64$ Volts
 $I_1 = 1.66$ Amps
 $R_1 = 4$ Ohms

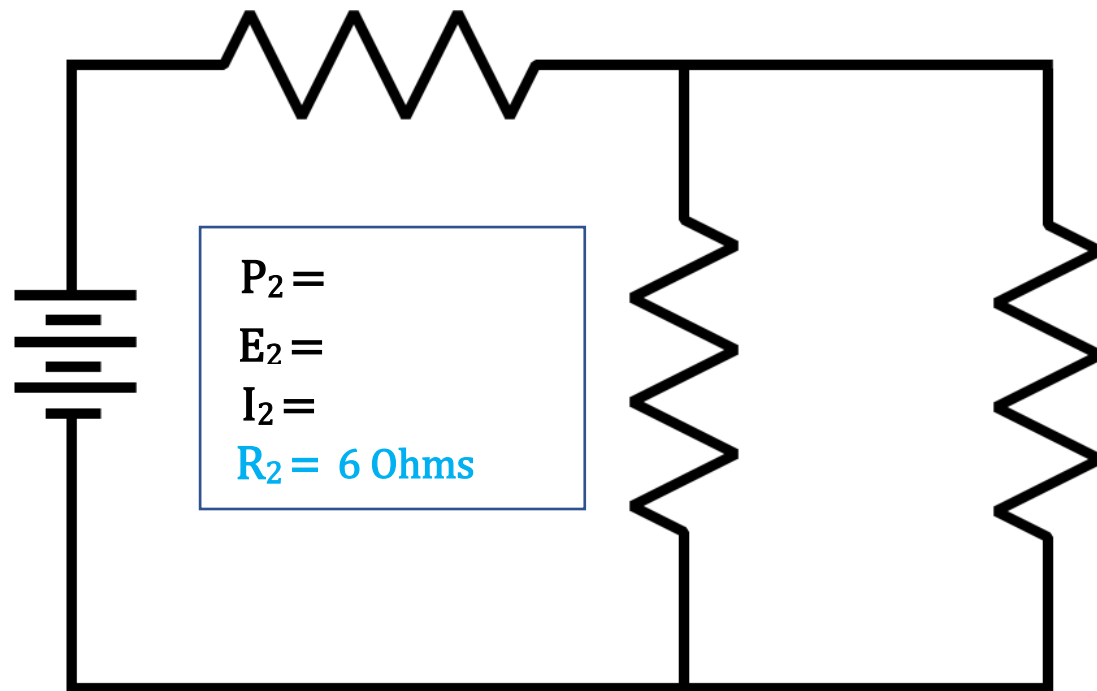$P_T = 20.92$ Watts
 $E_T = 12.6$ Volts
 $I_T = 1.66$ Amps
 $R_T = 7.6$ Ohms



$P_2 =$
 $E_2 =$
 $I_2 =$
 $R_2 = 6$ Ohms

$P_3 =$
 $E_3 =$
 $I_3 =$
 $R_3 = 9$ Ohms


$$E_{2,3} = E_T - E_1 = 12.6 - 6.64 = 5.96 \text{ Volts}$$

Math

Rule

$P_1 = 11.02$ Watts
 $E_1 = 6.64$ Volts
 $I_1 = 1.66$ Amps
 $R_1 = 4$ Ohms

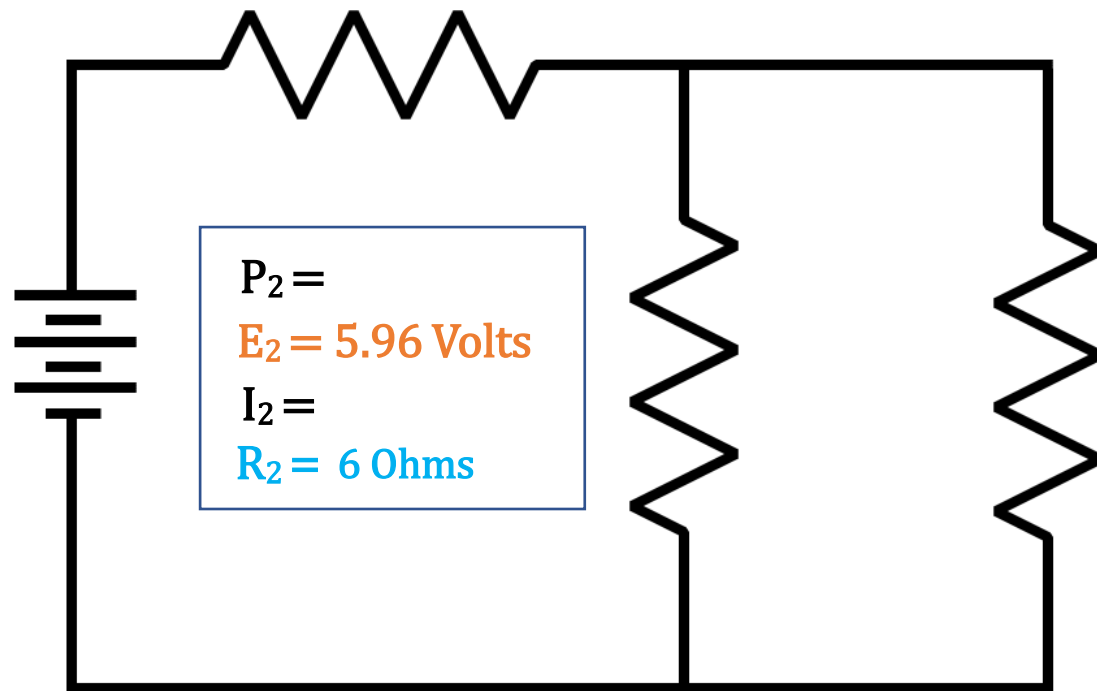$P_T = 20.92$ Watts
 $E_T = 12.6$ Volts
 $I_T = 1.66$ Amps
 $R_T = 7.6$ Ohms



$P_2 =$
 $E_2 = 5.96$ Volts
 $I_2 =$
 $R_2 = 6$ Ohms


$P_3 =$
 $E_3 = 5.96$ Volts
 $I_3 =$
 $R_3 = 9$ Ohms

$$E_{2,3} = E_T - E_1 = 12.6 - 6.64 = 5.96 \text{ Volts}$$

Math

Rule

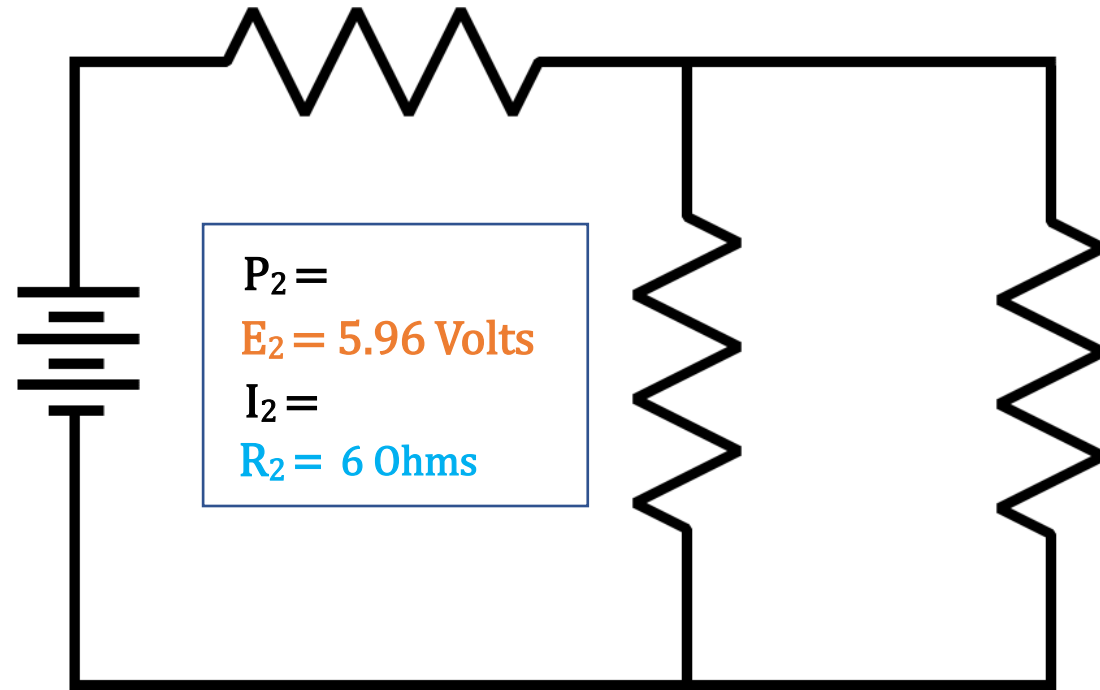$P_T = 20.92$ Watts
 $E_T = 12.6$ Volts
 $I_T = 1.66$ Amps
 $R_T = 7.6$ Ohms



$P_1 = 11.02$ Watts
 $E_1 = 6.64$ Volts
 $I_1 = 1.66$ Amps
 $R_1 = 4$ Ohms


$P_2 =$
 $E_2 = 5.96$ Volts
 $I_2 =$
 $R_2 = 6$ Ohms

$P_3 =$
 $E_3 = 5.96$ Volts
 $I_3 =$
 $R_3 = 9$ Ohms

Math

Rule

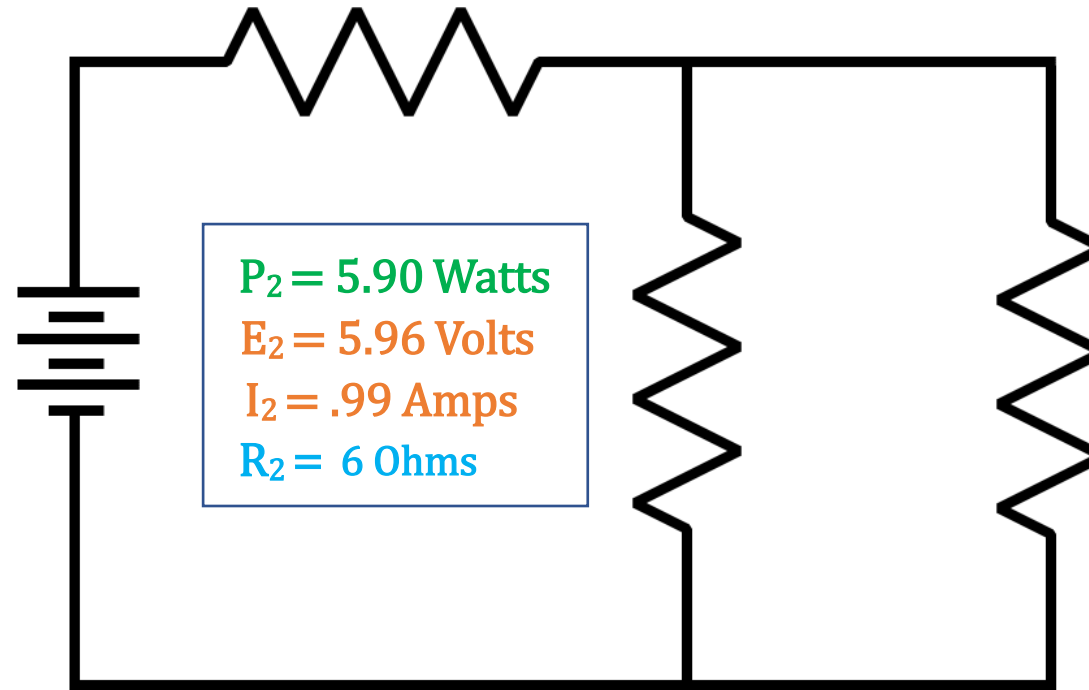$P_T = 20.92$ Watts
 $E_T = 12.6$ Volts
 $I_T = 1.66$ Amps
 $R_T = 7.6$ Ohms



$P_1 = 11.02$ Watts
 $E_1 = 6.64$ Volts
 $I_1 = 1.66$ Amps
 $R_1 = 4$ Ohms


$P_2 = 5.90$ Watts
 $E_2 = 5.96$ Volts
 $I_2 = .99$ Amps
 $R_2 = 6$ Ohms

$P_3 =$
 $E_3 = 5.96$ Volts
 $I_3 =$
 $R_3 = 9$ Ohms

Math

Rule

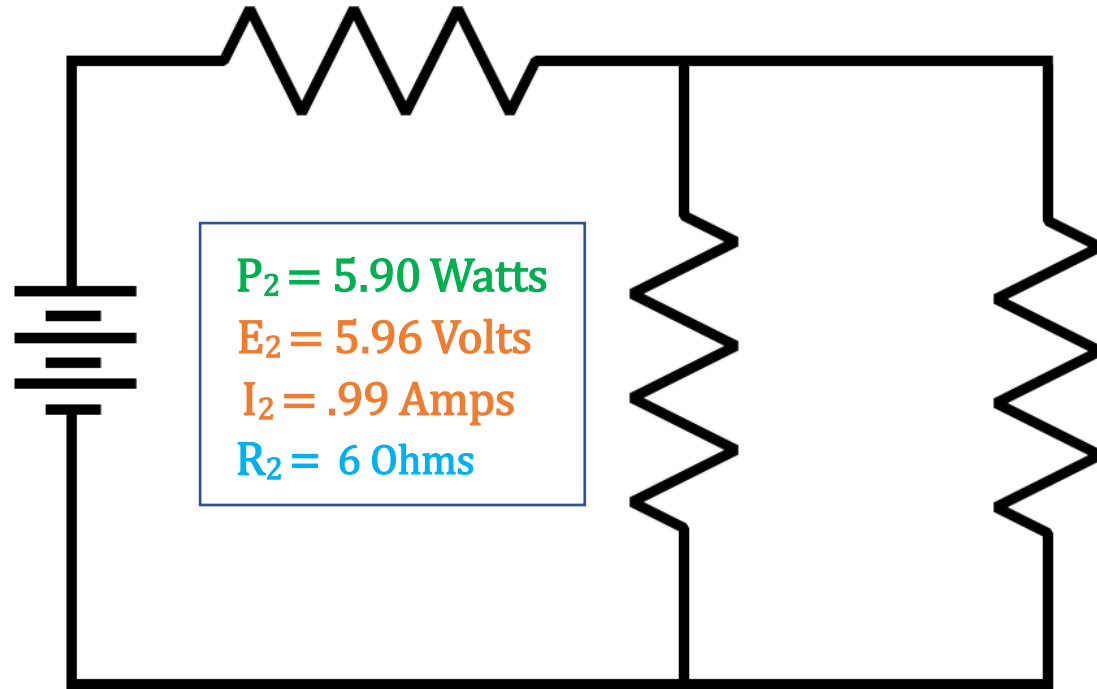$P_T = 20.92$ Watts
 $E_T = 12.6$ Volts
 $I_T = 1.66$ Amps
 $R_T = 7.6$ Ohms



$P_1 = 11.02$ Watts
 $E_1 = 6.64$ Volts
 $I_1 = 1.66$ Amps
 $R_1 = 4$ Ohms

$P_2 = 5.90$ Watts
 $E_2 = 5.96$ Volts
 $I_2 = .99$ Amps
 $R_2 = 6$ Ohms

$P_3 = 3.93$ Watts
 $E_3 = 5.96$ Volts
 $I_3 = .66$ Amps
 $R_3 = 9$ Ohms