

# Series Parallel Math Example 2

# Math


# Rule

$$\begin{aligned}P_1 = \\E_1 = \\I_1 &= \text{3.5 Amps} \\R_1 =\end{aligned}$$

$$\begin{aligned}P_T = \\E_T &= \text{28 Volts} \\I_T = \\R_T =\end{aligned}$$

$$\begin{aligned}P_2 = \\E_2 = \\I_2 = \\R_2 &= \text{18 Ohms}\end{aligned}$$
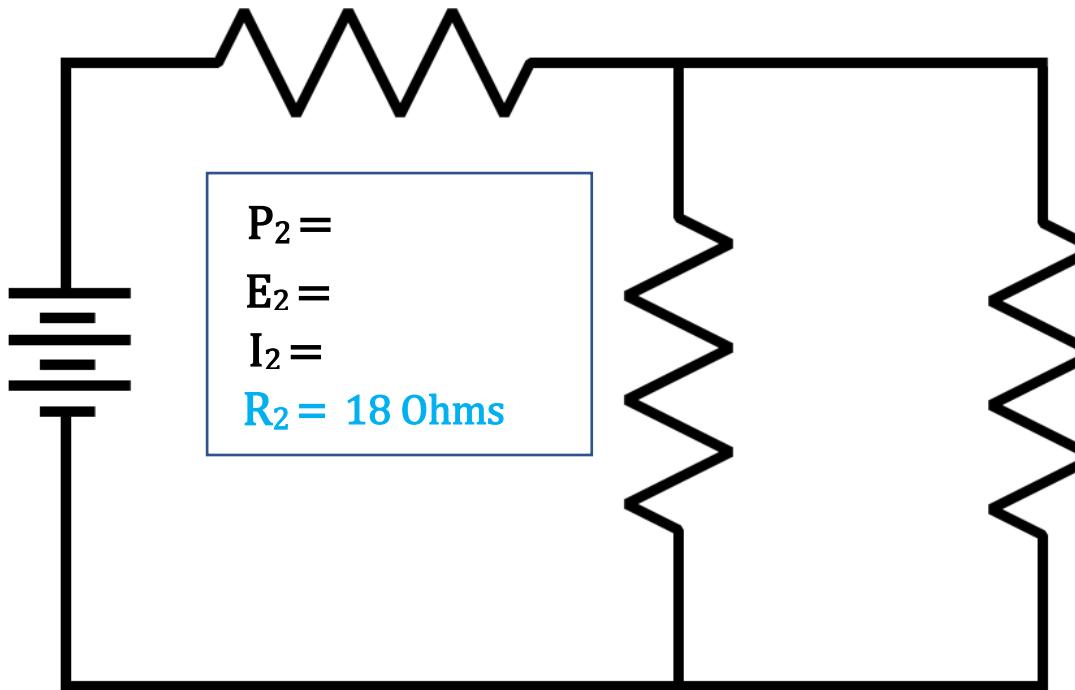
$$\begin{aligned}P_3 = \\E_3 = \\I_3 = \\R_3 &= \text{6.6 Ohms}\end{aligned}$$



# Math


# Rule

$$\begin{aligned}P_1 = \\E_1 = \\I_1 &= 3.5 \text{ Amps} \\R_1 =\end{aligned}$$

$$\begin{aligned}P_T = \\E_T &= 28 \text{ Volts} \\I_T &= 3.5 \text{ Amps} \\R_T =\end{aligned}$$

$$\begin{aligned}P_2 = \\E_2 = \\I_2 = \\R_2 &= 18 \text{ Ohms}\end{aligned}$$
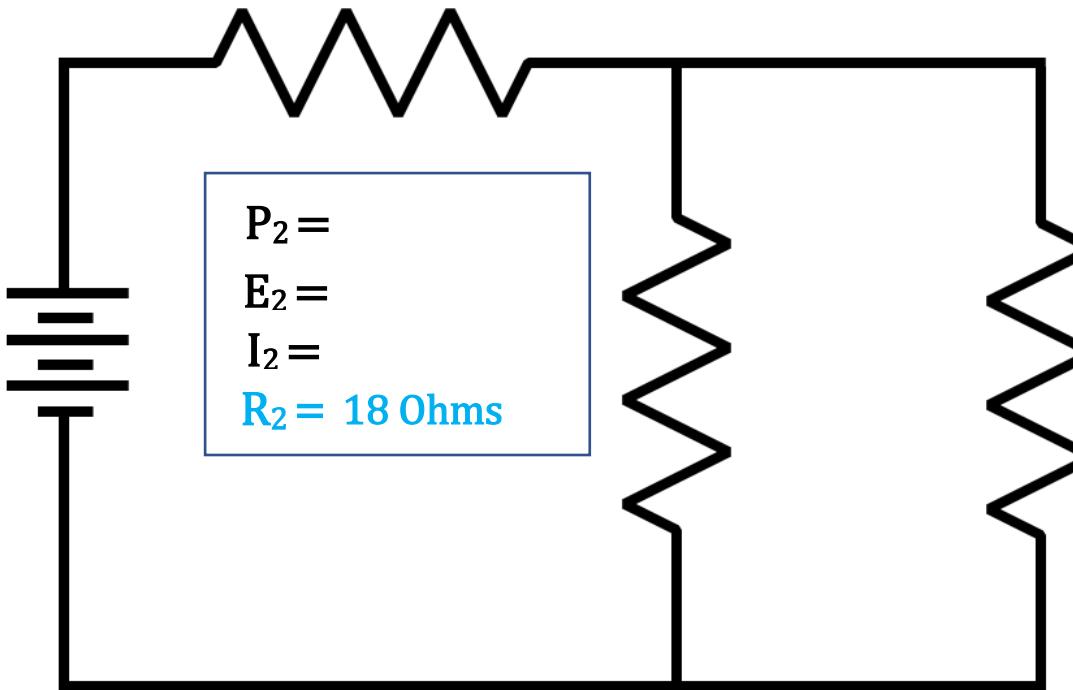
$$\begin{aligned}P_3 = \\E_3 = \\I_3 = \\R_3 &= 6.6 \text{ Ohms}\end{aligned}$$



# Math


# Rule

$$\begin{aligned}P_1 = \\E_1 = \\I_1 &= 3.5 \text{ Amps} \\R_1 =\end{aligned}$$

$$\begin{aligned}P_T &= 98 \text{ Watts} \\E_T &= 28 \text{ Volts} \\I_T &= 3.5 \text{ Amps} \\R_T &= 8 \text{ Ohms}\end{aligned}$$

$$\begin{aligned}P_2 = \\E_2 = \\I_2 = \\R_2 &= 18 \text{ Ohms}\end{aligned}$$
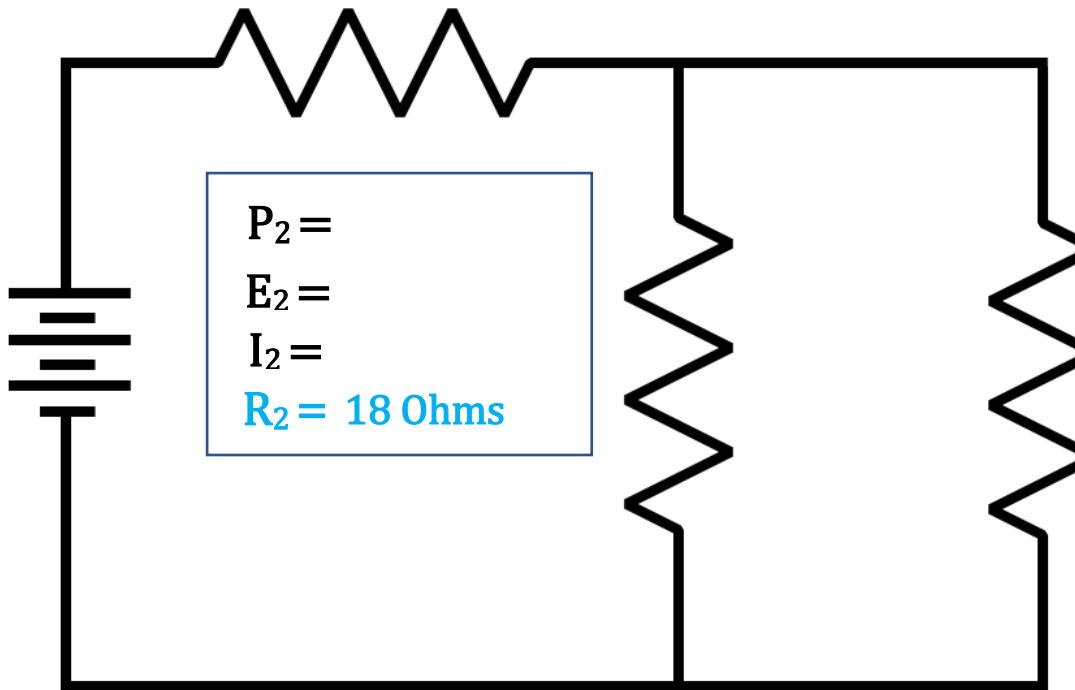
$$\begin{aligned}P_3 = \\E_3 = \\I_3 = \\R_3 &= 6.6 \text{ Ohms}\end{aligned}$$




# Math
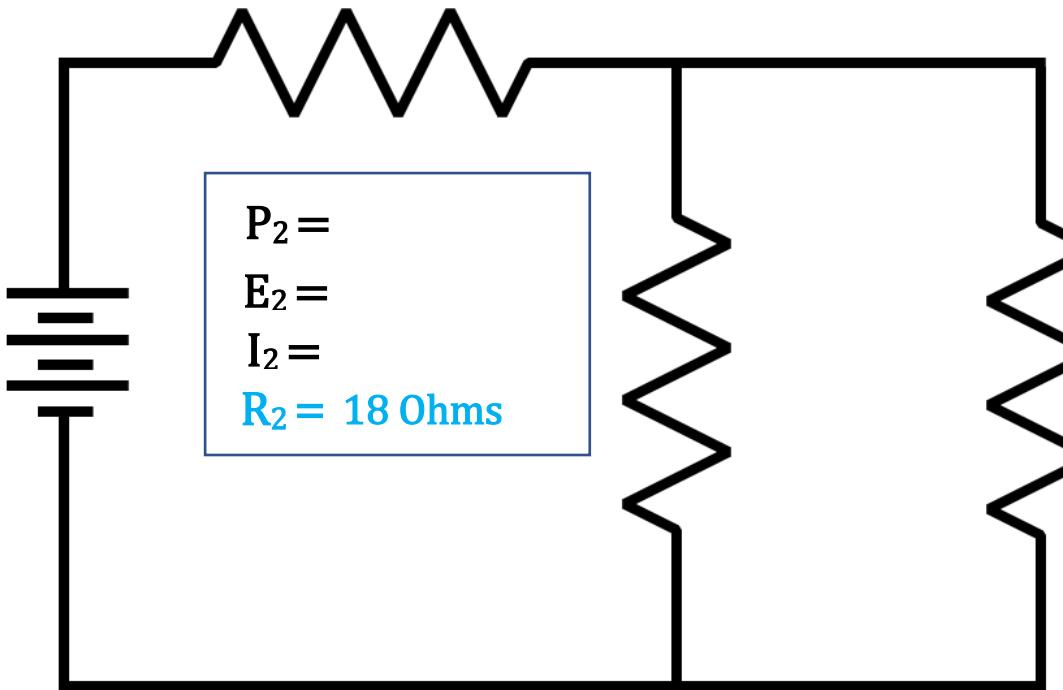
# Rule

$$\begin{aligned}P_1 &= \\E_1 &= \\I_1 &= 3.5 \text{ Amps} \\R_1 &= \end{aligned}$$

$$\begin{aligned}P_T &= 98 \text{ Watts} \\E_T &= 28 \text{ Volts} \\I_T &= 3.5 \text{ Amps} \\R_T &= 8 \text{ Ohms} \end{aligned}$$



$$\begin{aligned}P_2 &= \\E_2 &= \\I_2 &= \\R_2 &= 18 \text{ Ohms} \end{aligned}$$

$$\begin{aligned}P_3 &= \\E_3 &= \\I_3 &= \\R_3 &= 6.6 \text{ Ohms} \end{aligned}$$

$$R_{2,3} = \frac{R_2 \times R_3}{R_2 + R_3}$$

$$R_{2,3} = \frac{18 \times 6.6}{18 + 6.6}$$

$$R_{2,3} = \frac{118.8}{24.6}$$


$$R_{2,3} = 4.83 \text{ Ohms}$$

# Math

$$\begin{aligned}P_T &= 98 \text{ Watts} \\E_T &= 28 \text{ Volts} \\I_T &= 3.5 \text{ Amps} \\R_T &= 8 \text{ Ohms}\end{aligned}$$

$$\begin{aligned}P_1 &= \\E_1 &= \\I_1 &= 3.5 \text{ Amps} \\R_1 &= \end{aligned}$$

# Rule

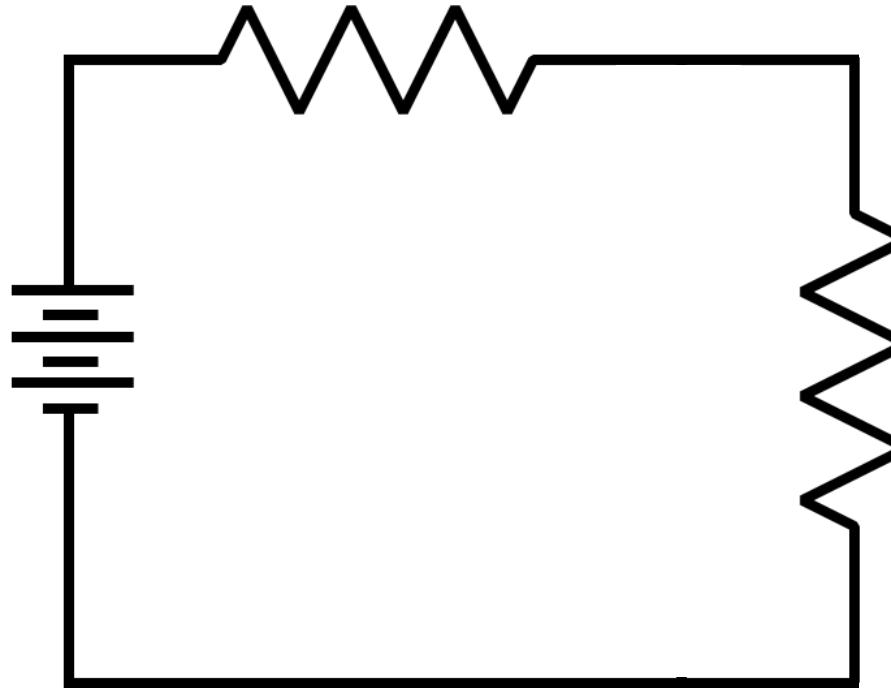

$$\begin{aligned}P_{2,3} &= \\E_{2,3} &= \\I_{2,3} &= \\R_{2,3} &= 4.83 \text{ Ohms}\end{aligned}$$

$$R_{2,3} = \frac{R_2 \times R_3}{R_2 + R_3}$$

$$R_{2,3} = \frac{18 \times 6.6}{18 + 6.6}$$

$$R_{2,3} = \frac{118.8}{24.6}$$


$$R_{2,3} = 4.83 \text{ Ohms}$$

# Math
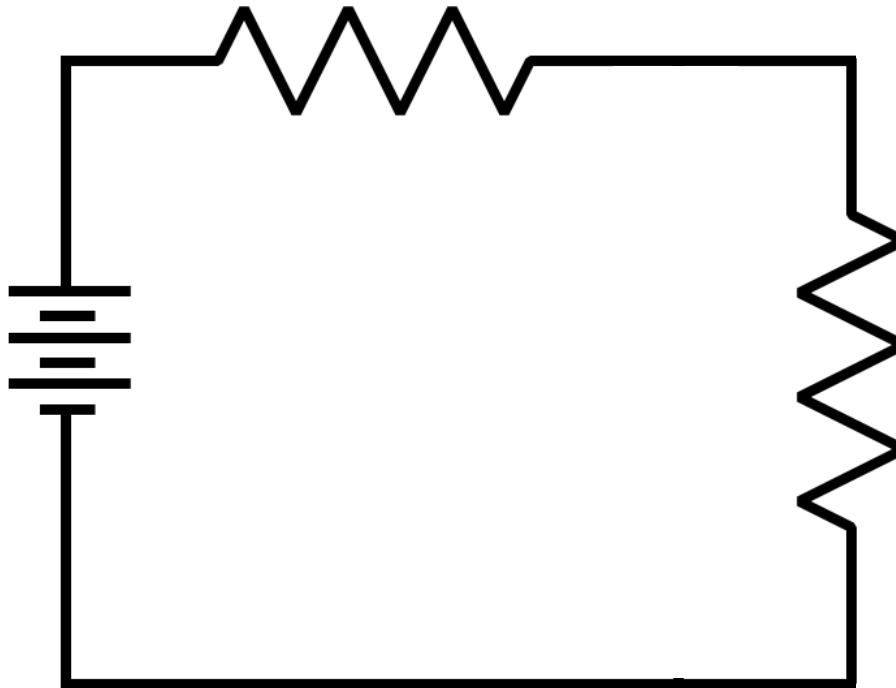
# Rule

$$\begin{aligned}P_1 &= \\E_1 &= \\I_1 &= 3.5 \text{ Amps} \\R_1 &= \end{aligned}$$

$$\begin{aligned}P_T &= 98 \text{ Watts} \\E_T &= 28 \text{ Volts} \\I_T &= 3.5 \text{ Amps} \\R_T &= 8 \text{ Ohms} \end{aligned}$$



$$\begin{aligned}P_{2,3} &= \\E_{2,3} &= \\I_{2,3} &= \\R_{2,3} &= 4.83 \text{ Ohms} \end{aligned}$$

$$R_{2,3} = \frac{R_2 \times R_3}{R_2 + R_3}$$

$$R_{2,3} = \frac{18 \times 6.6}{18 + 6.6}$$

$$R_{2,3} = \frac{118.8}{24.6}$$

$$R_{2,3} = 4.83 \text{ Ohms}$$


$$R_1 = R_T - R_{2,3} = 8 - 4.83 = 3.17 \text{ Ohms}$$

# Math
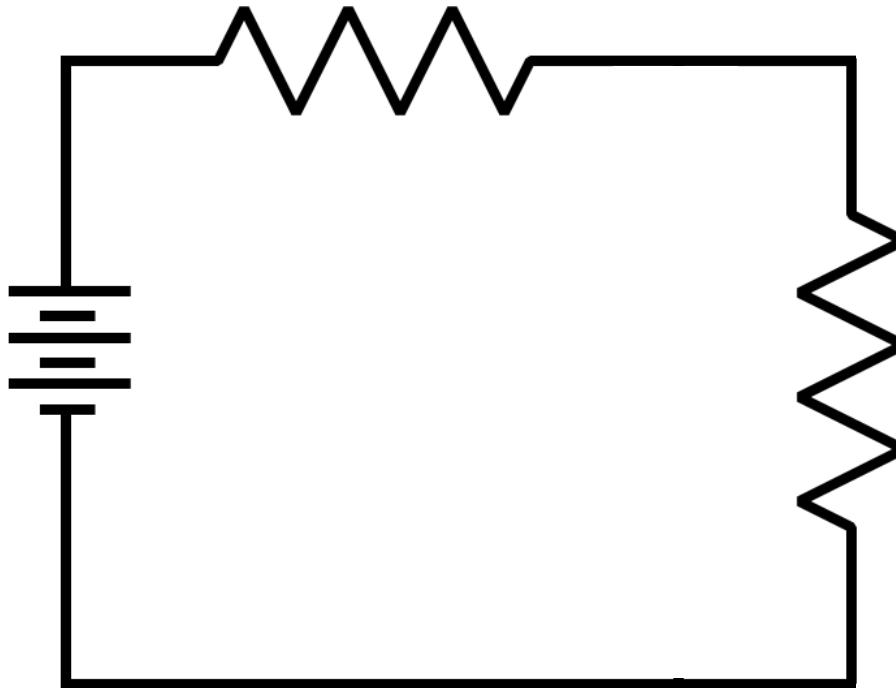
# Rule

$$\begin{aligned}P_1 &= \\E_1 &= \\I_1 &= 3.5 \text{ Amps} \\R_1 &= 3.17 \text{ Ohms}\end{aligned}$$

$$\begin{aligned}P_T &= 98 \text{ Watts} \\E_T &= 28 \text{ Volts} \\I_T &= 3.5 \text{ Amps} \\R_T &= 8 \text{ Ohms}\end{aligned}$$



$$\begin{aligned}P_{2,3} &= \\E_{2,3} &= \\I_{2,3} &= \\R_{2,3} &= 4.83 \text{ Ohms}\end{aligned}$$

$$R_{2,3} = \frac{R_2 \times R_3}{R_2 + R_3}$$

$$R_{2,3} = \frac{18 \times 6.6}{18 + 6.6}$$

$$R_{2,3} = \frac{118.8}{24.6}$$

$$R_{2,3} = 4.83 \text{ Ohms}$$


$$R_1 = R_T - R_{2,3} = 8 - 4.83 = 3.17 \text{ Ohms}$$

# Math
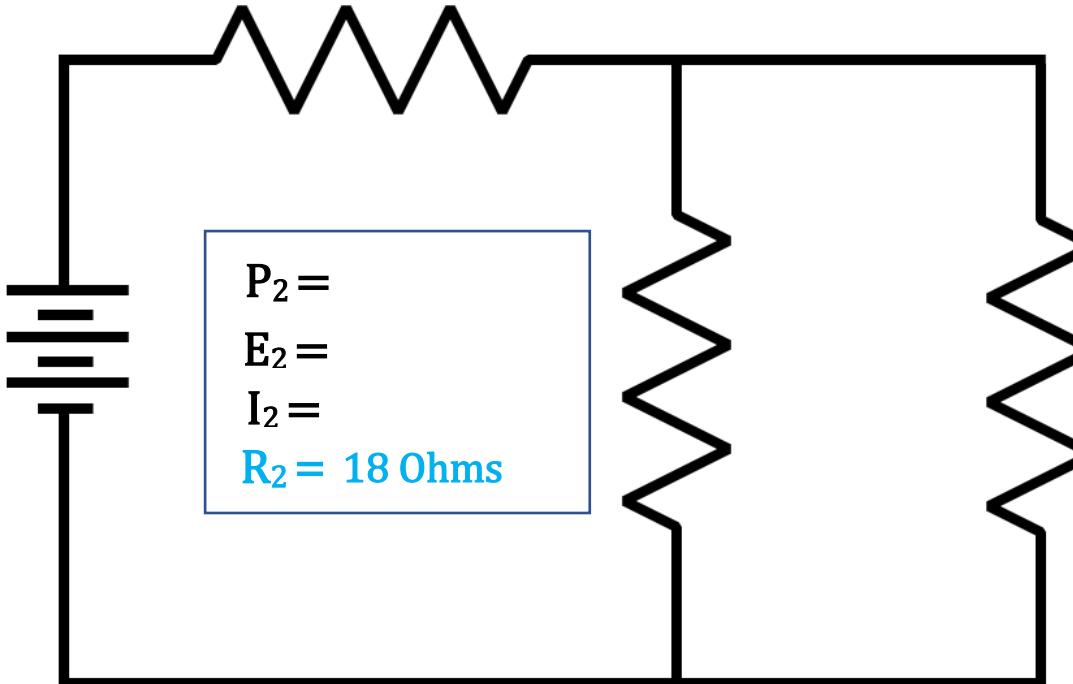
# Rule

$$\begin{aligned}P_1 &= \\E_1 &= \\I_1 &= 3.5 \text{ Amps} \\R_1 &= 3.17 \text{ Ohms}\end{aligned}$$

$$\begin{aligned}P_T &= 98 \text{ Watts} \\E_T &= 28 \text{ Volts} \\I_T &= 3.5 \text{ Amps} \\R_T &= 8 \text{ Ohms}\end{aligned}$$



$$\begin{aligned}P_2 &= \\E_2 &= \\I_2 &= \\R_2 &= 18 \text{ Ohms}\end{aligned}$$

$$\begin{aligned}P_3 &= \\E_3 &= \\I_3 &= \\R_3 &= 6.6 \text{ Ohms}\end{aligned}$$

$$R_{2,3} = \frac{R_2 \times R_3}{R_2 + R_3}$$

$$R_{2,3} = \frac{18 \times 6.6}{18 + 6.6}$$

$$R_{2,3} = \frac{118.8}{24.6}$$

$$R_{2,3} = 4.83 \text{ Ohms}$$


$$R_1 = R_T - R_{2,3} = 8 - 4.83 = 3.17 \text{ Ohms}$$

# Math

$$\begin{aligned}P_T &= 98 \text{ Watts} \\E_T &= 28 \text{ Volts} \\I_T &= 3.5 \text{ Amps} \\R_T &= 8 \text{ Ohms}\end{aligned}$$

$$\begin{aligned}P_1 &= 38.85 \text{ Watts} \\E_1 &= 11.10 \text{ Volts} \\I_1 &= 3.5 \text{ Amps} \\R_1 &= 3.17 \text{ Ohms}\end{aligned}$$

# Rule

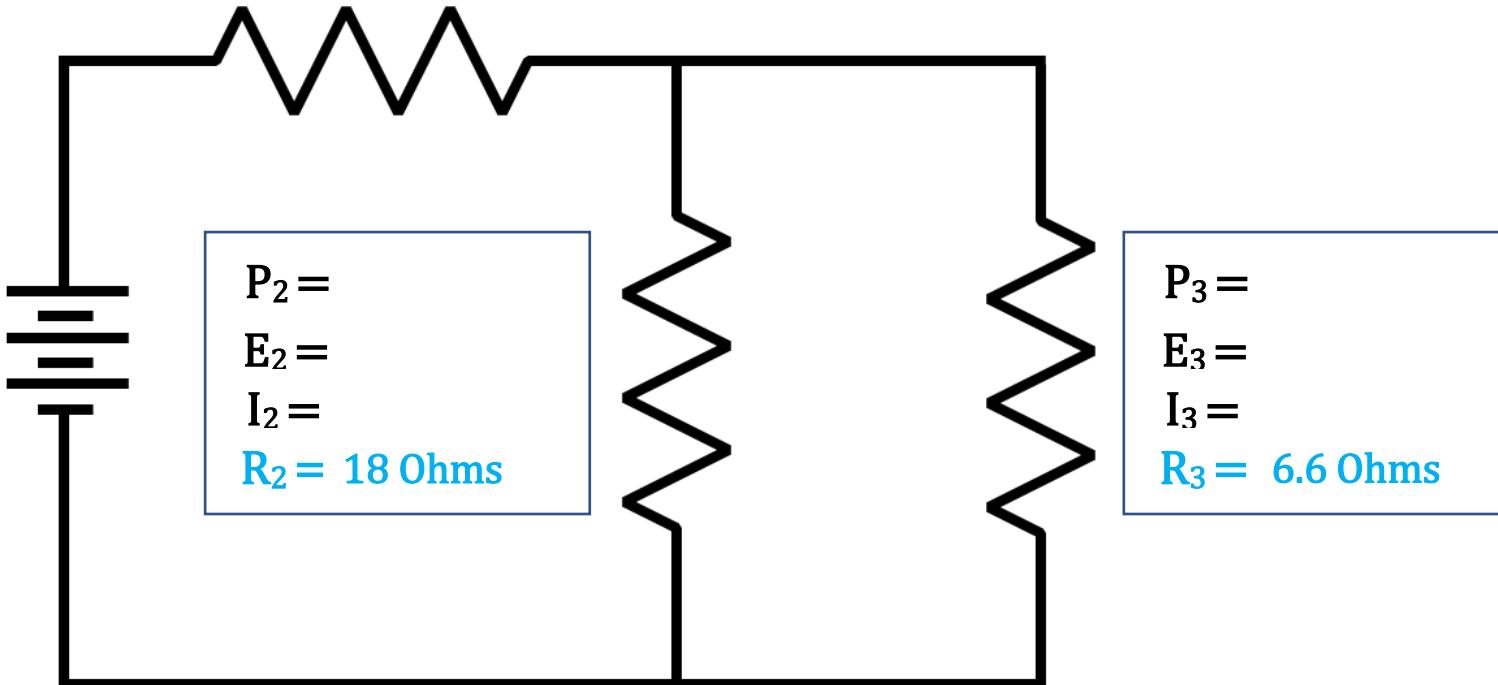


# Math

$$\begin{aligned}P_T &= 98 \text{ Watts} \\E_T &= 28 \text{ Volts} \\I_T &= 3.5 \text{ Amps} \\R_T &= 8 \text{ Ohms}\end{aligned}$$

$$\begin{aligned}P_1 &= 38.85 \text{ Watts} \\E_1 &= 11.10 \text{ Volts} \\I_1 &= 3.5 \text{ Amps} \\R_1 &= 3.17 \text{ Ohms}\end{aligned}$$

# Rule

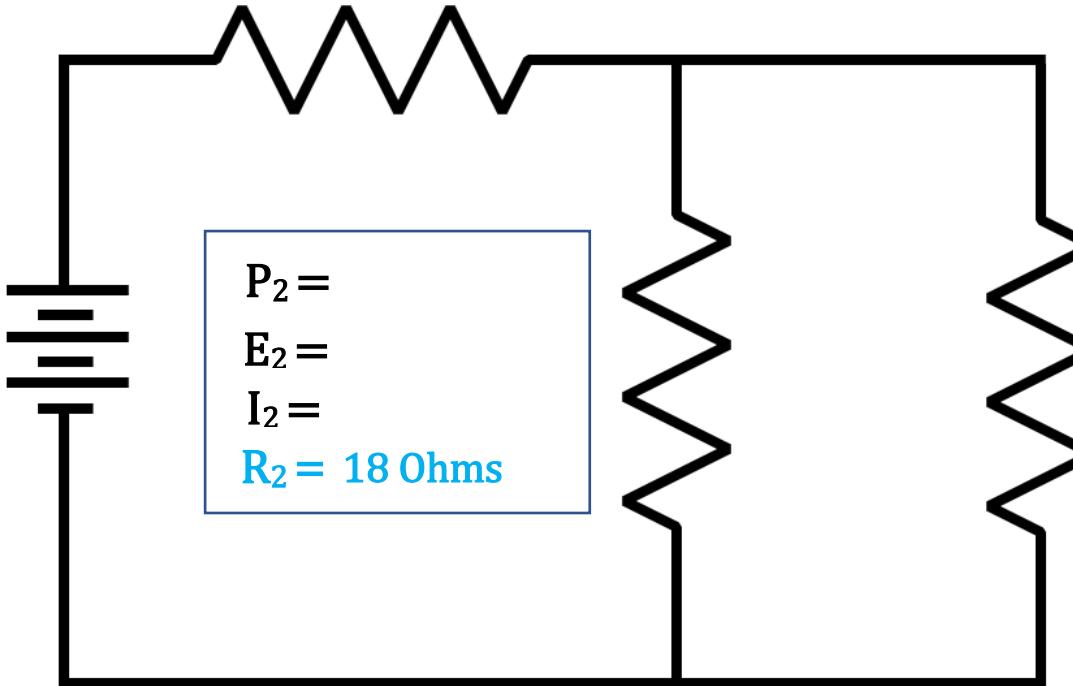


$$E_{2,3} = E_T - E_1 = 28 - 11.10 = 16.9 \text{ Volts}$$

# Math

$$\begin{aligned}P_T &= 98 \text{ Watts} \\E_T &= 28 \text{ Volts} \\I_T &= 3.5 \text{ Amps} \\R_T &= 8 \text{ Ohms}\end{aligned}$$

$$\begin{aligned}P_1 &= 38.85 \text{ Watts} \\E_1 &= 11.10 \text{ Volts} \\I_1 &= 3.5 \text{ Amps} \\R_1 &= 3.17 \text{ Ohms}\end{aligned}$$

# Rule

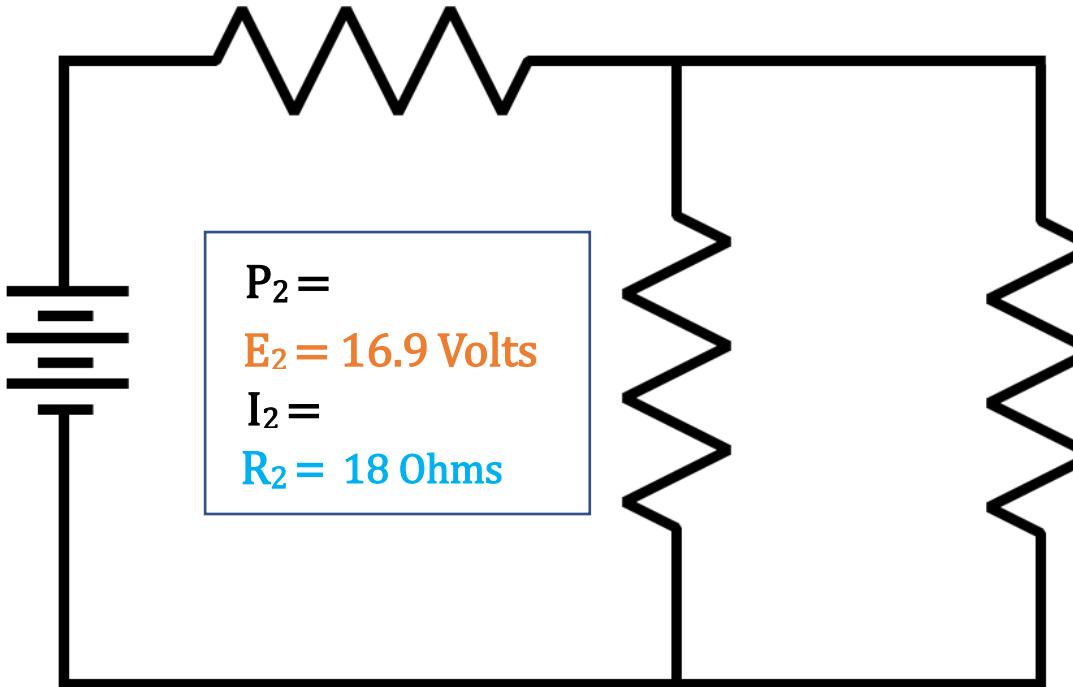

$$\begin{aligned}P_2 &= \\E_2 &= 16.9 \text{ Volts} \\I_2 &= \\R_2 &= 18 \text{ Ohms}\end{aligned}$$

$$\begin{aligned}P_3 &= \\E_3 &= 16.9 \text{ Volts} \\I_3 &= \\R_3 &= 6.6 \text{ Ohms}\end{aligned}$$


$$E_{2,3} = E_T - E_1 = 28 - 11.10 = 16.9 \text{ Volts}$$

# Math

$$\begin{aligned}P_T &= 98 \text{ Watts} \\E_T &= 28 \text{ Volts} \\I_T &= 3.5 \text{ Amps} \\R_T &= 8 \text{ Ohms}\end{aligned}$$

$$\begin{aligned}P_1 &= 38.85 \text{ Watts} \\E_1 &= 11.10 \text{ Volts} \\I_1 &= 3.5 \text{ Amps} \\R_1 &= 3.17 \text{ Ohms}\end{aligned}$$

# Rule

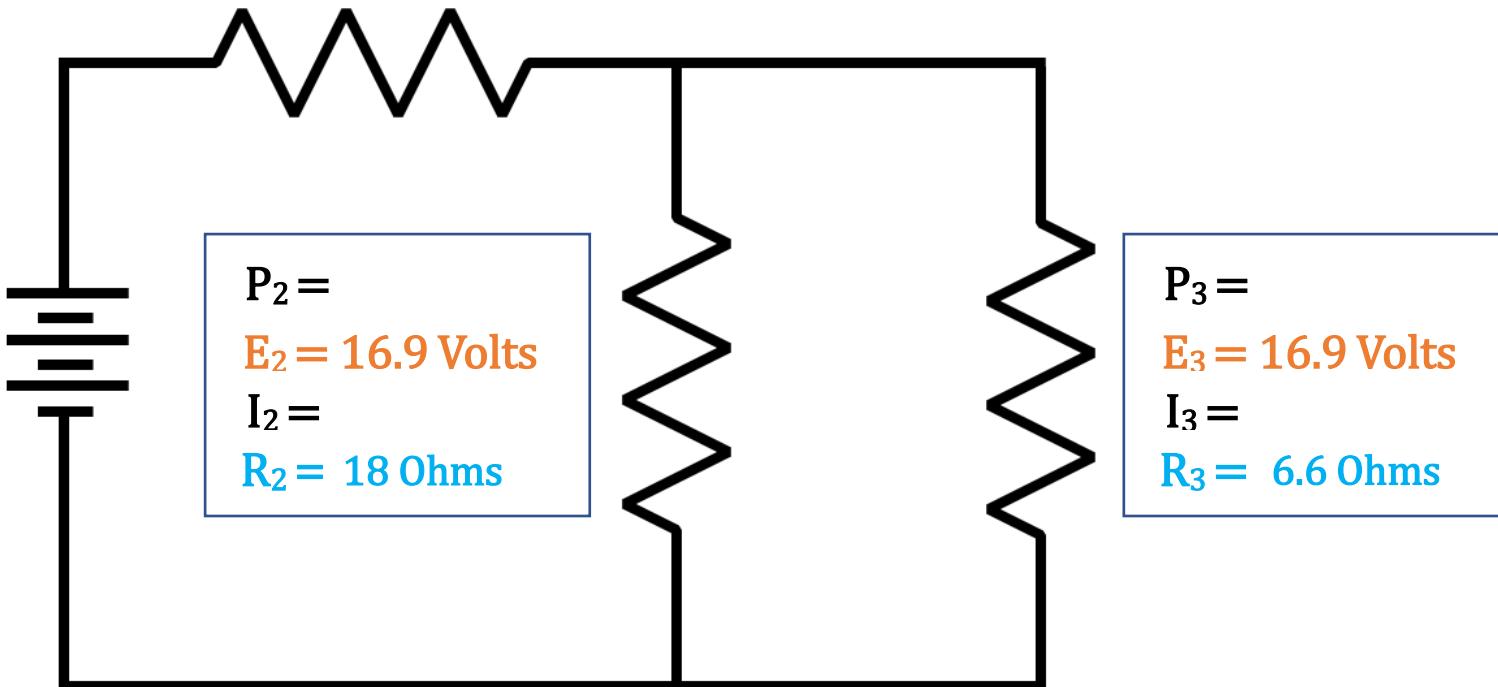


# Math

$$\begin{aligned}P_T &= 98 \text{ Watts} \\E_T &= 28 \text{ Volts} \\I_T &= 3.5 \text{ Amps} \\R_T &= 8 \text{ Ohms}\end{aligned}$$

$$\begin{aligned}P_1 &= 38.85 \text{ Watts} \\E_1 &= 11.10 \text{ Volts} \\I_1 &= 3.5 \text{ Amps} \\R_1 &= 3.17 \text{ Ohms}\end{aligned}$$

# Rule

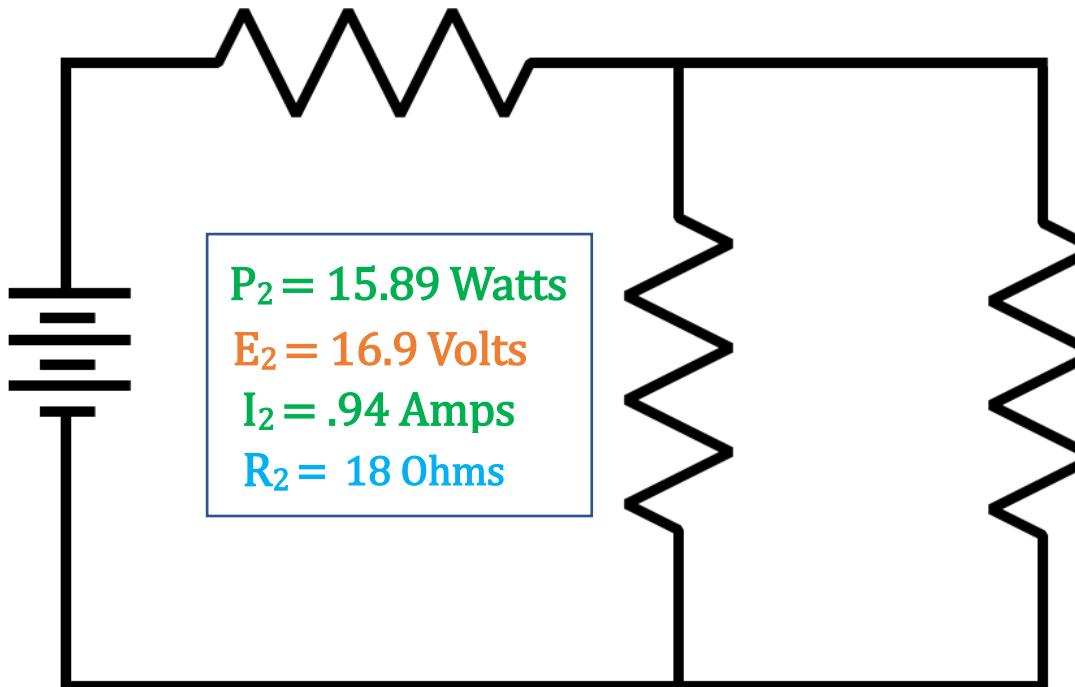

$$\begin{aligned}P_2 &= 15.89 \text{ Watts} \\E_2 &= 16.9 \text{ Volts} \\I_2 &= .94 \text{ Amps} \\R_2 &= 18 \text{ Ohms}\end{aligned}$$

$$\begin{aligned}P_3 &= \\E_3 &= 16.9 \text{ Volts} \\I_3 &= \\R_3 &= 6.6 \text{ Ohms}\end{aligned}$$

# Math

$$\begin{aligned}P_T &= 98 \text{ Watts} \\E_T &= 28 \text{ Volts} \\I_T &= 3.5 \text{ Amps} \\R_T &= 8 \text{ Ohms}\end{aligned}$$

$$\begin{aligned}P_1 &= 38.85 \text{ Watts} \\E_1 &= 11.10 \text{ Volts} \\I_1 &= 3.5 \text{ Amps} \\R_1 &= 3.17 \text{ Ohms}\end{aligned}$$

# Rule

