

Series Parallel Math Example 4

12 V

$P_T =$
 $E_T = 12 \text{ Volts}$
 $I_T =$
 $R_T =$



$P_1 =$
 $E_1 =$
 $I_1 =$
 $R_1 = 50 \text{ Ohms}$



$P_2 =$
 $E_2 =$
 $I_2 =$
 $R_2 =$



$P_3 =$
 $E_3 =$
 $I_3 = 3.25 \text{ Amps}$
 $R_3 =$



$P_4 =$
 $E_4 =$
 $I_4 =$
 $R_4 = 6 \text{ Ohms}$



$P_5 =$
 $E_5 =$
 $I_5 = 11.01 \text{ Amps}$
 $R_5 = .5 \text{ Ohms}$



12 V

$P_T =$
 $E_T = 12 \text{ Volts}$
 $I_T =$
 $R_T =$



$P_1 =$
 $E_1 =$
 $I_1 =$
 $R_1 = 50 \text{ Ohms}$



$P_2 =$
 $E_2 =$
 $I_2 =$
 $R_2 =$



$P_3 =$
 $E_3 =$
 $I_3 = 3.25 \text{ Amps}$
 $R_3 =$



$P_4 =$
 $E_4 =$
 $I_4 =$
 $R_4 = 6 \text{ Ohms}$




$P_5 = 60.67 \text{ Watts}$
 $E_5 = 5.51 \text{ Volts}$
 $I_5 = 11.01 \text{ Amps}$
 $R_5 = .5 \text{ Ohms}$



12 V

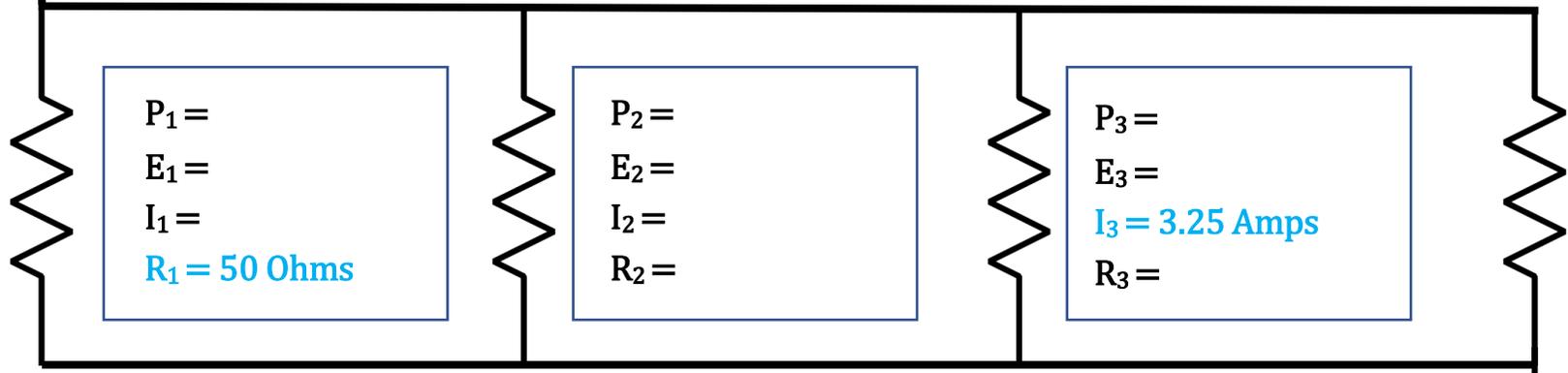$P_T =$
 $E_T = 12 \text{ Volts}$
 $I_T = 11.01 \text{ Amps}$
 $R_T =$



$P_1 =$
 $E_1 =$
 $I_1 =$
 $R_1 = 50 \text{ Ohms}$

$P_2 =$
 $E_2 =$
 $I_2 =$
 $R_2 =$

$P_3 =$
 $E_3 =$
 $I_3 = 3.25 \text{ Amps}$
 $R_3 =$


$P_4 =$
 $E_4 =$
 $I_4 =$
 $R_4 = 6 \text{ Ohms}$

$P_5 = 60.67 \text{ Watts}$
 $E_5 = 5.51 \text{ Volts}$
 $I_5 = 11.01 \text{ Amps}$
 $R_5 = .5 \text{ Ohms}$



12 V

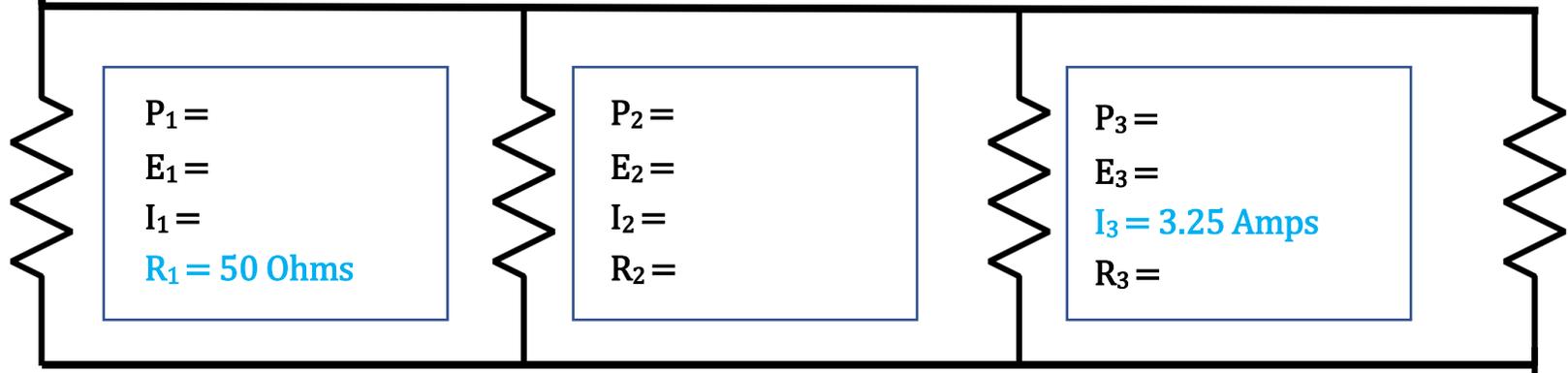$P_T = 132.12$ Watts
 $E_T = 12$ Volts
 $I_T = 11.01$ Amps
 $R_T = 1.09$ Ohms



$P_1 =$
 $E_1 =$
 $I_1 =$
 $R_1 = 50$ Ohms

$P_2 =$
 $E_2 =$
 $I_2 =$
 $R_2 =$

$P_3 =$
 $E_3 =$
 $I_3 = 3.25$ Amps
 $R_3 =$

$P_4 =$
 $E_4 =$
 $I_4 =$
 $R_4 = 6$ Ohms


$P_5 = 60.67$ Watts
 $E_5 = 5.51$ Volts
 $I_5 = 11.01$ Amps
 $R_5 = .5$ Ohms



12 V

$P_T = 132.12$ Watts
 $E_T = 12$ Volts
 $I_T = 11.01$ Amps
 $R_T = 1.09$ Ohms
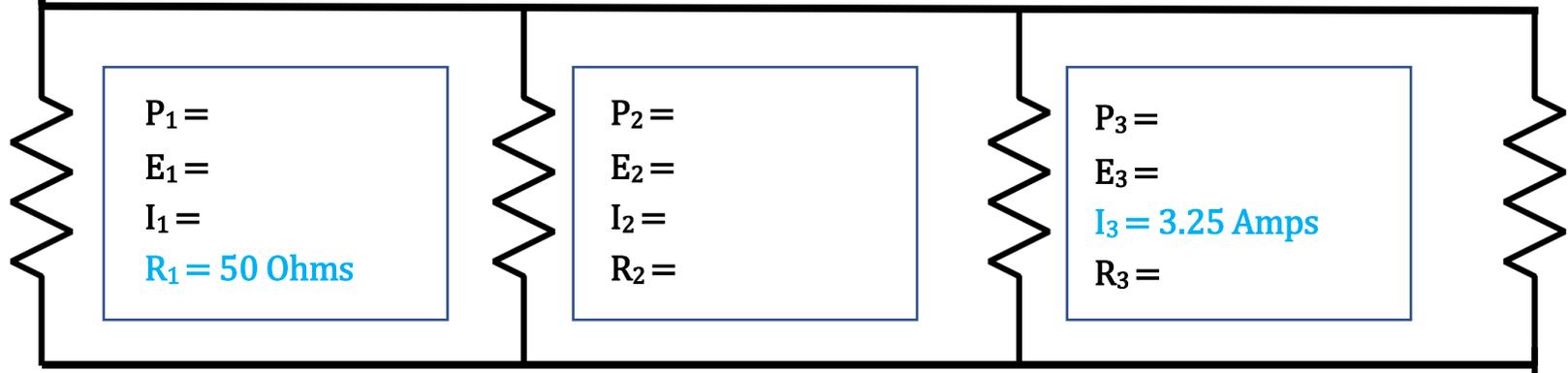
$$E_{1,2,3,4} = E_T - E_5 = 12 - 5.51 = 6.49 \text{ Volts}$$



$P_1 =$
 $E_1 =$
 $I_1 =$
 $R_1 = 50$ Ohms

$P_2 =$
 $E_2 =$
 $I_2 =$
 $R_2 =$

$P_3 =$
 $E_3 =$
 $I_3 = 3.25$ Amps
 $R_3 =$

$P_4 =$
 $E_4 =$
 $I_4 =$
 $R_4 = 6$ Ohms


$P_5 = 60.67$ Watts
 $E_5 = 5.51$ Volts
 $I_5 = 11.01$ Amps
 $R_5 = .5$ Ohms



12 V

$P_T = 132.12$ Watts
 $E_T = 12$ Volts
 $I_T = 11.01$ Amps
 $R_T = 1.09$ Ohms

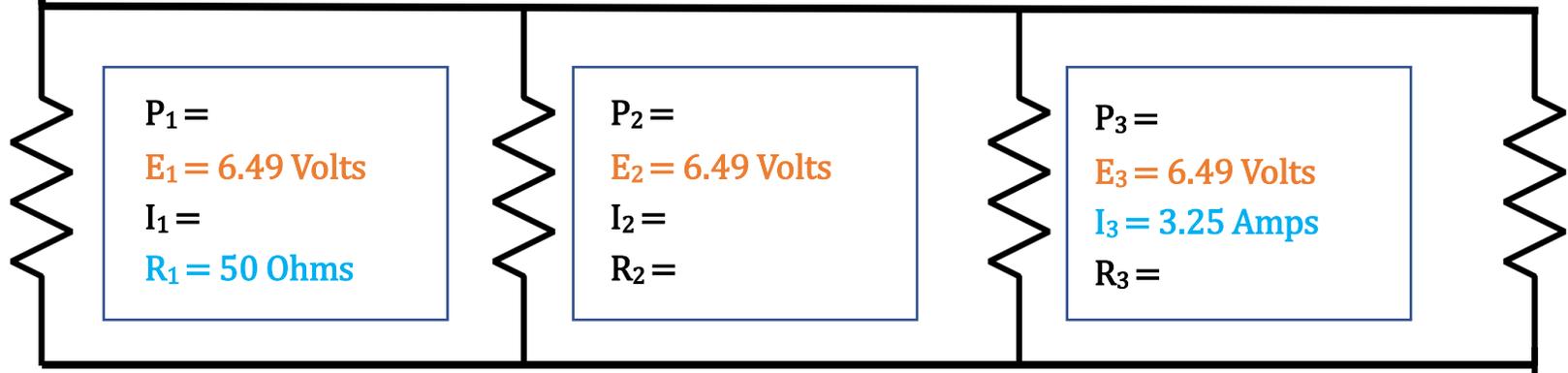$E_{1,2,3,4} = E_T - E_5 = 12 - 5.51 = 6.49$ Volts



$P_1 =$
 $E_1 = 6.49$ Volts
 $I_1 =$
 $R_1 = 50$ Ohms

$P_2 =$
 $E_2 = 6.49$ Volts
 $I_2 =$
 $R_2 =$

$P_3 =$
 $E_3 = 6.49$ Volts
 $I_3 = 3.25$ Amps
 $R_3 =$

$P_4 =$
 $E_4 = 6.49$ Volts
 $I_4 =$
 $R_4 = 6$ Ohms

$P_5 = 60.67$ Watts
 $E_5 = 5.51$ Volts
 $I_5 = 11.01$ Amps
 $R_5 = .5$ Ohms



12 V

$P_T = 132.12$ Watts
 $E_T = 12$ Volts
 $I_T = 11.01$ Amps
 $R_T = 1.09$ Ohms



$P_1 = .84$ Watts
 $E_1 = 6.49$ Volts
 $I_1 = .13$ Amps
 $R_1 = 50$ Ohms



$P_2 =$
 $E_2 = 6.49$ Volts
 $I_2 =$
 $R_2 =$



$P_3 =$
 $E_3 = 6.49$ Volts
 $I_3 = 3.25$ Amps
 $R_3 =$



$P_4 =$
 $E_4 = 6.49$ Volts
 $I_4 =$
 $R_4 = 6$ Ohms




$P_5 = 60.67$ Watts
 $E_5 = 5.51$ Volts
 $I_5 = 11.01$ Amps
 $R_5 = .5$ Ohms



12 V

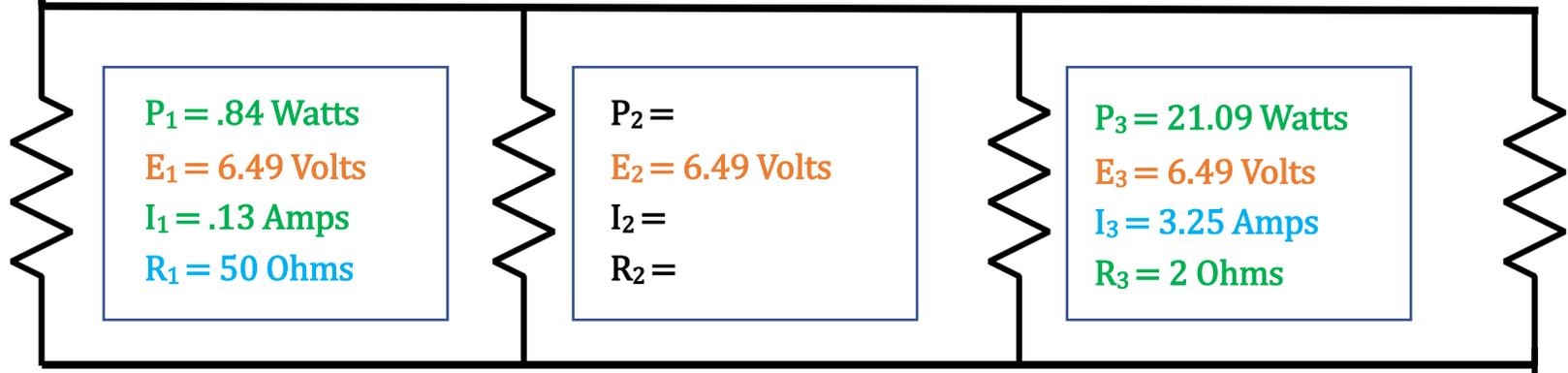$P_T = 132.12$ Watts
 $E_T = 12$ Volts
 $I_T = 11.01$ Amps
 $R_T = 1.09$ Ohms



$P_1 = .84$ Watts
 $E_1 = 6.49$ Volts
 $I_1 = .13$ Amps
 $R_1 = 50$ Ohms

$P_2 =$
 $E_2 = 6.49$ Volts
 $I_2 =$
 $R_2 =$

$P_3 = 21.09$ Watts
 $E_3 = 6.49$ Volts
 $I_3 = 3.25$ Amps
 $R_3 = 2$ Ohms


$P_4 =$
 $E_4 = 6.49$ Volts
 $I_4 =$
 $R_4 = 6$ Ohms

$P_5 = 60.67$ Watts
 $E_5 = 5.51$ Volts
 $I_5 = 11.01$ Amps
 $R_5 = .5$ Ohms



12 V

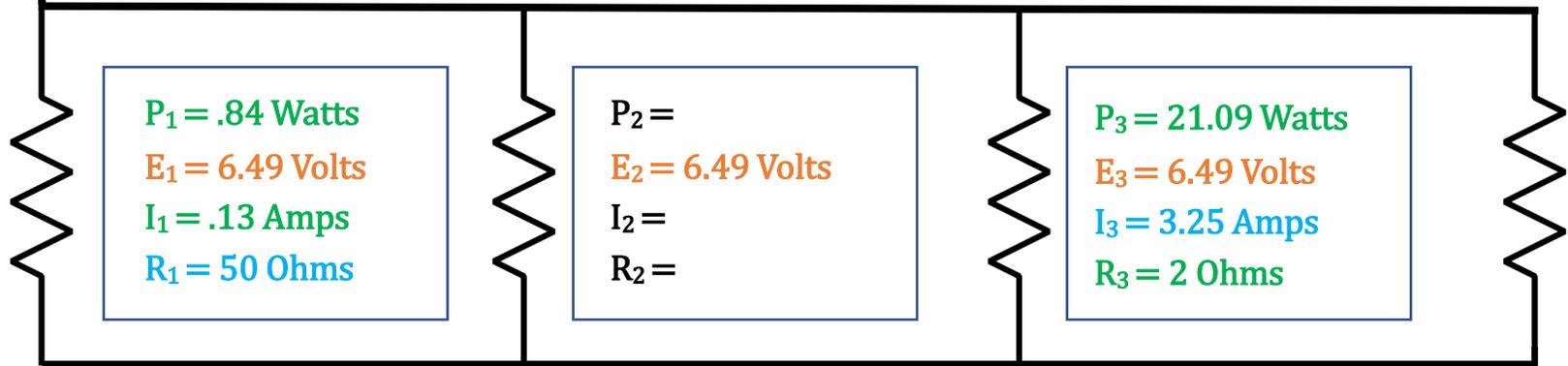$P_T = 132.12$ Watts
 $E_T = 12$ Volts
 $I_T = 11.01$ Amps
 $R_T = 1.09$ Ohms



$P_1 = .84$ Watts
 $E_1 = 6.49$ Volts
 $I_1 = .13$ Amps
 $R_1 = 50$ Ohms

$P_2 =$
 $E_2 = 6.49$ Volts
 $I_2 =$
 $R_2 =$

$P_3 = 21.09$ Watts
 $E_3 = 6.49$ Volts
 $I_3 = 3.25$ Amps
 $R_3 = 2$ Ohms


$P_4 = 7.01$ Watts
 $E_4 = 6.49$ Volts
 $I_4 = 1.08$ Amps
 $R_4 = 6$ Ohms

$P_5 = 60.67$ Watts
 $E_5 = 5.51$ Volts
 $I_5 = 11.01$ Amps
 $R_5 = .5$ Ohms



12 V

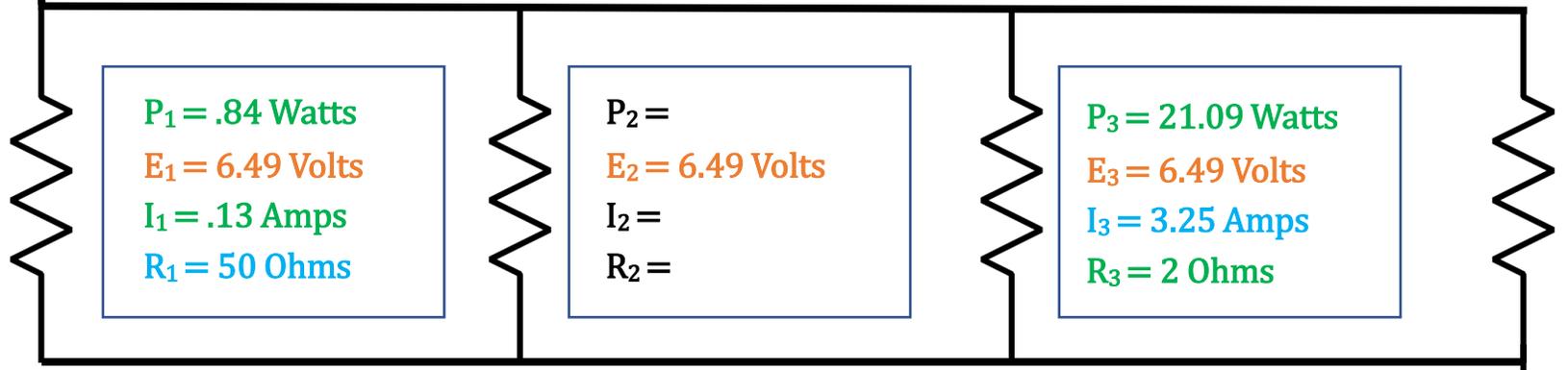$P_T = 132.12$ Watts
 $E_T = 12$ Volts
 $I_T = 11.01$ Amps
 $R_T = 1.09$ Ohms



$P_1 = .84$ Watts
 $E_1 = 6.49$ Volts
 $I_1 = .13$ Amps
 $R_1 = 50$ Ohms

$P_2 =$
 $E_2 = 6.49$ Volts
 $I_2 =$
 $R_2 =$

$P_3 = 21.09$ Watts
 $E_3 = 6.49$ Volts
 $I_3 = 3.25$ Amps
 $R_3 = 2$ Ohms

$P_4 = 7.01$ Watts
 $E_4 = 6.49$ Volts
 $I_4 = 1.08$ Amps
 $R_4 = 6$ Ohms


$P_5 = 60.67$ Watts
 $E_5 = 5.51$ Volts
 $I_5 = 11.01$ Amps
 $R_5 = .5$ Ohms

$I_2 = I_T - I_1 - I_3 - I_4$ $I_2 = 11.01 - .13 - 3.25 - 1.08 = 6.55$ Amps



12 V

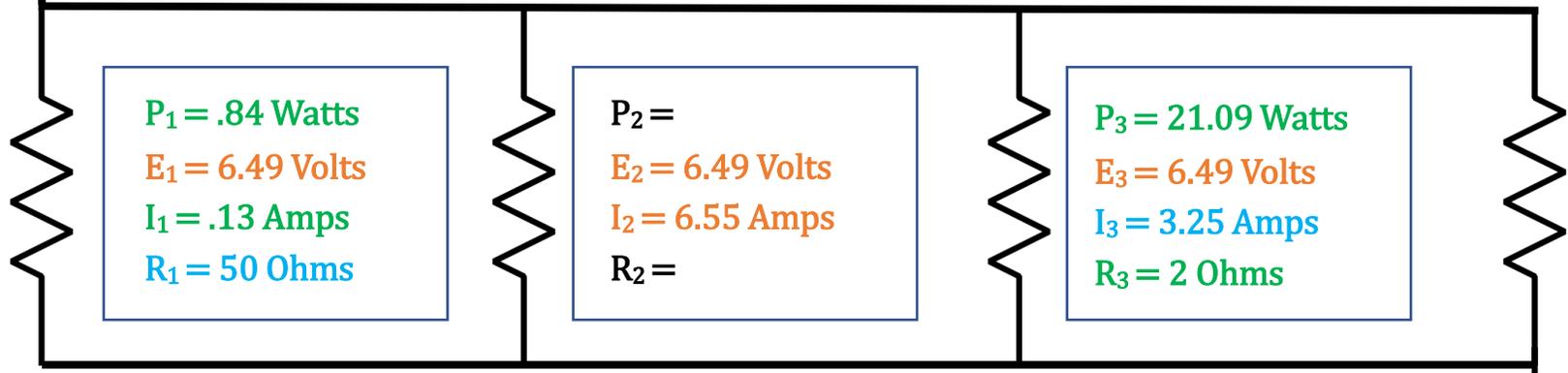$P_T = 132.12$ Watts
 $E_T = 12$ Volts
 $I_T = 11.01$ Amps
 $R_T = 1.09$ Ohms



$P_1 = .84$ Watts
 $E_1 = 6.49$ Volts
 $I_1 = .13$ Amps
 $R_1 = 50$ Ohms

$P_2 =$
 $E_2 = 6.49$ Volts
 $I_2 = 6.55$ Amps
 $R_2 =$

$P_3 = 21.09$ Watts
 $E_3 = 6.49$ Volts
 $I_3 = 3.25$ Amps
 $R_3 = 2$ Ohms

$P_4 = 7.01$ Watts
 $E_4 = 6.49$ Volts
 $I_4 = 1.08$ Amps
 $R_4 = 6$ Ohms

$P_5 = 60.67$ Watts
 $E_5 = 5.51$ Volts
 $I_5 = 11.01$ Amps
 $R_5 = .5$ Ohms

$I_2 = I_T - I_1 - I_3 - I_4$ $I_2 = 11.01 - .13 - 3.25 - 1.08 = 6.55$ Amps

