Consumed by Three Phase Load

Power consumed by three phase load

The power consumed by the three phase load is given by sum of power consumed by each individual load in each phase.

$$\begin{split} P &= \left| V_R \right| \; \left| I_R \right| \; COS\varnothing_R + \left| V_Y \right| \; \left| I_Y \right| \; COS\varnothing_Y + \left| V_B \right| \; \left| I_B \right| \; COS\varnothing_B \\ \text{Where, } \theta_R &= \; \text{Phase difference between } V_R \; \text{and } I_R \\ \theta_Y &= \; \text{Phase difference between } V_Y \; \text{and } I_Y \\ \theta_B &= \; \text{Phase difference between } V_B \; \text{and } I_B \\ \text{Since the system is balanced,} \\ \left| V_R \right| &= \left| V_Y \right| &= \left| V_B \right| &= V \\ \left| I_R \right| &= \left| I_Y \right| &= \left| I_B \right| &= I \\ \theta_R &= \; \theta_Y = \; \theta_B = \; \theta \\ P &= \; VI \; cos\theta \; + \; VI \; cos\theta \\ &= \; \; 3VI \; cos\theta \\ \text{In balanced star system, } V &= \; V_L \; \text{and } I = \; I_L \; / \; \sqrt{3} \\ P &= \; 3V_L \; (I_L \; / \; \sqrt{3}) \; cos\theta \\ P &= \; \sqrt{3} \; V_L \; I_L \; cos\theta \end{split}$$

The above equation represents the power consumed by a three phase star connected load in a four wire system.