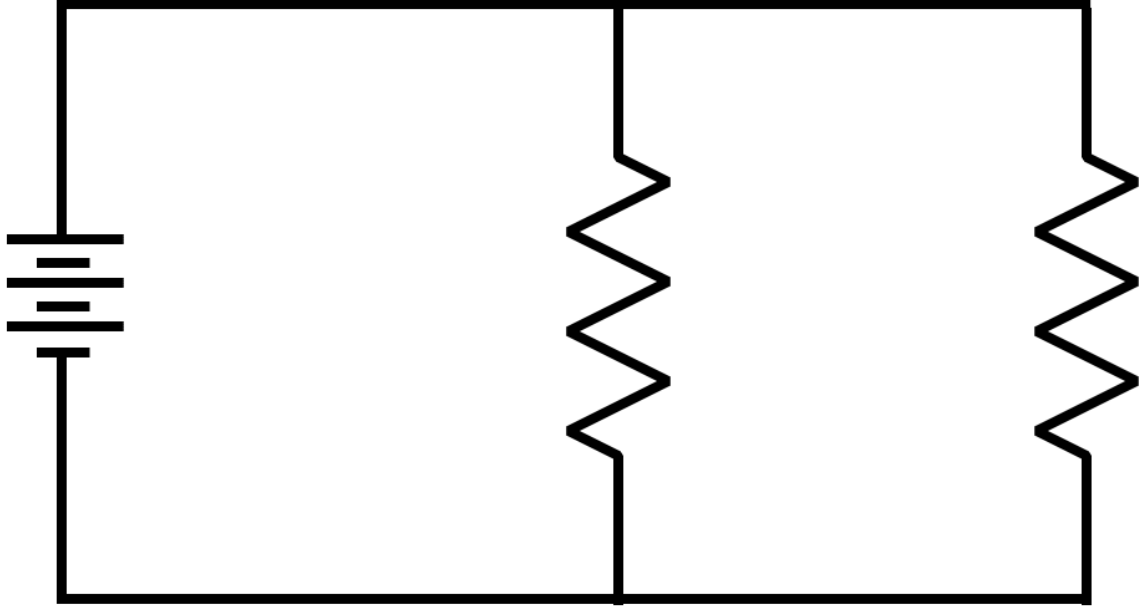


Parallel Example 1

$P_1 =$
 $E_1 =$
 $I_1 =$
 $R_1 =$

$P_T =$
 $E_T =$
 $I_T =$
 $R_T =$



$P_2 =$
 $E_2 =$
 $I_2 =$
 $R_2 =$

Math

Rule

$P_1 =$

$E_1 =$

$I_1 =$


$R_1 =$

$P_T =$

$E_T =$

$I_T =$

$R_T =$

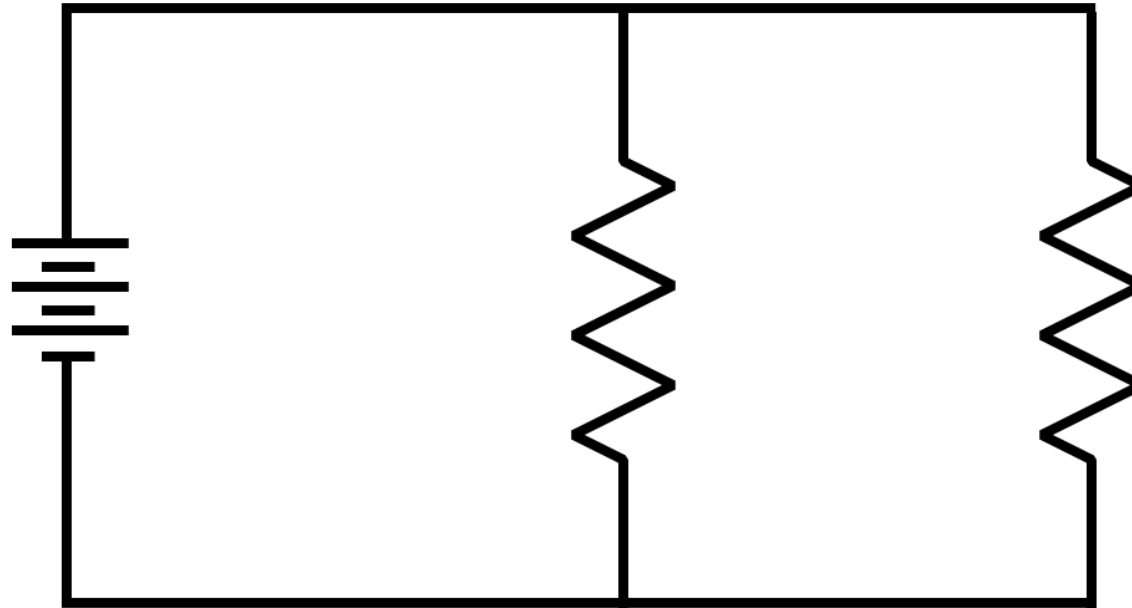

$P_2 =$

$E_2 =$

$I_2 =$

$R_2 =$

$E_T = 48$ Volts

$R_1 = 14.4$ Ohms

$I_2 = 8$ Amps


Find All Values of P, E, I and R using Ohm's Law and Parallel Rules

Math

Rule

$$\begin{aligned} P_1 &= \\ E_1 &= \\ I_1 &= \\ R_1 &= 14.4 \text{ Ohms} \end{aligned}$$
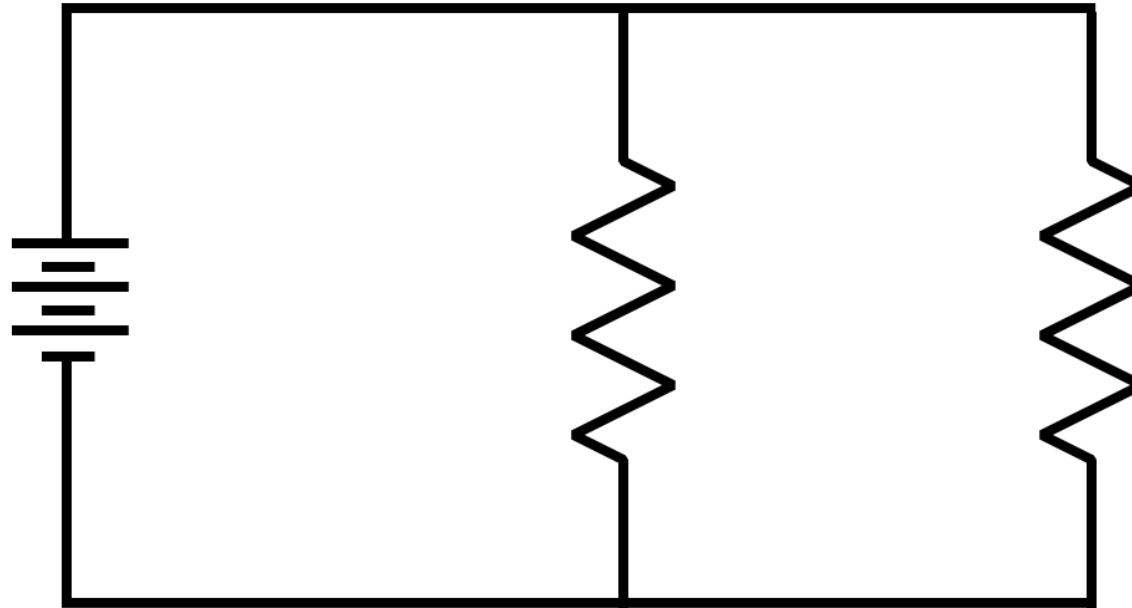
$$\begin{aligned} P_T &= \\ E_T &= 48 \text{ Volts} \\ I_T &= \\ R_T &= \end{aligned}$$



$$\begin{aligned} P_2 &= \\ E_2 &= \\ I_2 &= 8 \text{ Amps} \\ R_2 &= \end{aligned}$$

$$E_T = 48 \text{ Volts}$$

$$R_1 = 14.4 \text{ Ohms}$$

$$I_2 = 8 \text{ Amps}$$


Find All Values of P, E, I and R using Ohm's Law and Parallel Rules

Math

Rule

$$P_1 =$$
$$E_1 = 48 \text{ Volts}$$
$$I_1 =$$
$$R_1 = 14.4 \text{ Ohms}$$
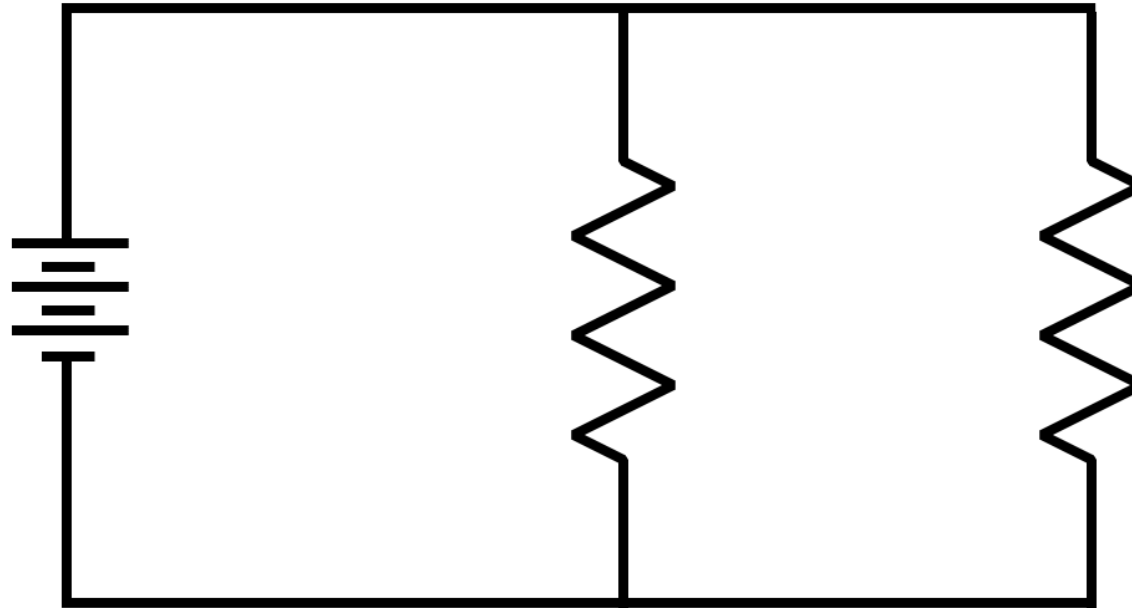
$$P_T =$$
$$E_T = 48 \text{ Volts}$$
$$I_T =$$
$$R_T =$$



$$P_2 =$$
$$E_2 = 48 \text{ Volts}$$
$$I_2 = 8 \text{ Amps}$$
$$R_2 =$$

$$E_T = 48 \text{ Volts}$$

$$R_1 = 14.4 \text{ Ohms}$$

$$I_2 = 8 \text{ Amps}$$


Find All Values of P, E, I and R using Ohm's Law and Parallel Rules

Math

Rule

$$P_1 =$$
$$E_1 = 48 \text{ Volts}$$
$$I_1 = 3.33 \text{ Amps}$$
$$R_1 = 14.4 \text{ Ohms}$$
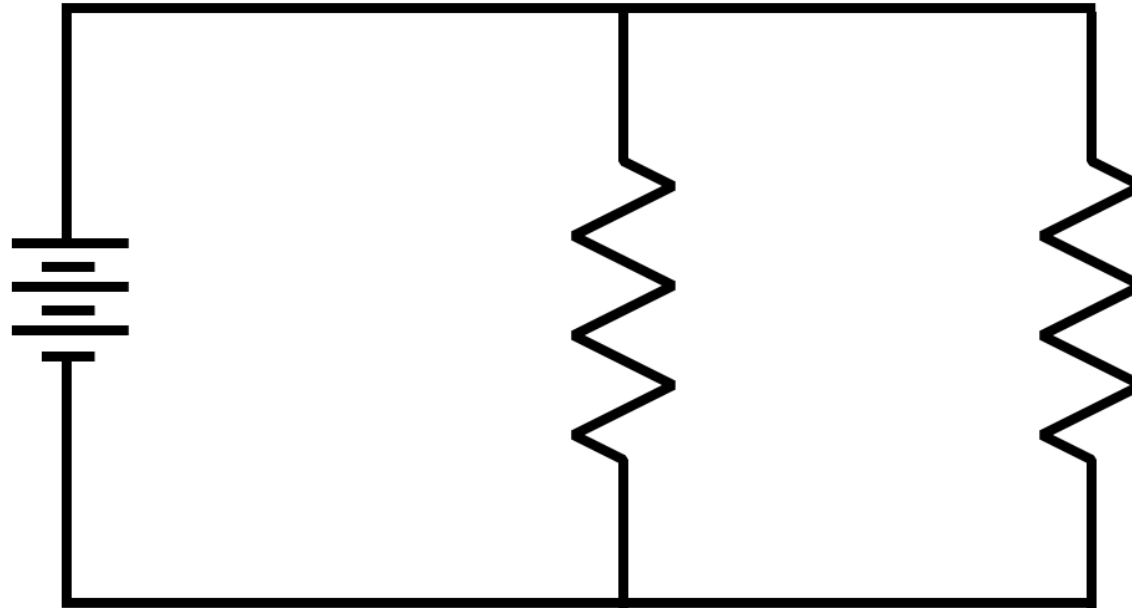
$$P_T =$$
$$E_T = 48 \text{ Volts}$$
$$I_T =$$
$$R_T =$$



$$P_2 =$$
$$E_2 = 48 \text{ Volts}$$
$$I_2 = 8 \text{ Amps}$$
$$R_2 = 6 \text{ Ohms}$$

$$E_T = 48 \text{ Volts}$$

$$R_1 = 14.4 \text{ Ohms}$$

$$I_2 = 8 \text{ Amps}$$

Find All Values of P, E, I and R using Ohm's Law and Parallel Rules

Math

Rule

$$P_1 = 159.84 \text{ Watts}$$

$$E_1 = 48 \text{ Volts}$$

$$I_1 = 3.33 \text{ Amps}$$


$$R_1 = 14.4 \text{ Ohms}$$

$$P_T =$$

$$E_T = 48 \text{ Volts}$$

$$I_T =$$

$$R_T =$$

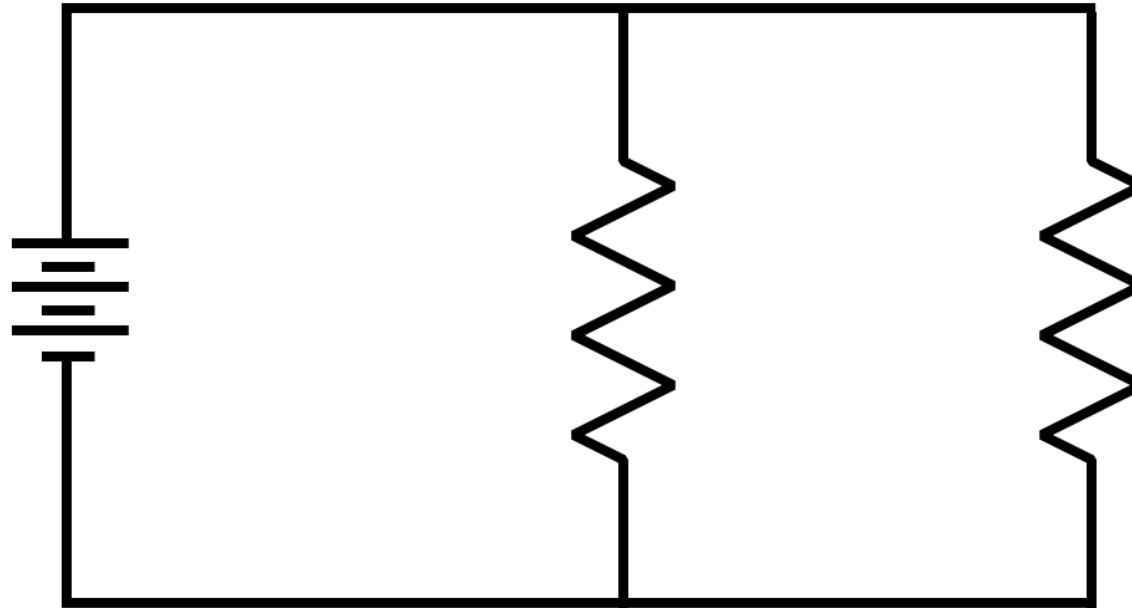

$$P_2 = 384 \text{ Watts}$$

$$E_2 = 48 \text{ Volts}$$

$$I_2 = 8 \text{ Amps}$$

$$R_2 = 6 \text{ Ohms}$$

$$E_T = 48 \text{ Volts}$$

$$R_1 = 14.4 \text{ Ohms}$$

$$I_2 = 8 \text{ Amps}$$

Find All Values of P, E, I and R using Ohm's Law and Parallel Rules

Math

Rule

$$P_1 = 159.84 \text{ Watts}$$

$$E_1 = 48 \text{ Volts}$$

$$I_1 = 3.33 \text{ Amps}$$


$$R_1 = 14.4 \text{ Ohms}$$

$$P_T =$$

$$E_T = 48 \text{ Volts}$$

$$I_T = 11.33 \text{ Amps}$$

$$R_T =$$

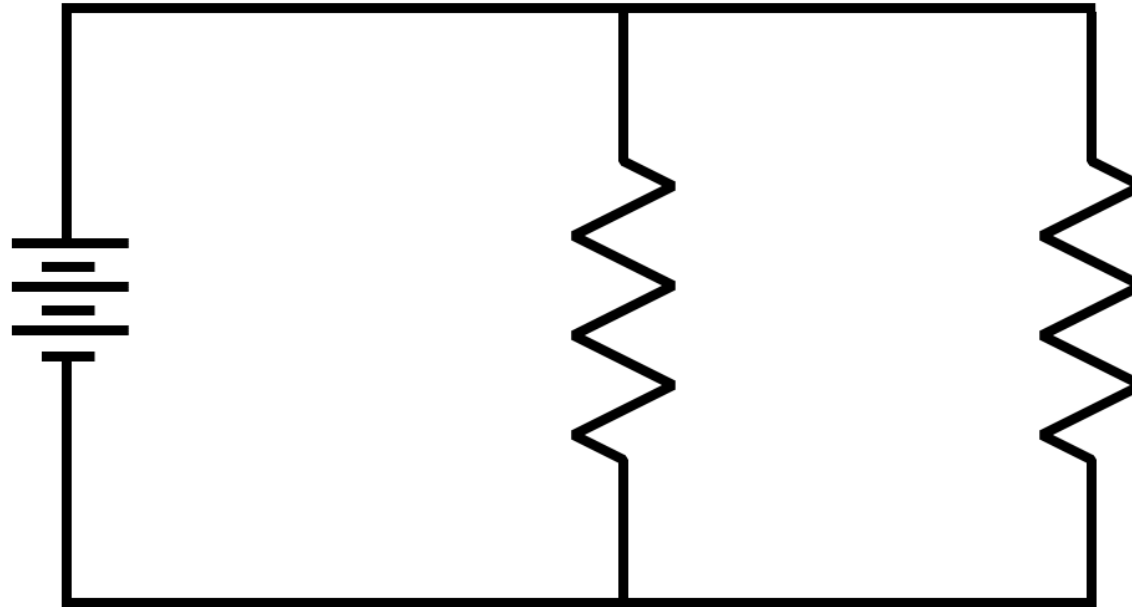

$$P_2 = 384 \text{ Watts}$$

$$E_2 = 48 \text{ Volts}$$

$$I_2 = 8 \text{ Amps}$$

$$R_2 = 6 \text{ Ohms}$$

$$E_T = 48 \text{ Volts}$$

$$R_1 = 14.4 \text{ Ohms}$$

$$I_2 = 8 \text{ Amps}$$

Find All Values of P, E, I and R using Ohm's Law and Parallel Rules

Math

Rule

$$P_1 = 159.84 \text{ Watts}$$

$$E_1 = 48 \text{ Volts}$$

$$I_1 = 3.33 \text{ Amps}$$


$$R_1 = 14.4 \text{ Ohms}$$

$$P_T = 543.84 \text{ Watts}$$

$$E_T = 48 \text{ Volts}$$

$$I_T = 11.33 \text{ Amps}$$

$$R_T = 4.24 \text{ Ohms}$$

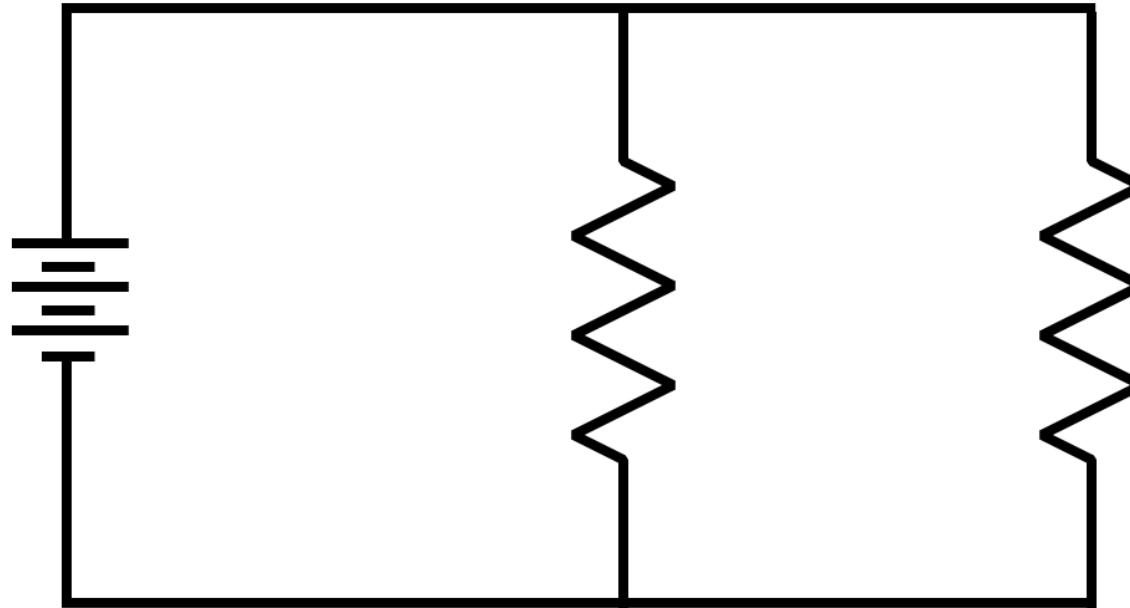

$$P_2 = 384 \text{ Watts}$$

$$E_2 = 48 \text{ Volts}$$

$$I_2 = 8 \text{ Amps}$$

$$R_2 = 6 \text{ Ohms}$$

$$E_T = 48 \text{ Volts}$$

$$R_1 = 14.4 \text{ Ohms}$$

$$I_2 = 8 \text{ Amps}$$

Find All Values of P, E, I and R using Ohm's Law and Parallel Rules