

Math

$P_1 =$

$E_1 = 12.6 \text{ Volts}$

$I_1 =$

$R_1 = 6.4 \text{ Ohms}$

$P_2 =$

$E_2 =$

$I_2 =$

$R_2 = 4 \text{ Ohms}$


Rule

$P_T =$

$E_T =$

$I_T =$

$R_T =$

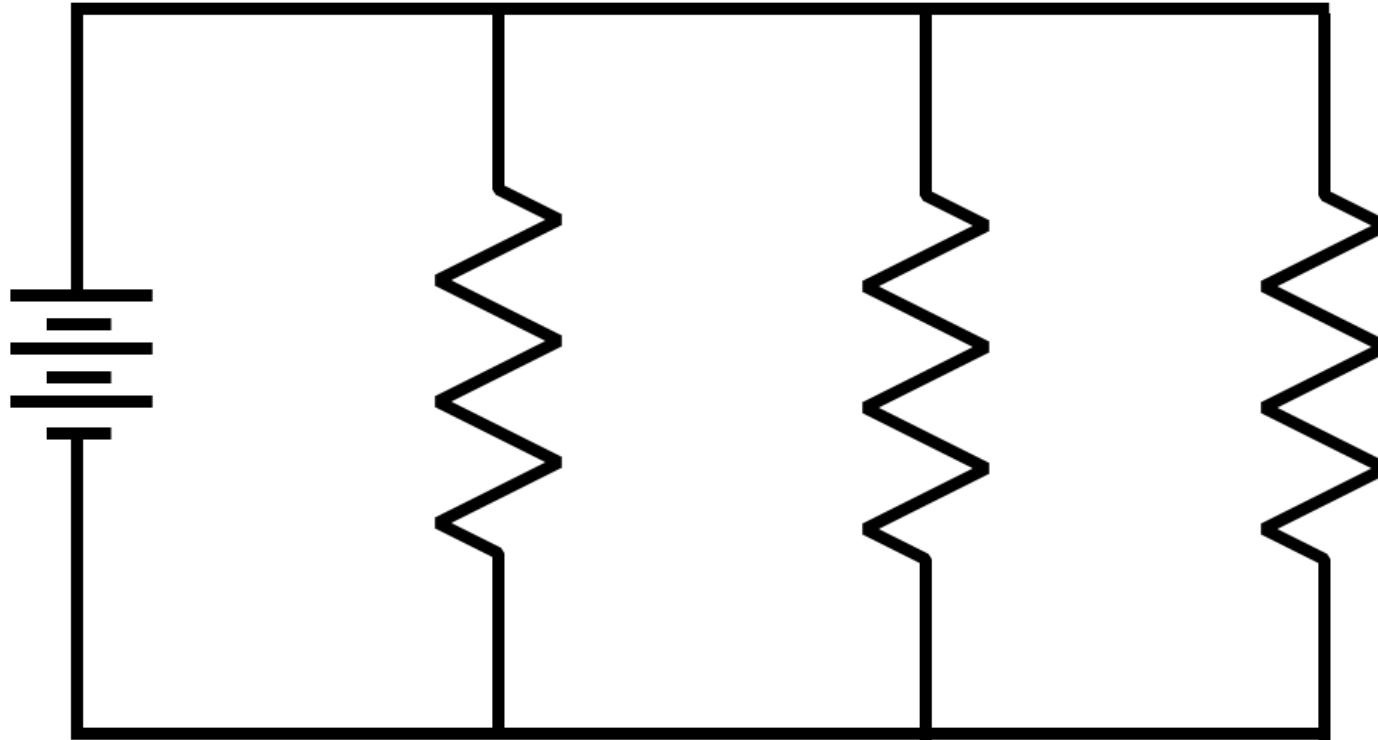

$P_3 =$

$E_3 =$

$I_3 =$

$R_3 = 16 \text{ Ohms}$

$E_1 = 12.6 \text{ Volts}$

$R_1 = 6.4 \text{ Ohms}$

$R_2 = 4 \text{ Ohms}$

$R_3 = 16 \text{ Ohms}$

Find All Values of P, E, I and R using Ohm's Law and Parallel Rules