

Example 3

Math

Rule

$P_1 =$

$E_1 =$

$I_1 =$

$R_1 =$

$P_2 =$

$E_2 =$

$I_2 =$

$R_2 =$

$P_T =$

$E_T =$

$I_T =$


$R_T =$

$P_3 =$

$E_3 =$

$I_3 =$

$R_3 =$

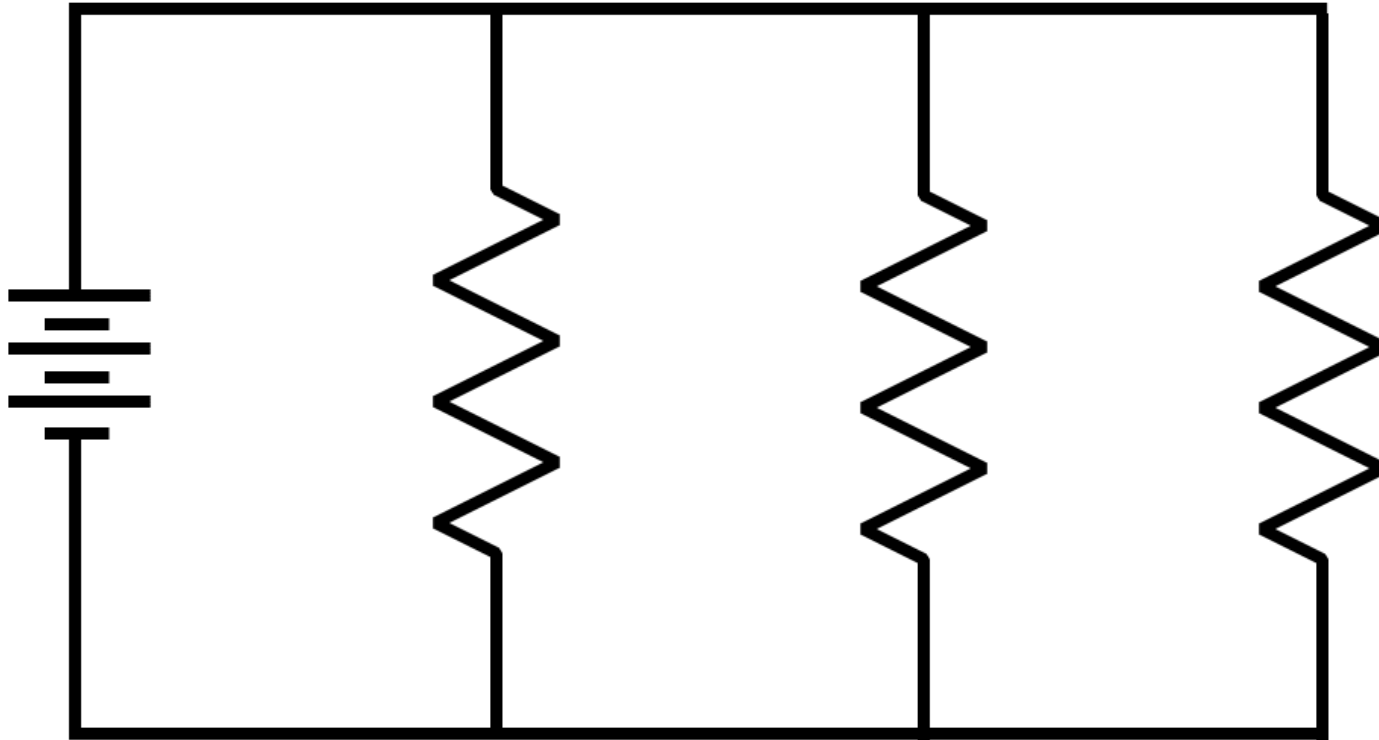

$I_T = 10 \text{ Amps}$

$R_1 = 12 \text{ Ohms}$

$R_2 = 8 \text{ Ohms}$

$R_3 = 4.8 \text{ Ohms}$

Find All Values of P, E, I and R using Ohm's Law and Parallel Rules

Math

Rule

$P_1 =$

$E_1 =$

$I_1 =$

$R_1 = 12 \text{ Ohms}$

$P_2 =$

$E_2 =$

$I_2 =$

$R_2 = 8 \text{ Ohms}$

$P_T =$

$E_T =$

$I_T = 10 \text{ Amps}$


$R_T =$

$P_3 =$

$E_3 =$

$I_3 =$

$R_3 = 4.8 \text{ Ohms}$

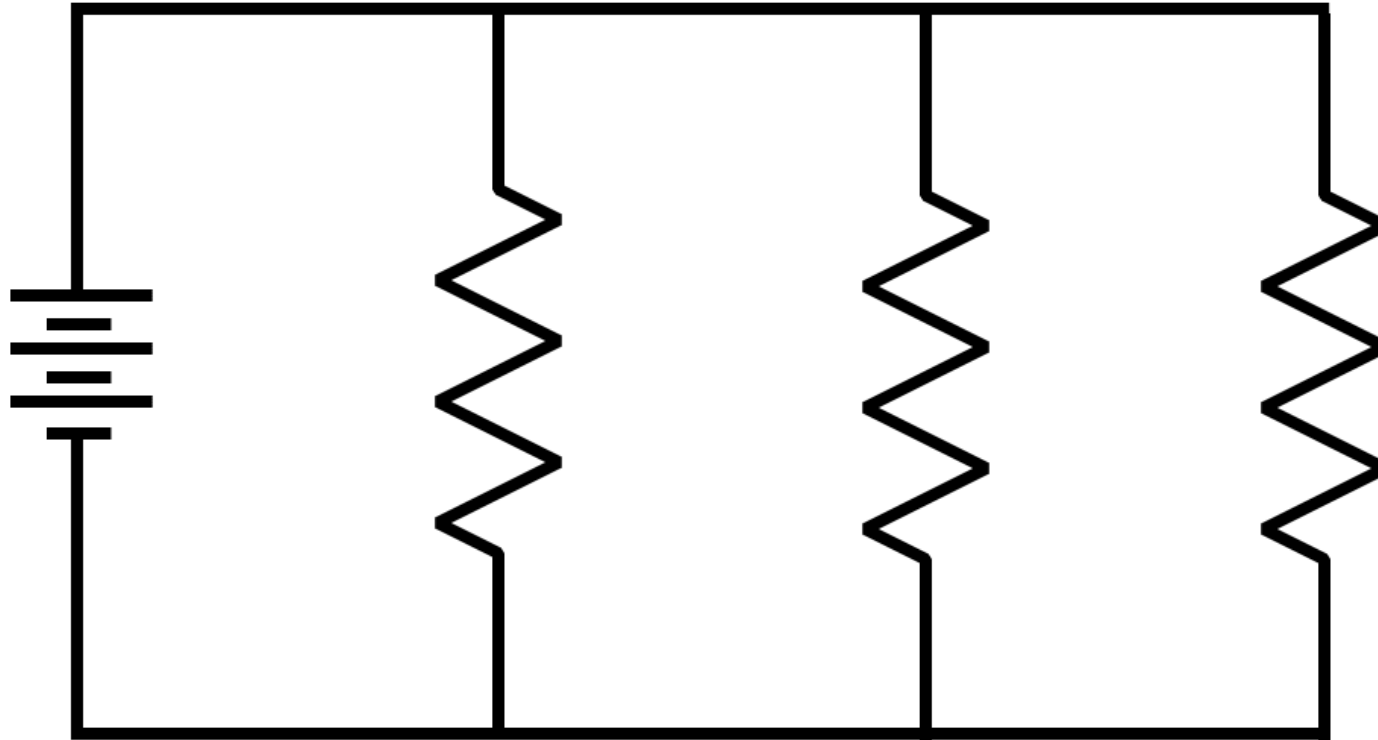

$I_T = 10 \text{ Amps}$

$R_1 = 12 \text{ Ohms}$

$R_2 = 8 \text{ Ohms}$

$R_3 = 4.8 \text{ Ohms}$

Find All Values of P, E, I and R using Ohm's Law and Parallel Rules

Math

Rule

$P_1 =$

$E_1 =$

$I_1 =$

$R_1 = 12 \text{ Ohms}$

$P_2 =$

$E_2 =$

$I_2 =$


$R_2 = 8 \text{ Ohms}$

$P_T =$

$E_T =$

$I_T = 10 \text{ Amps}$

$R_T = 2.4 \text{ Ohms}$

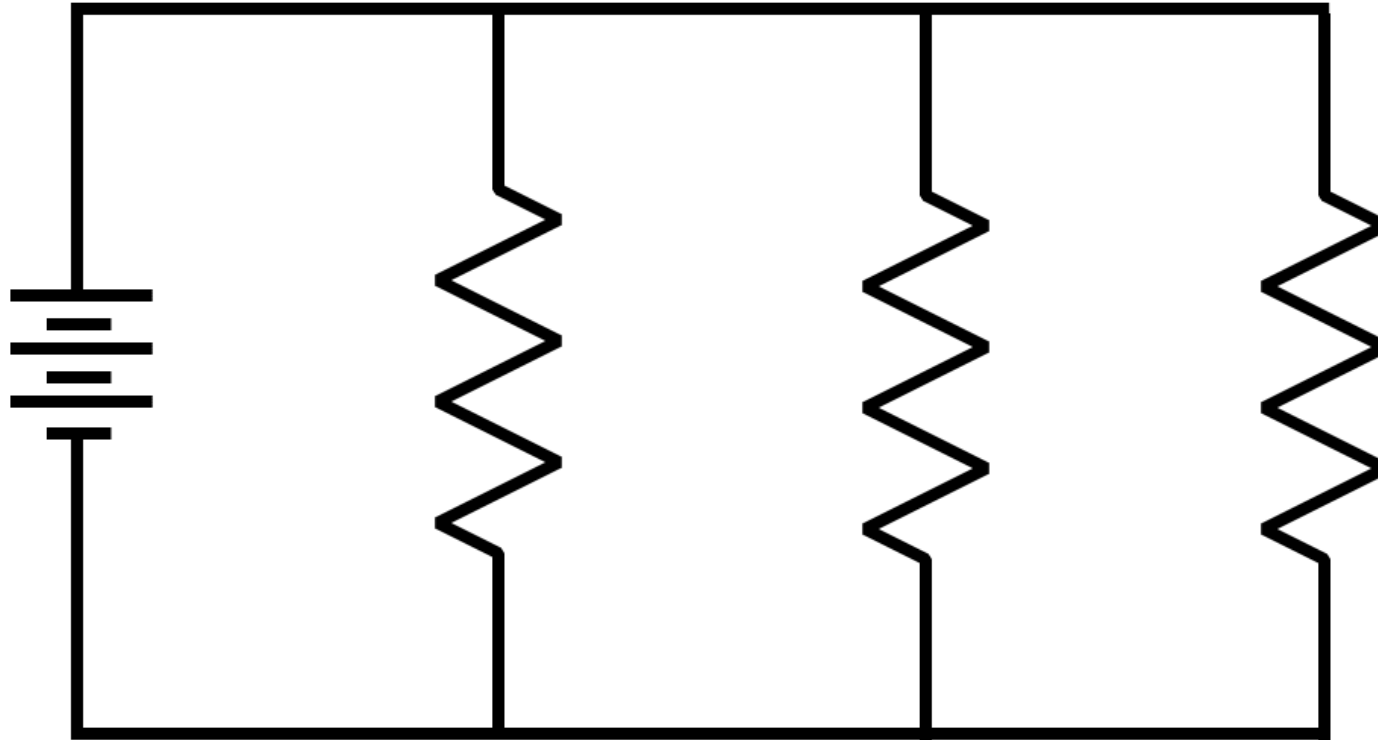

$P_3 =$

$E_3 =$

$I_3 =$

$R_3 = 4.8 \text{ Ohms}$

$I_T = 10 \text{ Amps}$

$R_1 = 12 \text{ Ohms}$

$R_2 = 8 \text{ Ohms}$

$R_3 = 4.8 \text{ Ohms}$

Find All Values of P, E, I and R using Ohm's Law and Parallel Rules

Math

$P_1 =$

$E_1 =$

$I_1 =$

$R_1 = 12 \text{ Ohms}$

$P_2 =$

$E_2 =$

$I_2 =$

$R_2 = 8 \text{ Ohms}$


Rule

$P_T = 240 \text{ Watts}$

$E_T = 24 \text{ Volts}$

$I_T = 10 \text{ Amps}$

$R_T = 2.4 \text{ Ohms}$

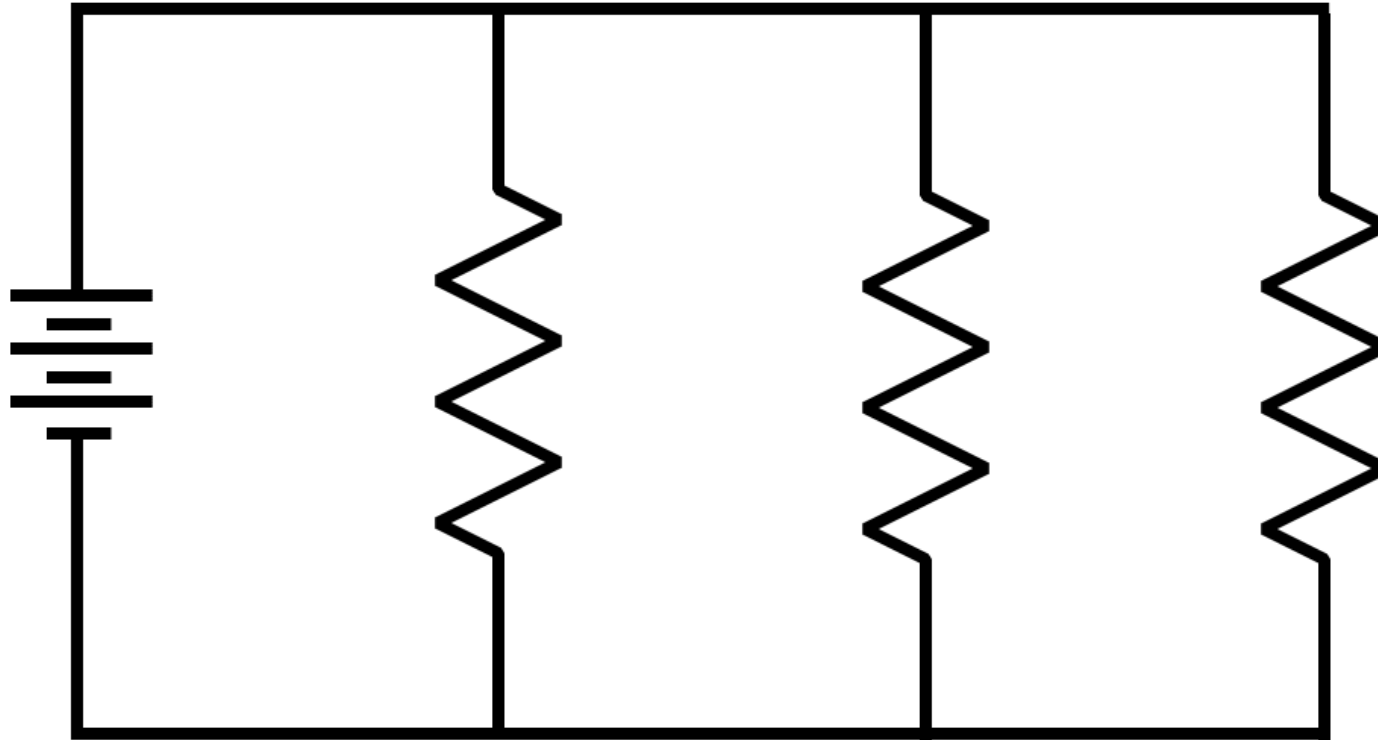

$P_3 =$

$E_3 =$

$I_3 =$

$R_3 = 4.8 \text{ Ohms}$

$I_T = 10 \text{ Amps}$

$R_1 = 12 \text{ Ohms}$

$R_2 = 8 \text{ Ohms}$

$R_3 = 4.8 \text{ Ohms}$

Find All Values of P, E, I and R using Ohm's Law and Parallel Rules


Math

Rule

$$P_1 =$$
$$E_1 = 24 \text{ Volts}$$
$$I_1 =$$
$$R_1 = 12 \text{ Ohms}$$

$$P_2 =$$
$$E_2 = 24 \text{ Volts}$$
$$I_2 =$$
$$R_2 = 8 \text{ Ohms}$$
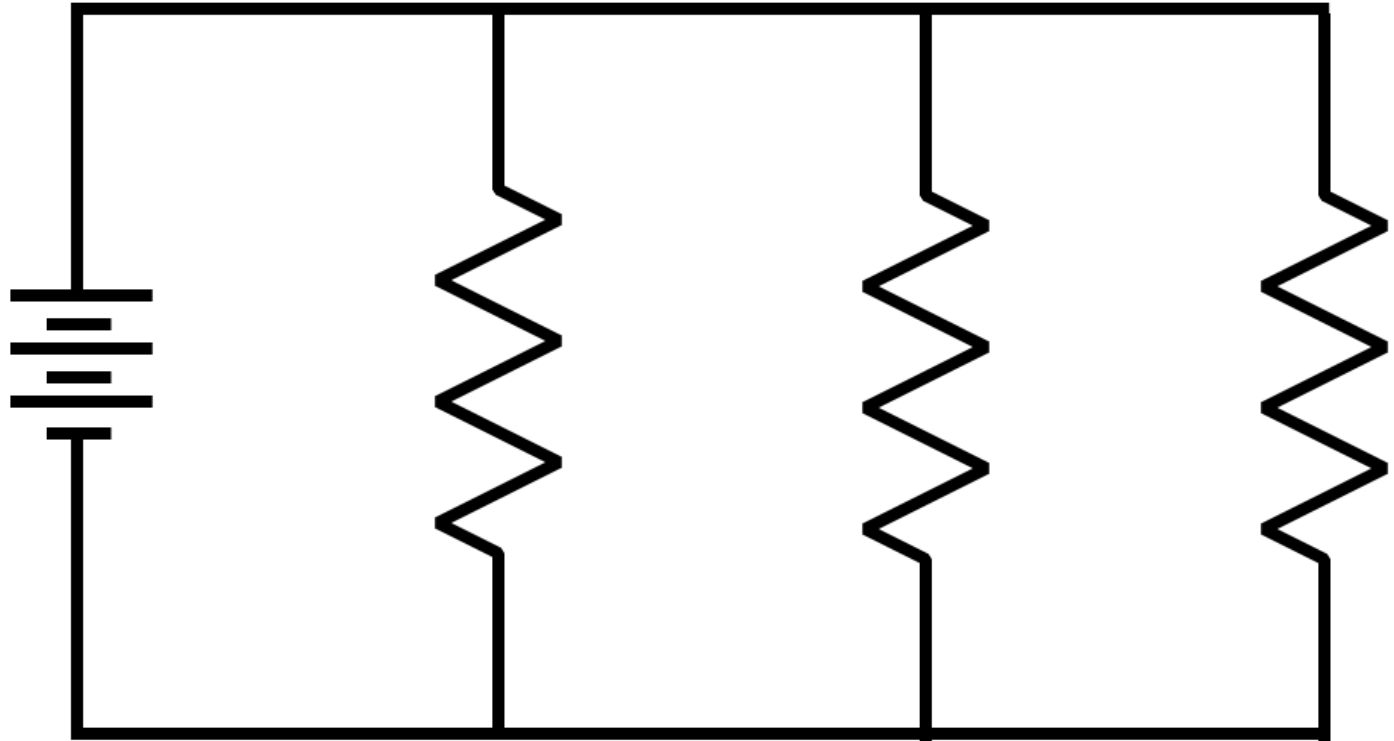
$$P_T = 240 \text{ Watts}$$
$$E_T = 24 \text{ Volts}$$
$$I_T = 10 \text{ Amps}$$
$$R_T = 2.4 \text{ Ohms}$$



$$P_3 =$$
$$E_3 = 24 \text{ Volts}$$
$$I_3 =$$
$$R_3 = 4.8 \text{ Ohms}$$

$$I_T = 10 \text{ Amps}$$

$$R_1 = 12 \text{ Ohms}$$

$$R_2 = 8 \text{ Ohms}$$

$$R_3 = 4.8 \text{ Ohms}$$

Find All Values of P, E, I and R using Ohm's Law and Parallel Rules

Math

$$P_1 = 48 \text{ Watts}$$

$$E_1 = 24 \text{ Volts}$$

$$I_1 = 2 \text{ Amps}$$

$$R_1 = 12 \text{ Ohms}$$

$$P_2 =$$

$$E_2 = 24 \text{ Volts}$$

$$I_2 =$$

$$R_2 = 8 \text{ Ohms}$$


Rule

$$P_T = 240 \text{ Watts}$$

$$E_T = 24 \text{ Volts}$$

$$I_T = 10 \text{ Amps}$$

$$R_T = 2.4 \text{ Ohms}$$

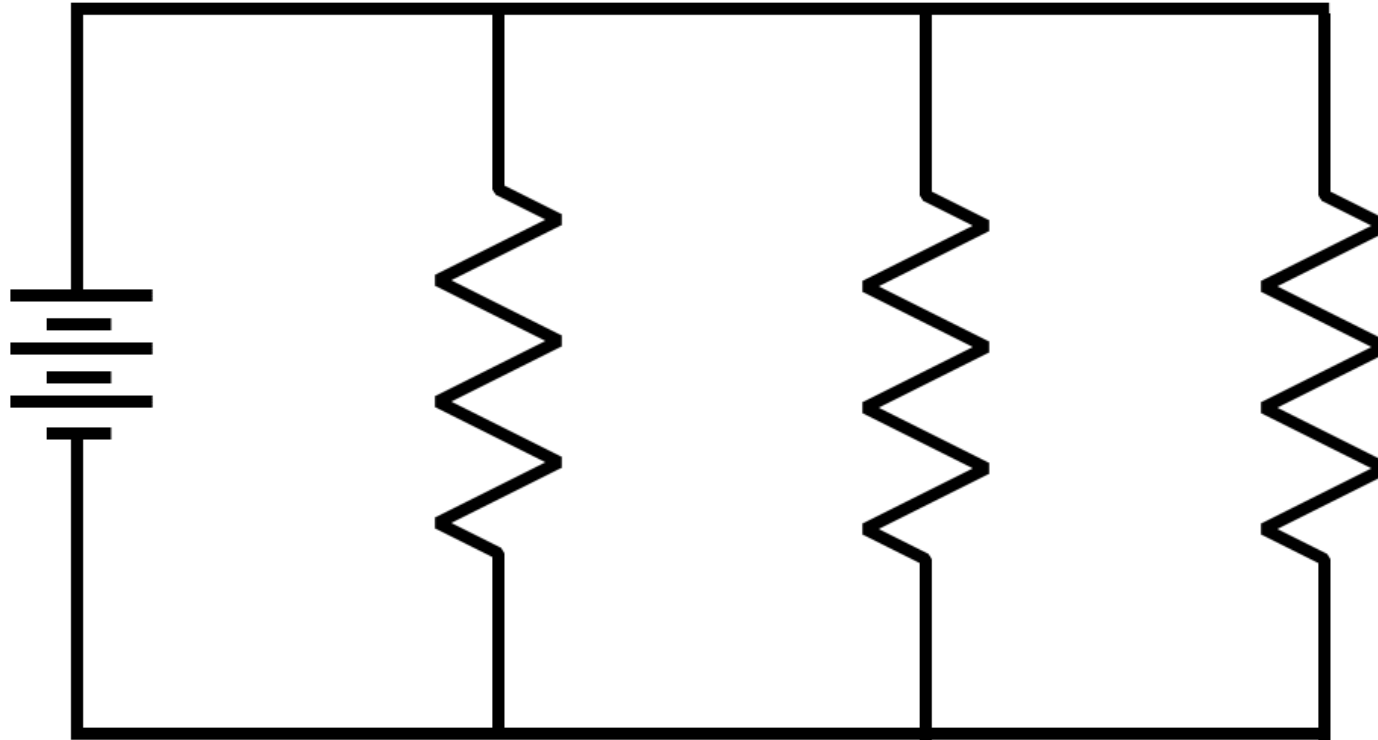

$$P_3 =$$

$$E_3 = 24 \text{ Volts}$$

$$I_3 =$$

$$R_3 = 4.8 \text{ Ohms}$$

$$I_T = 10 \text{ Amps}$$

$$R_1 = 12 \text{ Ohms}$$

$$R_2 = 8 \text{ Ohms}$$

$$R_3 = 4.8 \text{ Ohms}$$

Find All Values of P, E, I and R using Ohm's Law and Parallel Rules

Math

Rule

$$P_1 = 48 \text{ Watts}$$

$$E_1 = 24 \text{ Volts}$$

$$I_1 = 2 \text{ Amps}$$

$$R_1 = 12 \text{ Ohms}$$

$$P_2 = 72 \text{ Watts}$$

$$E_2 = 24 \text{ Volts}$$

$$I_2 = 3 \text{ Amps}$$


$$R_2 = 8 \text{ Ohms}$$

$$P_T = 240 \text{ Watts}$$

$$E_T = 24 \text{ Volts}$$

$$I_T = 10 \text{ Amps}$$

$$R_T = 2.4 \text{ Ohms}$$

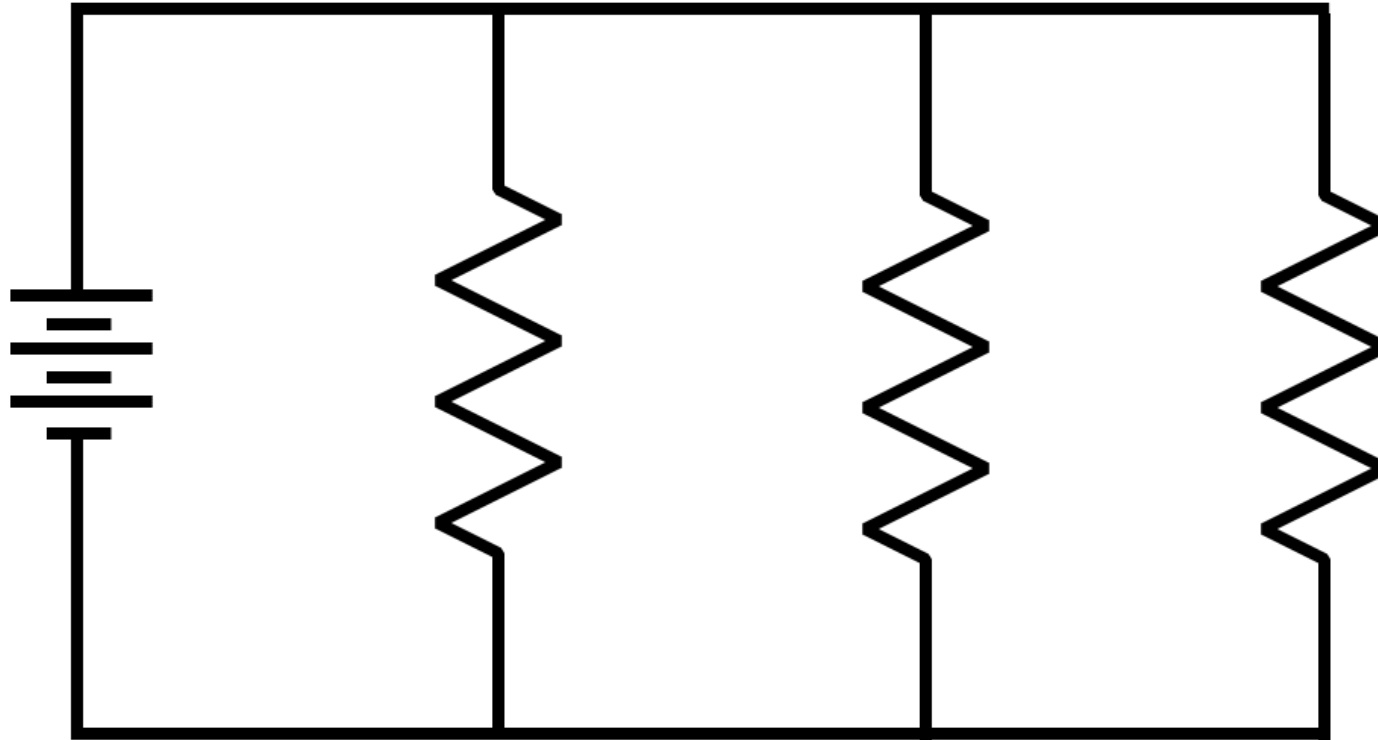

$$P_3 =$$

$$E_3 = 24 \text{ Volts}$$

$$I_3 =$$

$$R_3 = 4.8 \text{ Ohms}$$

$$I_T = 10 \text{ Amps}$$

$$R_1 = 12 \text{ Ohms}$$

$$R_2 = 8 \text{ Ohms}$$

$$R_3 = 4.8 \text{ Ohms}$$

Find All Values of P, E, I and R using Ohm's Law and Parallel Rules

Math

Rule

$$P_1 = 48 \text{ Watts}$$

$$E_1 = 24 \text{ Volts}$$

$$I_1 = 2 \text{ Amps}$$

$$R_1 = 12 \text{ Ohms}$$

$$P_2 = 72 \text{ Watts}$$

$$E_2 = 24 \text{ Volts}$$

$$I_2 = 3 \text{ Amps}$$

$$R_2 = 8 \text{ Ohms}$$

$$P_T = 240 \text{ Watts}$$

$$E_T = 24 \text{ Volts}$$

$$I_T = 10 \text{ Amps}$$


$$R_T = 2.4 \text{ Ohms}$$

$$P_3 = 120 \text{ Watts}$$

$$E_3 = 24 \text{ Volts}$$

$$I_3 = 5 \text{ Amps}$$

$$R_3 = 4.8 \text{ Ohms}$$

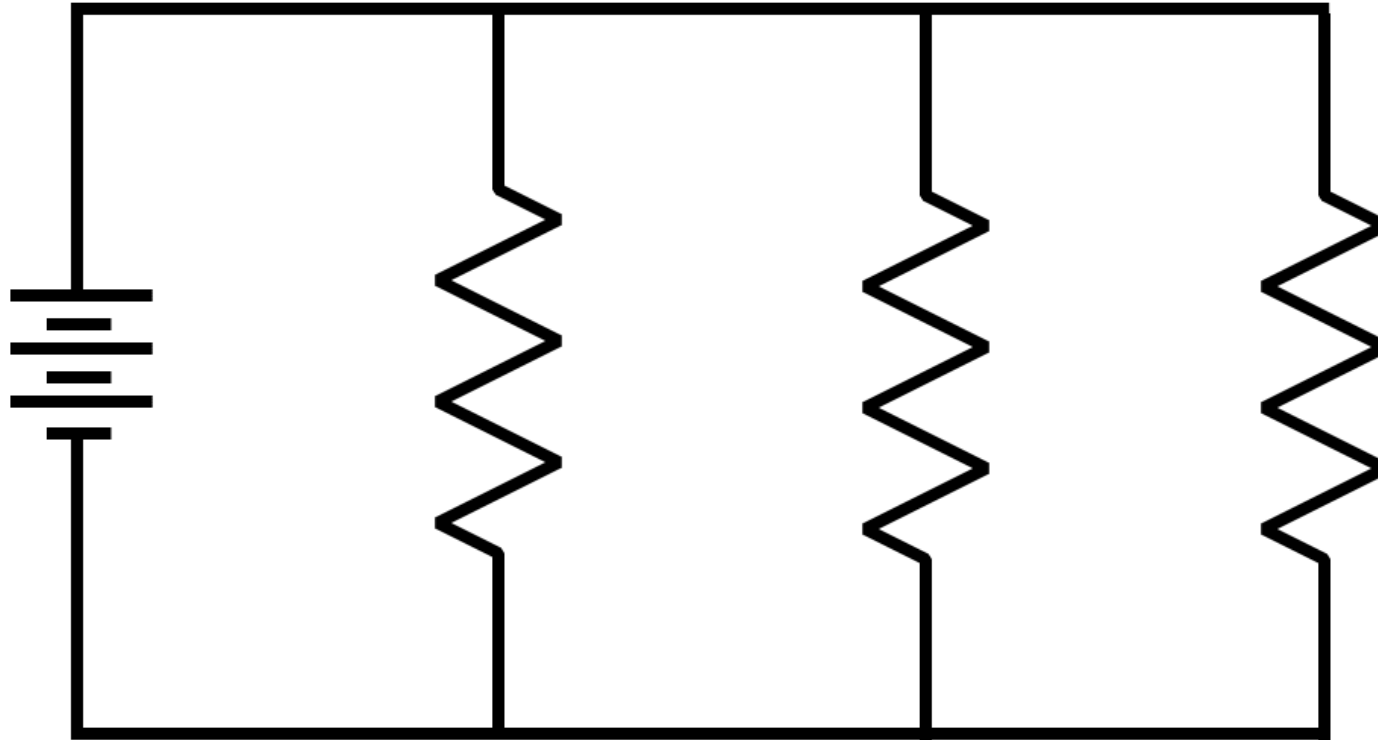

$$I_T = 10 \text{ Amps}$$

$$R_1 = 12 \text{ Ohms}$$

$$R_2 = 8 \text{ Ohms}$$

$$R_3 = 4.8 \text{ Ohms}$$

Find All Values of P, E, I and R using Ohm's Law and Parallel Rules