

Math

Rule

$P_1 =$

$E_1 =$

$I_1 =$

$R_1 =$

$P_2 =$

$E_2 =$

$I_2 =$

$R_2 =$

$P_T =$

$E_T =$

$I_T =$


$R_T =$

$P_3 =$

$E_3 =$

$I_3 =$

$R_3 =$

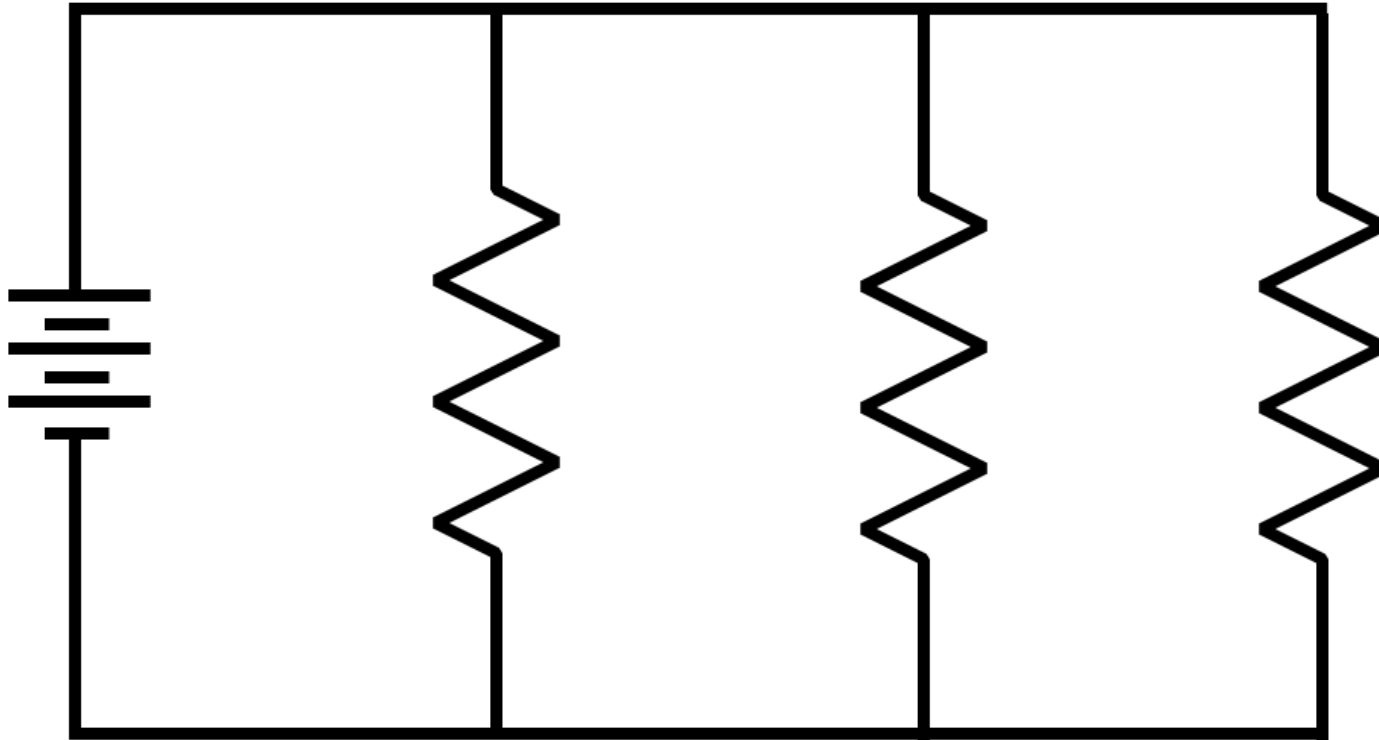

$I_T = 10 \text{ Amps}$

$R_1 = 12 \text{ Ohms}$

$R_2 = 8 \text{ Ohms}$

$R_3 = 4.8 \text{ Ohms}$

Find All Values of P, E, I and R using Ohm's Law and Parallel Rules