

## Star Connected Unbalanced Load

### Power consumed by three phase load

The power consumed by the three phase load is given by sum of power consumed by each individual load in each phase.

$$P = |V_R| |I_R| \cos\theta_R + |V_Y| |I_Y| \cos\theta_Y + |V_B| |I_B| \cos\theta_B$$
$$= V_R I_R \cos\theta_R + V_Y I_Y \cos\theta_Y + V_B I_B \cos\theta_B$$

Where,  $\theta_R$  = Phase difference between  $V_R$  and  $I_R$

$\theta_Y$  = Phase difference between  $V_Y$  and  $I_Y$

$\theta_B$  = Phase difference between  $V_B$  and  $I_B$

Since the current and voltage through each phase is unbalanced the total power can be calculated by using the current and voltage flowing through each phase

$$I_R \neq I_Y \neq I_B$$

$$V_R \neq V_Y \neq V_B$$

Hence the power consumed by the three phase unbalanced load is given by,

$$P = V_R I_R \cos\theta_R + V_Y I_Y \cos\theta_Y + V_B I_B \cos\theta_B$$