## Three Phase Delta Connected Load

## Power consumed by three phase load

The power consumed by the three phase load is given by sum of power consumed by each individual load in each phase.

$$\begin{split} P &= \left| V_{RY} \right| \, \left| I_{RY} \right| \, COS\varnothing_{RY} + \left| V_{YB} \right| \, \left| I_{YB} \right| COS\varnothing_{YB} + \left| V_{BR} \right| \, \left| I_{BR} \right| \, COS\varnothing_{BR} \\ \text{Where,} \\ \theta_{RY} &= \text{Phase difference between } V_{RY} \, \text{and } I_{RY} \\ \theta_{YB} &= \text{Phase difference between } V_{YB} \, \text{and } I_{YB} \\ \theta_{BR} &= \text{Phase difference between } V_{BR} \, \text{and } I_{BR} \\ \text{Since the system is balanced,} \\ \left| V_{R} \right| &= \left| V_{Y} \right| \, = \left| V_{B} \right| \, = \, V \\ \left| I_{R} \right| &= \left| I_{Y} \right| \, = \left| I_{B} \right| \, = \, I \\ \theta_{RY} &= \theta_{YB} \, = \, \theta_{BR} \, = \, \theta \end{split}$$

P=VI cosθ + VI cosθ + VI cosθ= 3 VI cosθ

In balanced delta system,  $V = V_L$  and  $I = I_L / \sqrt{3}$ 

 $P = 3V_{L} (I_{L} / \sqrt{3}) \cos\theta$  $P = \sqrt{3} V_{L} I_{L} \cos\theta$ 

The above equation represents the power consumed by a 3 phase delta connected load.

This expression is same as that of the power in balanced star connected load.