

## Three Phase Delta Connected Unbalanced Load

### **Power consumed by three phase load**

The power consumed by the three phase load is given by sum of power consumed by each individual load in each phase.

$$P = |V_{RY}| |I_1| \cos\phi_{RY} + |V_{YB}| |I_2| \cos\phi_{YB} + |V_{BR}| |I_3| \cos\phi_{BR}$$
$$= V_L I_1 \cos\phi_{RY} + V_L I_2 \cos\phi_{YB} + V_L I_3 \cos\phi_{BR}$$

Where,  $\phi_{RY}$  = Phase difference between  $V_{RY}$  and  $I_{RY}$

$\phi_{YB}$  = Phase difference between  $V_{YB}$  and  $I_{YB}$

$\phi_{BR}$  = Phase difference between  $V_{BR}$  and  $I_{BR}$