

Instantaneous Power of an AC Circuit

In an a.c. circuit the current and emf vary continuously with time. Therefore power at a given instant of time is calculated and then its mean is taken over a complete cycle. Thus, we define instantaneous power of an a.c. circuit as the product of the instantaneous emf and the instantaneous current flowing through it.

The instantaneous value of emf and current is given by

$$e = E_0 \sin \omega t$$

$$i = I_0 \sin (\omega t + \theta)$$

where θ is the phase difference between the emf and current in an a.c. circuit

The average power consumed over one complete cycle is

$$P_{av} = [E_0 I_0 / 2] \times \cos \theta$$

$$P_{av} = E_{rms} I_{rms} \cos \theta$$

Alternate Method

$$\text{Instantaneous power } i \cdot v = V_m \sin \omega t \times I_m \sin (\omega t - \theta)$$

$$= \frac{1}{2} \times V_m I_m [\cos \theta - \cos(2\omega t - \theta)]$$

The instantaneous power consists of two parts

(i) The constant part $(\frac{1}{2}) V_m I_m \cos \theta$ contributing to real power.

(ii) The pulsating component is $\frac{1}{2} \times V_m I_m \cos(2\omega t - \theta)$

This has a frequency twice that of the voltage/current.

It is not contributing to actual power since its average value over a complete cycle is zero.

Therefore, average power consumed $(\frac{1}{2}) V_m I_m \cos \theta = V \cos \theta$ where V and I represent the r.m.s values.

$$\text{Now } P = VI \cos \theta = VI \times (R/Z) = (V/Z) \times I. R = I^2 R \text{ (} \cos \theta = R/Z \text{) or } P = I^2 R \text{ watt}$$

Active and Reactive Components of power

Active component of power is in phase with the applied voltage V i.e. $V.I \cos \theta$. It is known as 'wattful' component.

Reactive component of power is in quadrature with V i.e. $V.I \sin \theta$. It is known as 'wattless' or 'idle' component.

kVA is called the apparent power.

While dealing electric power in general, we use kilowatt as the unit.

$$kW = kVA \cos \theta; kVAR = kVA \times \sin \theta; kVA = \sqrt{(kW)^2 + (kVAR)^2}$$

In an a.c. circuit the current and emf vary continuously with time. Therefore power at a given instant of time is calculated and then its mean is taken over a complete cycle. Thus, we define instantaneous power of an a.c. circuit as the product of the instantaneous emf and the instantaneous current flowing through it.

The instantaneous value of emf and current is given by

$$e = E_0 \sin \omega t$$

$$i = I_0 \sin (\omega t + \theta)$$

where θ is the phase difference between the emf and current in an a.c. circuit

The average power consumed over one complete cycle is

$$P_{av} = [E_0 I_0 / 2] \times \cos \theta$$

$$P_{av} = E_{rms} I_{rms} \cos \theta$$

Alternate Method

Instantaneous power $i_s = v_i = V_m \sin \omega t \times I_m \sin (\omega t - \theta)$
 $= \frac{1}{2} \times V_m I_m [\cos \theta - \cos(2\omega t - \theta)]$

The instantaneous power consists of two parts

(i) The constant part $(\frac{1}{2}) V_m I_m \cos \theta$ contributing to real power.

(ii) The pulsating component is $\frac{1}{2} \times V_m I_m \cos(2\omega t - \theta)$

This has a frequency twice that of the voltage/current.

It is not contributing to actual power since its average value over a complete cycle is zero.

Therefore, average power consumed $(\frac{1}{2}) V_m I_m \cos \theta = V \cos \theta$ where V and I represent the r.m.s values.

Now $P = VI \cos \theta = VI \times (R/Z) = (V/Z) \times I$. $R = I^2 R$ ($\cos \theta = R/Z$) or $P = I^2 R$ watt

Active and Reactive Components of power

Active component of power is in phase with the applied voltage V i.e. $V.I \cos \theta$. It is known as 'wattful' component.

Reactive component of power is in quadrature with V i.e. $V.I \sin \theta$. It is known as 'wattless' or 'idle' component.

kVA is called the apparent power.

While dealing electric power in general, we use kilowatt as the unit.

$kW = kVA \cos \theta$; $kVAR = kVA \sin \theta$; $kVA = \sqrt{(kW)^2 + (kVAR)^2}$