

Series Circuit Rules

- 1) Current remains constant throughout the circuit**
- 2) The total circuit resistance is the sum of all resistance in the circuit**
- 3) The sum of all voltage drops is equal to the source voltage**
- 4) The voltage drop across each resistor will differ depending on the value of the resistor**