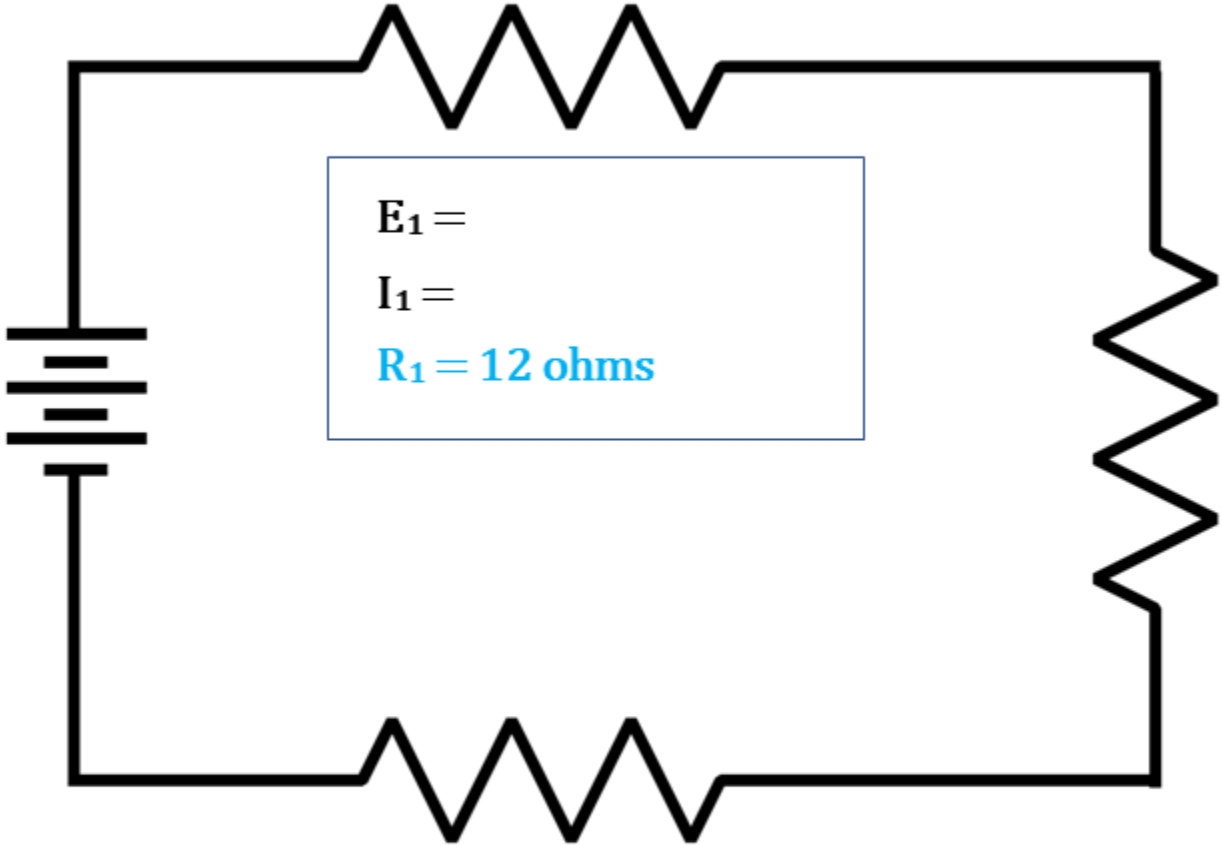


$E_T =$
 $I_T = 1.75 \text{ Amps}$
 $R_T =$



$E_1 =$
 $I_1 =$
 $R_1 = 12 \text{ ohms}$

$E_2 =$
 $I_2 =$
 $R_2 = 4 \text{ ohms}$

$E_3 =$
 $I_3 =$
 $R_3 = 8 \text{ ohms}$