

Parallel Circuit Rules

- 1) Source voltage is applied to all legs in the circuit**
- 2) The total current is the sum of the current flowing in each leg**
- 3) The current flowing through each leg depends on the amount of resistance in each leg**
- 4) The total resistance is always lower than the resistance of the lowest leg**